



The QTC loop antenna  
Real-time clock for Atari ST  
Stepper motor board - Part 1  
Universal battery charger  
Timecode interface - Part 1

# DIGITAL PHASE METER

14 20 32 46 49 54 63



9 770268 451029

06



# CONTENTS

 June 1991  
 Volume 17  
 Number 190

## Apologies

We regret that owing to circumstances beyond our control the "Timecode interface for slide controller" had to be postponed after this month's front cover had already been printed.

## In next month's issue

- As usual in our July issue, more than 50 small but interesting articles presenting new and practical ideas, concepts, and developments on all aspects of electronics

## PLUS

- Timecode interface for slide controller - Part 1
- Multi I/O for IBM
- Black-and-white video digitizer
- Radio data systems
- Modern LED clock
- Logic analyser - Part 5
- Measurement techniques - Part 6
- Laser - Part 3
- One-shot solid-state relay timer
- 8088 single-board computer

## Front cover

This month's project in our measurement series features a digital phase meter. This is a rare instrument, even in the laboratory or workshop of audio and hi-fi engineers. Many engineers and technicians measure phase shift with the aid of an oscilloscope (Lissajous figures). That is not a very accurate method: the phase meter presented is accurate to within  $0.5^\circ$  over the frequency range 10 Hz to 20 kHz.

Copyright © 1991 Elektor BV

**ABC**

 MEMBER OF "THE AUDIT"  
 BUREAU OF CIRCULATIONS

## 13 Main results of the 1991 Young Electronic Designer Awards →

### LEADER

- 11 Telecommunications and safety of human life

### APPLICATION NOTES

- 58 UHF audio/video modulator TDA5664X  
Siemens Components

### COMPUTERS & MICROPROCESSORS

- 60 **PROJECT:** Real-time clock for Atari ST  
by F. Dossche

### GENERAL INTEREST

- 50 **PROJECT:** Laser - Part 2  
an ELV design
- 54 **PROJECT:** Light switch with TV remote control  
by J. Ruffell from an idea by M. Dupessey
- 63 **PROJECT:** Stepper motor board - Part 1  
by N. Kolter

### INTERMEDIATE PROJECT

- 43 Light transmitter-receiver  
by T. Giffard

### POWER SUPPLIES & BATTERY CHARGERS

- 14 **PROJECT:** Universal NiCd battery charger  
by A. Rigby
- 46 **PROJECT:** Variable a.c. power supply  
by L. Lemon

### RADIO, TELEVISION & COMMUNICATIONS


- 27 **PROJECT:** Video A-D and D-A converter - Part 2  
by P. Godon (Philips Components, Paris)
- 40 **PROJECT:** The QTC loop antenna  
by Richard Q. Marris, G2BZQ

### TEST & MEASUREMENT


- 20 **PROJECT:** Logic analyser - Part 4  
by K. Nischalke and H.J. Schulz
- 32 **PROJECT:** Digital phase meter  
by R. Lucassen
 
### MISCELLANEOUS INFORMATION


Events 13; Corrections 49; Switchboard 68; Terms of business 68; Readers services 69; Index of advertisers 74.



 
A picture to restore or increase your faith in youth and electronics: this young lady, Polyanna Robinson, who is only 14, won first prize in the Junior Category of the YEDA awards see page 13



QTC loop antenna - p. 40

 

Variable a.c. power supply - p. 46

 

Laser - p. 50



# TELECOMMUNICATIONS AND SAFETY OF HUMAN LIFE

**T**HE DAY after this issue of *Elektor Electronics* reaches the newsstands, Friday 17 May, is World Telecommunication Day, celebrated every year by member countries of the International Telecommunication Union—ITU. It is the date of signature in Paris, in 1865, of the first International Telegraph Convention which set up the International Telegraph Union, the forerunner of today's ITU.

This year, World Telecommunication Day is celebrated as part of the Natural Disaster Prevention Decade proclaimed by the United Nations General Assembly. Other international organizations, whose activities are significantly dependent on telecommunications, have therefore been associated to the celebrations: the International Civil Aviation Organization (ICAO), the International Maritime Organization (IMO), the World Meteorological Organization (WMO), the Office of the United Nations Disaster Relief Co-ordinator (UNDRO), and the League of Red Cross and Red Crescent Societies.

The topic chosen for this year by the Administrative Council of the International Telecommunication Union is *Telecommunications and safety of human life*.

Radio was first used to save life at sea in March 1899, when it was used by a lightship to report that the steamer *Elbe* had run aground. It was also in 1899 that the first ship was fitted with radio. Since that time, radiocommunications has proved to be of paramount importance to safety at sea.

In 1912, some three months after the passenger ship *Titanic* disaster occurred with the loss of more than 1500 lives, an international radio conference met in London to review and amend the 1906 International Radiotelegraph Convention which prescribed the distress and calling frequencies, classes of ship service (watchkeeping), ship's radio equipment, and requirements for certification of operators for ship stations. Later, in January

1914, also in London, an international maritime conference adopted the first International Convention for the Safety of Life at Sea (SOLAS), which required certain ships to carry an MF radiotelegraph installation.

## The existing distress system

The subsequent 1929, 1948, 1960 and 1974 SOLAS Conventions all required passenger ships and cargo ships of 1600 tons gross and upwards to carry a radiotelegraph station. It was not until 1948 that requirements for MF radiotelephone stations were included in the convention and then only for ships of between 300 and 1600 tons gross not fitted with an MF radiotelegraph station. Limited requirements for a VHF radiotelephone station for safety of navigation were included in SOLAS in 1974, but it was not until 1981 that requirements for all SOLAS ships to be capable of communicating with each other by VHF and MF radiotelephone were achieved.

Subsequent World Administrative Conferences (WARC) convened by the ITU provided the radiotelephone distress call, radiotelephone distress and calling frequencies, and reduced the distress bands as radio technology and equipment improved.

Until 1960, when IMO came into being, the ITU was solely responsible for all aspects of maritime radiocommunications, including distress and safety radiocommunications. The 1960s saw great changes and improvements in radiocommunication systems, e.g., satellite communications, selective calling, direct-printing telegraphy, etc. Both ITU and IMO recognized the advantages of these systems for improving all maritime radiocommunications.

The existing morse radiotelegraphy and radiotelephone system, with a required MF communication range of 100–150 nautical miles, provided a distress system based, if time permitted, on alerting ships in the vicinity

of the distress and coast stations within range. The system therefore did not cover ships that sank suddenly or ships in distress that were too far away from those who could assist.

## Improvement of maritime radio-communications

In February 1966, IMO decided to study the operational requirements for a maritime satellite communication system and in 1967 the ITU WARC invited IMO to continue this work.

In the early 1970s, IMO, in close co-operation with ITU's International Radio Consultative Committee (CCIR), started active preparations for the establishment of a maritime satellite communication system to serve the maritime community. This work resulted in 1979 in the establishment of the International Maritime Satellite Organization INMARSAT.

In 1973, IMO adopted a policy document on the development of the maritime distress system, which outlined the steps that should be taken to gradually improve the existing system and ultimately achieve what was then the distant future system and is now known as the Global Maritime Distress and Safety System (GMDSS).

IMO also sought to improve search and rescue (SAR) world-wide for those in distress at sea and, concurrent with the development of the INMARSAT Convention, prepared the SAR Convention, which was adopted in 1979. Under the convention, SAR is based upon co-ordination of all SAR operations, wherever they occur in the world, by responsible authorities ashore (rescue co-ordination centres (RCCs)). As MF and VHF communications have limited range, in order to enable RCCs to meet their responsibilities under the SAR Convention, ships operating outside the MF range need a long-range HF or satellite communication capability. →

Produced and published by **ELEKTOR ELECTRONICS (Publishing)**

**Editor/publisher:** Len Seymour

**Technical Editor:** J. Buiting

**Editorial Offices:**

Down House  
Broomhill Road  
LONDON SW18 4JQ  
England

**Telephone:** 081-877 1688 (National)  
or +44 81877 1688 (International)

**Telex:** 917003 (LPC G)

**Fax:** 081-874 9153 (National)

or +44 81874 9153 (International)

**Advertising:** PRB Limited

3 Wolsey Terrace  
CHELTENHAM GL50 1TH  
**Telephone:** (0242) 510760  
**Fax:** (0242) 226626

**Subscriptions:**

World Wide Subscription Service Ltd.  
Unit 4, Gibbs Reed Farm  
Pashley Road

TICEHURST TNS 7HE

**Telephone:** (0580) 200657 (National)

or +44 580 200 657 (International)

**Telefax:** (0580) 200616 (National)

or +44 580 200 616 (International)

**European Offices:**

Postbus 75

6190 AB BEEK

The Netherlands

**Telephone:** +31 46 38 94 44

**Telex:** 56617 (elekt nl)

**Fax:** +31 46 37 01 61

**Managing Director:** M.M.J. Landman

**Distribution:**

SEYMOUR

1270 London Road

LONDON SW16 4DH

**Printed in the Netherlands by NDB,**

Zoeterwoude

**Overseas editions:**

**FRANCE**

Elektor srl

Les Trois Tilleuls

B.P. 59; 59850 NIEPPE

**Editors:** D.R.S. Meyer-G.C.P. Raedersdorf

**GERMANY**

Elektor Verlag GmbH

Süsterfeld Straße 25

5100 AACHEN

**Editor:** E.J.A. Krempelsauer

**GREECE**

Elektor EPE

Kariskaki 14

16673 Voula - ATHENA

**Editor:** E. Xanthoulis

**INDIA**

Elektor Electronics PVT Ltd

Chhotani Building

52C, Proctor Road, Grant Road (E)

BOMBAY 400 007

**Editor:** C.R. Chandarana

**ISRAEL**

Elektorcal

P O Box 41096

TEL AVIV 61410

**Publisher:** M. Avraham

**NETHERLANDS**

Elektuur BV

Peter Treckpoelstraat 2-4

6191 VK BEEK

**Editor:** P.E.L. Kersemakers

**PORTUGAL**

Ferreira & Bento Lda.

R.D. Estéfani, 32-1<sup>o</sup>

1000 LISBOA

**Editor:** Jeremias Sequeira

**SPAIN**

Resistor Electronica Aplicada

Calle Maudes 15 Entlo C.

28003 MADRID

**Editor:** Agustín Gonzales Buelta

**SWEDEN**

Electronic Press AB

Box 5505

14105 HUDDINGE

**Editor:** Bill Cedrum

**USA & CANADA**

Elektor Electronics USA

P O Box 876

PETERBOROUGH NH 03458-0876

**Publisher:** Edward T. Dell



Continued from page 11

### Development of the GMDSS

The advent of INMARSAT enabled the development of the GMDSS through a carefully considered integration of satellite and modern terrestrial radiocommunication techniques and procedures. Development of the GMDSS required very close co-operation between ITU and IMO. In general, IMO are developing the operational requirements, while the ITU through CCIR recommend the technical specifications of the equipment and procedures for its use.

In the late 1970s, several countries, particularly the United States and the USSR, began experiments with satellites that resulted in the COSPAS-SARSAT system being established well before implementation of the GMDSS. Since that time, the system has provided a significant contribution to SAR operations and has assisted in saving hundreds of lives.

In the later 1970s, IMO, in co-operation with IHO, established the world-wide navigation warning service (WWNWS) for the co-ordination and broadcast of navigational warnings to ships. Since 1929, Contracting Governments to the SOLAS Convention have undertaken to broadcast meteorological warnings and forecasts to ships and to make arrangements for the reception of danger warnings and meteorological reports, co-ordinated

by WMO through its world weather watch (WWW), from ships. These matters, together with broadcasts of SAR and other urgent information, provide the maritime safety information (MSI) element of the GMDSS.

The GMDSS will be fully implemented in 1999 when, except possibly for a few remaining stations, use of morse radiotelegraphy by ships will cease after 100 years of dedicated and faithful service.

The concept of the GMDSS is based on the use of the most up-to-date radiocommunication technologies to provide a comprehensive distress and safety system of communication between ships and between ships and the shore and vice versa wherever in the world the ships may be situated. The functional requirements of the GMDSS include transmitting and receiving ship-to-shore and shore-to-ship distress alerts, ship-to-ship distress alerts, SAR co-ordinating communications, on-scene communications, signals for locating, maritime safety information (MSI), general radiocommunications, and bridge-to-bridge (navigational) communications.

### Implementation of the GMDSS


Implementation of the GMDSS will be phased to allow for equipment redundancy:

1. all ships to be fitted with a NAVTEX receiver and satellite EPIRB by 1 August 1993;

2. all ships constructed before 1 February 1992 to be fitted with a radar transponder and two-way radiotelephone apparatus for survival craft by 1 February 1995;
3. all ships constructed after 1 February 1995 to comply with all appropriate requirements for the GMDSS;
4. all ships to be fitted with at least one radar capable of operating in the 9 GHz band by 1 February 1995;
5. all ships to comply with the appropriate requirements for the GMDSS by 1 February 1999.
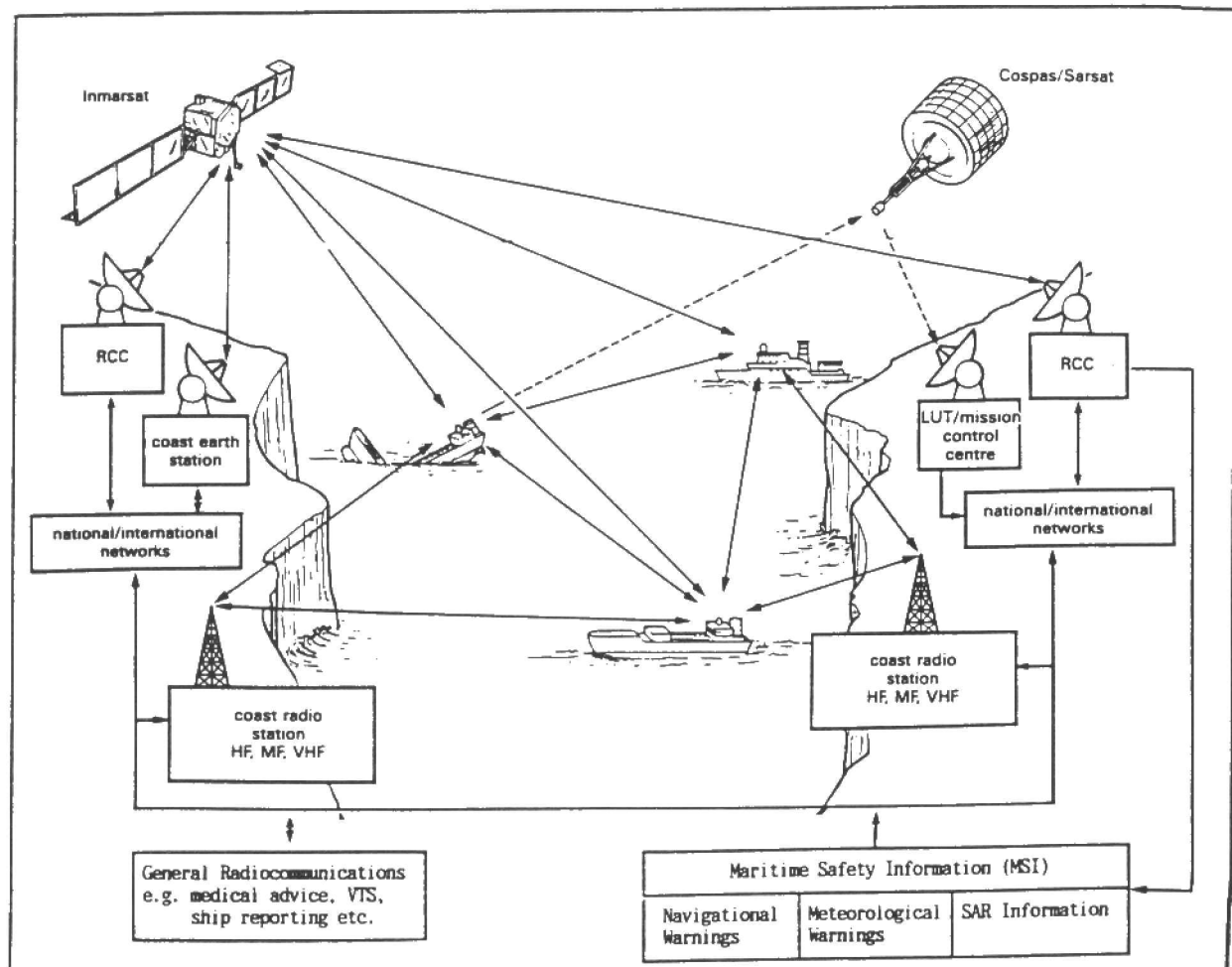
### Emergency distress alerting capability

A distress alert capability in case the ship sinks suddenly or the radio station is destroyed is provided by a satellite emergency position-indicating radio beacon (EPIRB) that is capable of floating free from the sinking ship and being automatically actuated and transmitting the ship's identity and either its position (INMARSAT) or a signal that provides the ship's position (COSPAS-SARSAT). The satellite EPIRB is portable and can be carried into survival craft, which will also be equipped with portable VHF transceivers, on-scene communications and search and rescue radar transponders (SARTs) for final location by SAR units arriving at the distress position. ■



General concept of the GMDSS



HRH The Duchess of York presented the 1991 Young Electronic Designer Awards on 3 April at the Science Museum, London. The Senior Category was won by Stephen Brown of the Royal Naval Engineering College, Plymouth; the Intermediate Category was won by Jonathan Saville of the Queen Elizabeth Grammar School, Wakefield; and the Junior Category was won by Polyanna Robinson of The Godolphin School, Salisbury.

The Texas Instruments' Prize of £2,500 for the most commercially viable project was awarded to Polyanna Robinson.

The Mercury Communications 'Planet Award', also worth £2,500, for the most environmentally and socially aware technology went to Jonathan Saville.

The Duchess praised the work of all 21


## RESULTS OF THE 1991 YOUNG ELECTRONIC DESIGNER AWARDS

finalists, saying how much she admired their ingenuity and their understanding of the science of electronics. The 21 young designers, whose ages ranged from 12 to 24, came from 15 different educational establishments in all parts of the UK.

YEDA is sponsored jointly by Texas Instruments Ltd and Mercury Communications Ltd. Ken Sanders, managing director of TIL, said: "A venture like YEDA requires a commitment of years, rather than days. Sponsorship is more than just signing cheques. Sponsors should also try to provide ideas and dy-

namism which will contribute to the *life* of the venture. This is why we are finding ways in which completed YEDA projects can be given a much wider audience among the general public".

 Peter van Cuylenburg, Mercury's chief executive, added: "Mercury's co-sponsorship of the YEDA awards and the introduction of the Planet Award underline our determination to encourage new talent and our concern for the well-being of our planet. By donating this award, we hope to encourage the development of safer and environmentally sympathetic technology". ■



HRH The Duchess of York and Professor John Eggleston, Chairman of the YEDA Board of Trustees, discuss Polyanna Robinson's Quizmaster. This device, which indicates the first contestant to respond to a question in a game, earned Polyanna (14) first place in the Junior Category.



Jonathan Saville (16) discusses his project, an electronic automated self-contained river water pollution monitor, with HRH The Duchess of York.



First place in the Senior Category went to Stephen Brown (24), who developed a system that interactively displays images from the AutoCad design package.

## IEE AND IEEE PROGRAMME

- 3 June—Inspection and testing of electrical installations.
- 4 June—Loud and clear—obtaining intelligible public address at stations.
- 5 June—Transparent optical networks in Europe.
- 5 June—High frequency resonant power supplies.
- 10 June—Testing tomorrow's technology today.
- 10–12 June—Reliability '91. International conference at the Royal Lancaster Hotel, London. Details from R. Matthews, AEA Technology, Wigshaw Lane, Culcheth, Warrington WA3 4NE, (0925) 31244.
- 11 June—Broadcasting traffic information.
- 12 June—Practical methods for robust control system design.
- 12 June—Satellite antenna technology for the 21st century.
- 14 June—Software in air traffic control systems.
- 14 June—National Library of Scotland—phase 1: electrical system and lighting.
- 17 June—Electronic CADMAT in teaching.
- 17 June—16th Edition—IEE wiring regulations.
- 20–22 June—Television measurements (Fourth International Conference, Montreux).

## EVENTS

- 21 June—Embedded software control systems.
  - 24 June—Measurement uncertainties for Europe—Is there a common approach?
  - 27 June—Electromagnetic compatibility for project engineers.
- Information on these, and many other, events may be obtained from the IEE, Savoy Place, London WC2R 0BL, Telephone 071 240 1871 or the IEEE, Savoy Hill House, Savoy Hill, London WC2R 0BS, Telephone 071 836 3357.

An easy-to-use character generator, cable communal systems, an in-line recording console and a newsroom autocue are among many new products that will feature on the stands of more than 40 British companies taking part in the **TV Symposium and Exhibition** in Montreux from 13 to 18 June. The group is being organized by the Electronic and Business Equipment Association in co-operation with the Department of Trade and

Industry. In addition, the Association will mount an information stand where any enquiries about the exhibits or the industry may be directed.

Details from the Department of Trade and Industry, 1–19 Victoria Street London SW1H 0ET; telephone 071 215 5000.


This month, Frost & Sullivan will conduct seminars on **ISDN Protocols and implementation; An introduction to telecommunications; the OSI reference model; X.25 and packet switching networks; Digital cellular telephony; What's new in IBM's SNA?; and Advanced packet switching.** Details from Frost & Sullivan, Sullivan House, 4 Grosvenor Gardens, London SW1W 0DH, Telephone 071 730 3438.



# UNIVERSAL Ni-Cd BATTERY CHARGER

by A. Rigby

 **Ni-Cd batteries are now used in so much everyday equipment that most households need at least one suitable charger. The one presented here can be used to charge virtually all current Ni-Cd batteries.**



THE charger is based on the Telefunken Type U2400B processor, which has been specially developed for this application. This device contains most of the logic circuits necessary for automatically controlling the charging of Ni-Cd batteries.

Initially, charging takes place during a pre-determined period of time, after which trickle charging takes over. The trickle charging, which may continue for long periods of time, ensures that the battery capacity does not degrade during the life of the battery.

The charger has a number of safety features. For instance, if the temperature of the battery becomes too high or when the e.m.f. of the battery rises above a certain (pre-determined) value, the charging cycle is discontinued immediately. The processor then assumes its stand-by mode and remains there until the temperature or the e.m.f. drops below its limiting value.

A flow diagram of the charging process is given in Fig. 2. After the battery has been connected and the start reset operated, the processor first arranges for the battery to be discharged. During the discharge cycle, the temperature of the battery ( $T < T_{max}$ ) and its e.m.f. ( $U < U_{min}$ ) are monitored continually. When the e.m.f. drops to the level of  $U_{min}$ , the processor assumes that the battery has been discharged completely, and sets its discharge register. The circuit then switches to the charging mode. During charging the elapsed charging time is compared with the preset charging time ( $t > t_{max}$ ) and the e.m.f. with the maximum (preset) voltage ( $U > U_{max}$ ). Furthermore, the content of the discharge register and the battery temperature are monitored constantly. At the end of the preset charging time ( $t > t_{max}$ ), the charging cycle is terminated and the processor actuates the trickle charging mode.

As already mentioned, if during charging one of the preset parameters is exceeded, charging is discontinued. At the same time, the status of the error register is increased by 1 and reread. If no error occurred previ-

ously, the status of the counter after the present error will be smaller than  $2(Z < 2)$ . If the counter status is smaller than 2, the e.m.f. and temperature of the battery are checked once again; if these are all right, the charging process is continued. If the content of the error register is greater than, or equal to, 2, charging is continued or stopped, depending on the position of a switch as explained later.

As is seen in Fig. 1, the processor needs only a few external components to perform the functions discussed so far. During the discharge cycle, the e.m.f. of the battery is monitored via  $U_{min}$  (pin 6). In this, use is made of a switchable voltage divider,  $R_{35}-R_{43}-R_3-P_2$ , which attenuates the battery voltage. During the discharge cycle, output DIS(charge) (pin 10) is active and high. The discharging is assumed complete when the voltage level at pin 6 drops below the level (0.53 V) of the internal reference voltage.

During charging, output LOAD (pin 12) becomes active and high; the battery voltage is then applied to pin 4 ( $U_{max}$ ) via potential divider  $R_{35}-R_{43}-R_2-P_1$ . If the voltage at pin 4 is higher than the internal reference potential, the processor switches to the stand-by mode.

Since it is important for the user to know in which state the processor is, two LEDs are driven via STATUS output pin 9. Table 1 shows the operation of these diodes in the various modes.

A reference voltage of 3 V (nominal) is applied to pin 7, the PWM input, switch  $S_1$ , network  $R_4-C_2$ , voltage divider  $R_5-R_6$  and the two series-connected LEDs.

Series combination  $R_4-C_2$  at the input of the internal oscillator, pin 3, is a fre-

quency-determining network.

Monitoring of the battery temperature is accomplished by  $R_6$ , which has a negative temperature coefficient. The potential at junction  $R_5-R_6$  is monitored via input  $U_{temp}$  (pin 5). The charging process is stopped when the battery temperature reaches  $40^\circ\text{C}$ ; the resistance of  $R_6$  is then about  $440\Omega$ .

The position of switch  $S_1$  determines the selection made by the processor when two or more errors in the charging process have been signalled. If the switch is connected to the reference voltage, charging is continued even when two (but no more) errors have occurred; if it is connected to earth, however, full charging is discontinued and trickle charging commenced.

The charging time is preset via the TIME input, pin 13. When the internal 200 Hz oscillator is used, a high level at pin 13 sets the charging time to 1 hour. When the pin is connected to earth (low level), the charging time is 30 minutes.

The timer may also be driven by an ex-

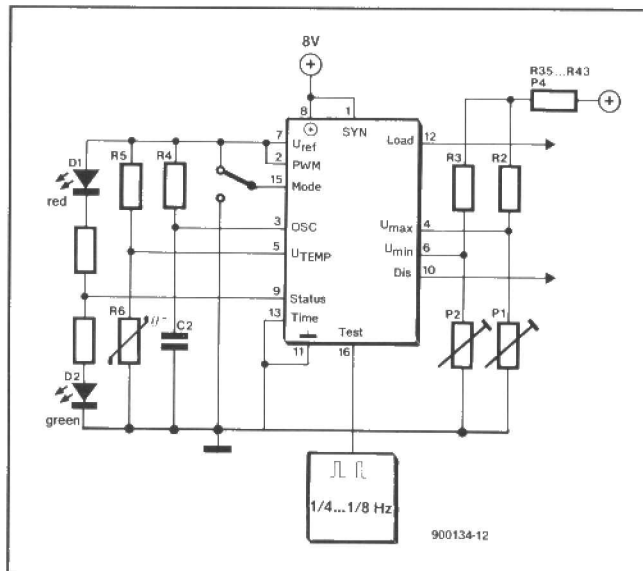


Fig. 1. Basic circuit for the U2400B processor.



Table 1

D <sub>1</sub>	D <sub>2</sub>	S <sub>1</sub>	Function
(red) on	(green) off	X	no battery connected; battery faulty or battery flat
flashes	off	X	discharge cycle
off	flashes	X	charging cycle
off	on	X	trickle charge mode
flashes	flashes	E	charging continues after two errors
on	off	D	trickle charging after two errors

X = irrelevant

E = connected to  $U_{ref}$ 

D = connected to earth

ternal clock, connected to pin 16; pin 13 must then be earthed. The internal 200 Hz oscillator then provides the clock signals for the remaining functions of the processor. A frequency of 0.5 Hz at pin 16 sets the charging time to 1 hour; halving that frequency doubles the time. An external clock based on a 4060 IC as shown in Fig. 8 can provide frequencies down to 0.125 Hz, which would give a charging time of 4 hours.

## Charging

In a practical charger, the processor does not drive a simple transistor, but a fairly complex current source, controlled as shown in Fig. 3. The charging current flows through  $R_{22}$ , resulting in a potential drop across this resistor that is directly proportional to the charging current:

$$U_{R22} = I_{load} R_{22}.$$

This voltage is used for controlling the charging current. Note that the negative battery voltage,  $U_{bat}$ , is in reality more positive than the supply voltage,  $U_V$ , because the positive terminal of the battery is connected to a second, higher supply voltage.

Since transistor  $T_5$  is connected as a diode, the emitter of  $T_6$  is connected to  $U_V$  at all times. Therefore, the potential drop across the emitter resistor,  $R_e$ , which is the equivalent of  $R_{29}-R_{34}-P_6$  in Fig. 8, is exactly the same as that across  $R_{22}$ :

$$U_{Re} = U_{R22} = I_{Re} R_e.$$

As an example, assume that  $R_{22} = 0.1 \Omega$ ,  $I_{load} = 1 \text{ A}$ , and that a current of 1 mA is required through the transistor. The drop across  $R_{22}$  is 100 mV, so that

$$R_e = 100 \times 10^{-3} / 10^{-3} = 100 \Omega.$$

Since the emitter current is now known, the voltage drop across the collector resistor is:

$$U_{Rc} = 1.2 \times 10^3 \times 10^{-3} = 1.2 \text{ V}.$$

This makes it clear that a change in the charging current results in a change in the voltage at  $F_B$ . That voltage may, therefore, be used for the control of a regulatory circuit in a switch-mode power supply.

 


Fig. 3. Part of the circuit controlling the charging current.

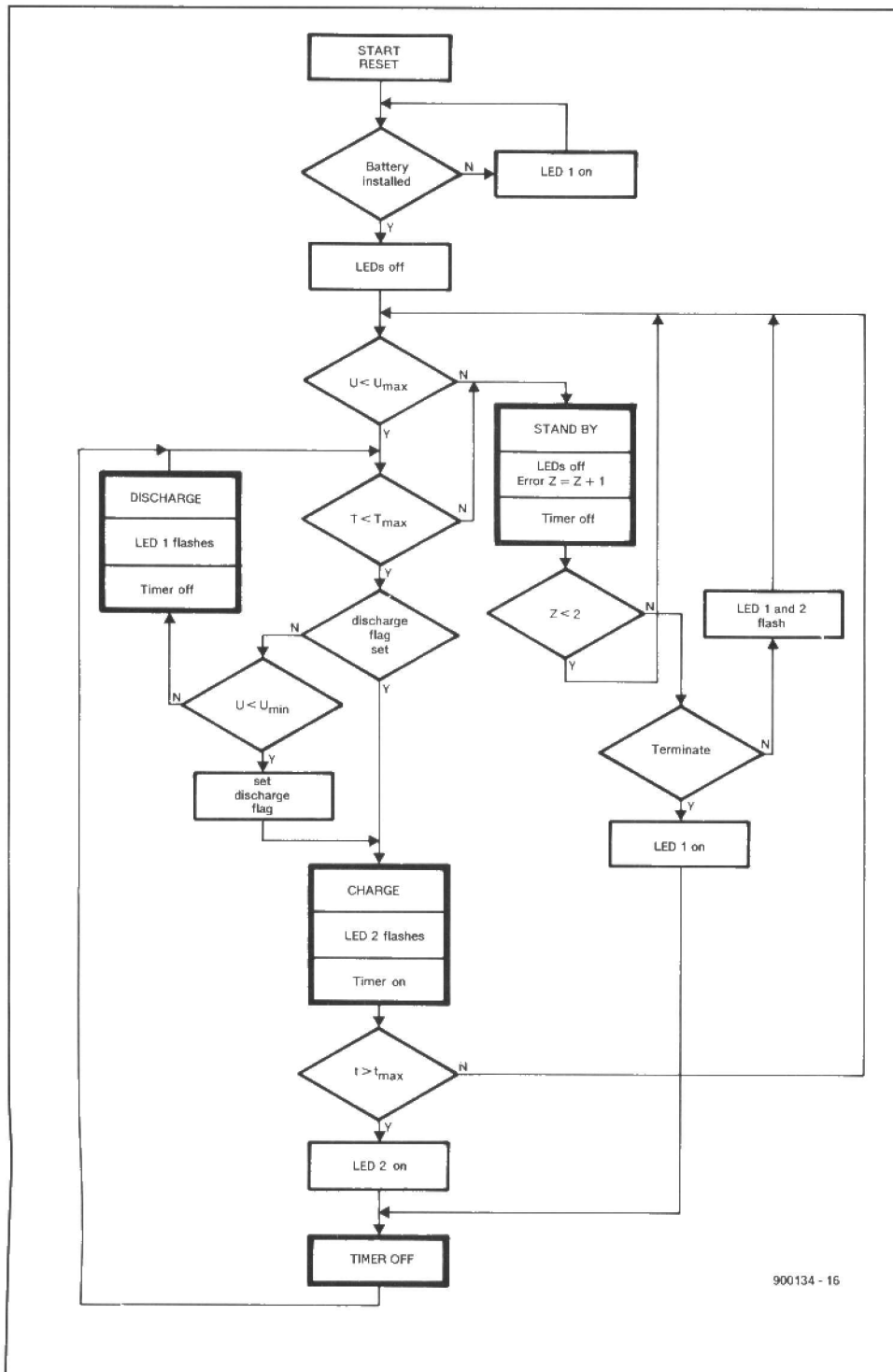


Fig. 2. Flow diagram of the battery charger.

## Switch-mode power supply

A switch-mode power supply is used to enable the charger to cater for the simultaneous charging of, say, up to ten batteries; a conventional mains supply could be used, but the dissipation in this will be quite large when only a few batteries are being charged.

 


Fig. 4. Concept of a switch-mode power supply.

The basic operation of such a supply is shown in Fig. 4. Electronic switch *S* is switched on and off by electrical circuits. When it is closed, a current  $i_1$  flows from the  $\oplus$  supply terminal to earth via inductor *L*, resulting in a magnetic field around the inductor. Diode *D* is switched off and capacitor *C*, therefore, has no influence on the circuit, although it can discharge via load resistance *R* (representing the batteries to be charged).

When *S* is opened, the self-inductance of *L* causes a current  $i_2$  in the opposite direction from  $i_1$  and this charges *C* via the diode.

The level of output voltage  $U_2$  depends on the properties of the inductor, the switching logics and the on-off ratio of the switch. In the present charger, a commercial inductor is used: it is not advisable to wind this yourself.

The circuit of the supply used is shown in Fig. 5. It is based on Linear Technology's Type LT 1070. A 40 kHz oscillator provides a train of rectangular pulses that are used to switch a transistor via a driver stage. The duty factor is determined primarily by the output voltage of the (differential) error amplifier.

The collector voltage of  $T_6$  is 1.2 V when the regulator is in a stable condition. Because of its internal reference voltage of 1.24 V, the error amplifier then has no effect on the switching behaviour of the output transistor. When the charging current increases to too high a level,  $U_c$  rises, and the output of the error amplifier goes low. This results in an alteration of the on-off ratio of the transistor, which lowers the charging current.

Zener diode  $D_6$  limits the voltage to 18 V.

## Discharging

The discharge circuit shown in Fig. 6 has some points in common with the circuit in Fig. 3. Again, use is made of the voltage drop across emitter resistor  $R_{22}$ . The supply voltage and the battery voltage have, of course, changed places, since the discharge current flows into a different direction from the charging current.

The non-inverting input of the comparator in the collector circuit of  $T_3$  is held at 2.7 V by zener diode  $D_3$ .

The value of  $R_{14}$  is determined by the collector current (1 mA) and the reference voltage:

$$R_{14} = 2.7 / 10^{-3} = 2.7 \text{ k}\Omega.$$

The connected batteries are discharged via  $R_{22}$  and  $T_8$ , which, with  $T_7$ , forms a darlington at the output of the comparator.

## Voltage monitoring

The processor continually monitors the battery voltage via its pins 4 and 6. Since these inputs measure the voltage with respect to earth and the negative terminal of the battery is connected to the  $\oplus$  supply rail, a simple circuit like that in Fig. 1 can not be used. This means that the battery voltage must be converted so that it *can* be measured with respect to earth.

To this end, a network as shown in Fig. 7 is used. The entire battery voltage is dropped across the emitter resistance,  $R_e$ , consisting

of resistors  $R_{35}$ – $R_{43}$ —see Fig. 8. Since  $R_e$  has a value of 1 k $\Omega$  per connected battery, the collector current,  $I_c$ , through  $T_1$  is

$$I_c = n \times U_z / n \times R_e = U_z / R_e,$$

where  $U_z$  is the zener voltage.

When the batteries are charged, the collector current is  $1.45 / 10^3 = 1.45 \text{ mA}$ , and the voltage drop across  $R_1$  and potential dividers  $R_2$ – $P_1$  and  $R_3$ – $P_2$  is 1.74 V. This voltage has the correct polarity with respect to earth. The correct operating point is set with the two potentiometers: how many batteries are connected to the charger is then no longer of importance.

## The complete circuit

Large parts of the diagram in Fig. 8 have already been discussed. Note that the switch-mode power supply operates only if pin 1 of the LT 1070 is connected to earth via the LOAD output of the processor and  $T_4$ .

Since the resistors at like positions of  $S_{4a}$  and  $S_{4b}$  have the same value, the discharge and charging currents of batteries are iden-

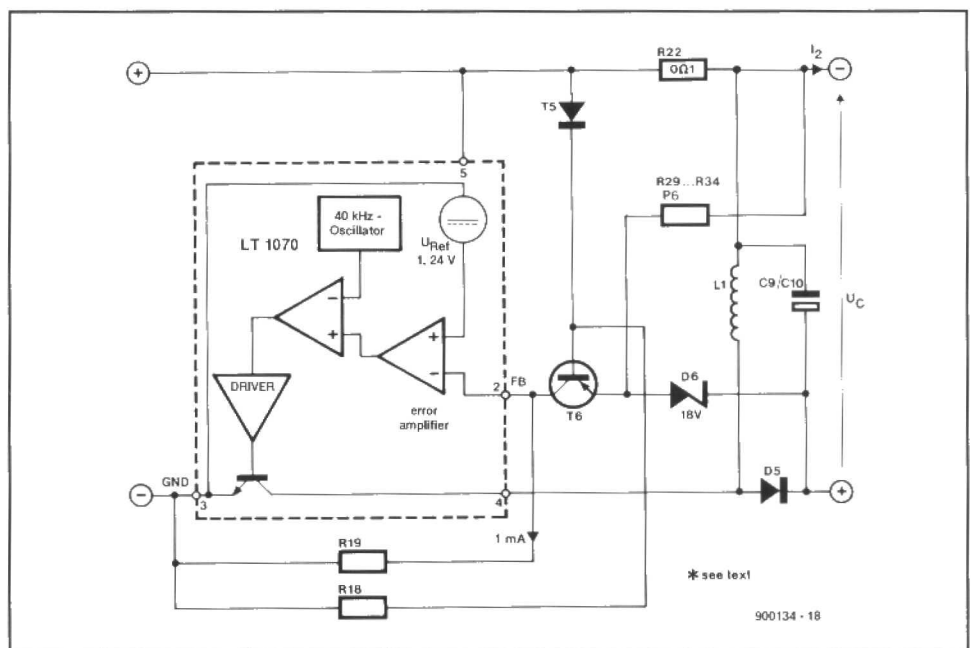


Fig. 5. The switch-mode power supply – see also Fig. 8.

 


Fig. 6. Circuit for controlling the discharge current. The Dis output of the U2400B provides the reference voltage for IC3.

 


Fig. 7. Circuit for measuring the battery voltage with respect to earth.



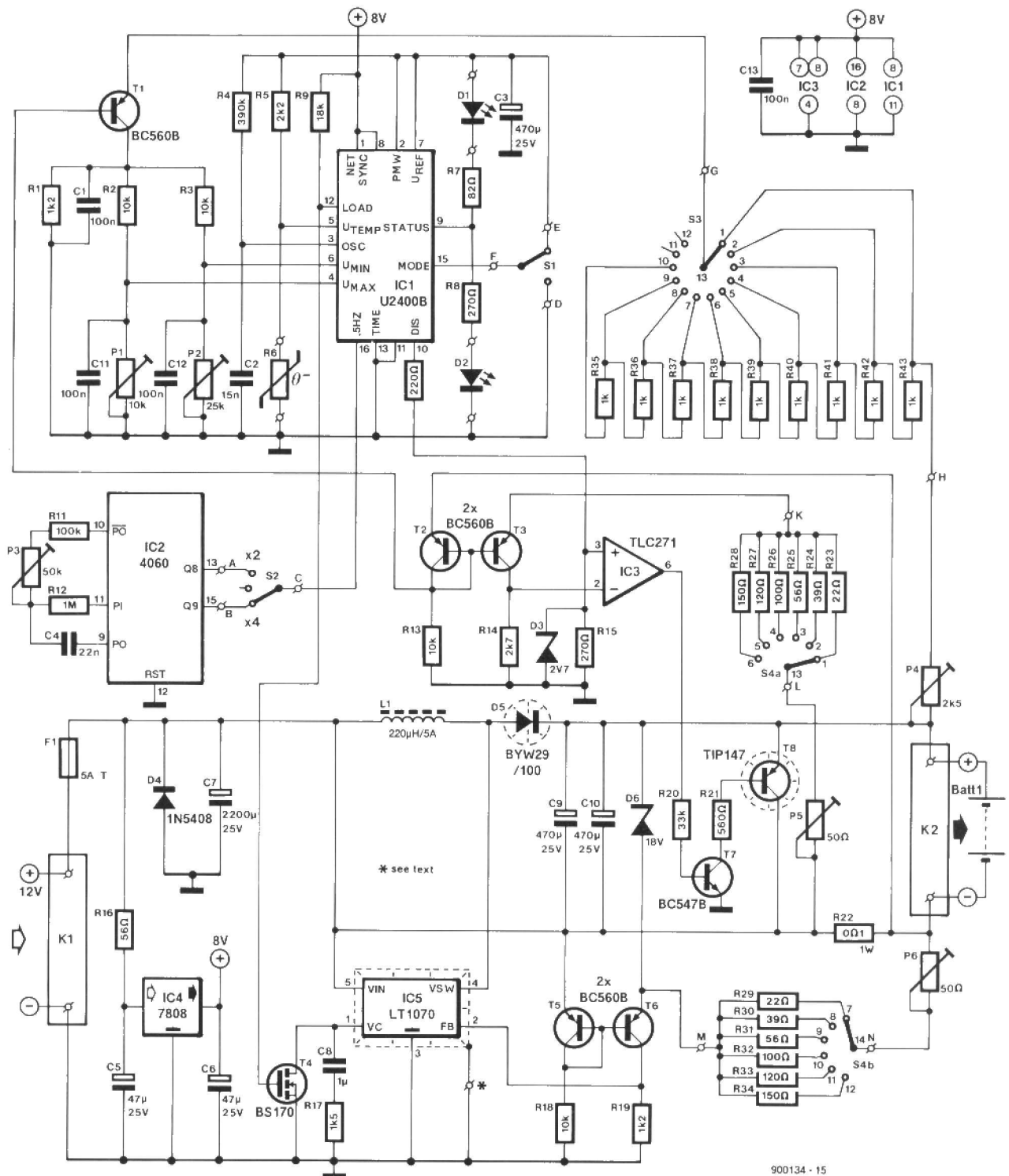


Fig. 8. Complete circuit diagram of the Ni-Cd battery charger.

tical. It is, of course, essential that switch  $S_3$  is set to the correct number of connected batteries (maximum 10).

Switch  $S_1$  selects the mode to be used when one or two errors are detected during the charging process—see Table 1.

When  $S_2$  is in its centre position, the processor uses the standard time setting (of charging) of 1 hour. Its pin 13 is then connected to earth. If this meets all your requirements, the external clock generator consisting of the 4060 (IC<sub>2</sub>),  $R_{11}$ ,  $R_{12}$ ,  $C_4$ ,

$P_3$ , and  $S_2$ , may be omitted.

Otherwise,  $R_{11}$ ,  $R_{12}$ ,  $P_3$ , and  $C_4$ , set the frequency of the oscillator in the 4060 at 100–150 Hz. The divider on board the 4060 provides the required signal frequencies at outputs  $Q_8$  and  $Q_9$ . The charging times of 2 and 4 hours respectively associated with these frequencies enable U7 and U11 size batteries to be charged in accordance with manufacturers' specifications.

Preset  $P_3$  enables the correct setting of 2-hour (position A) and 4-hour (position B)

charging periods. Should that not be possible, the value of  $C_4$  may be increased (longer periods) or reduced (shorter periods). If a standard time of 30 minutes is wanted instead of 1 hour ( $S_2$  in centre position), disconnect pin 13 of the U2400B from earth.

If  $C_4$  is replaced by a 10 nF type, periods of 30 minutes ( $S_2$  in centre position), 1 hour ( $S_2$  in position A), and 2 hours ( $S_2$  in position B), may be selected.

For trickle charging the normal charging circuit is used, but the on-off ratio is ar-

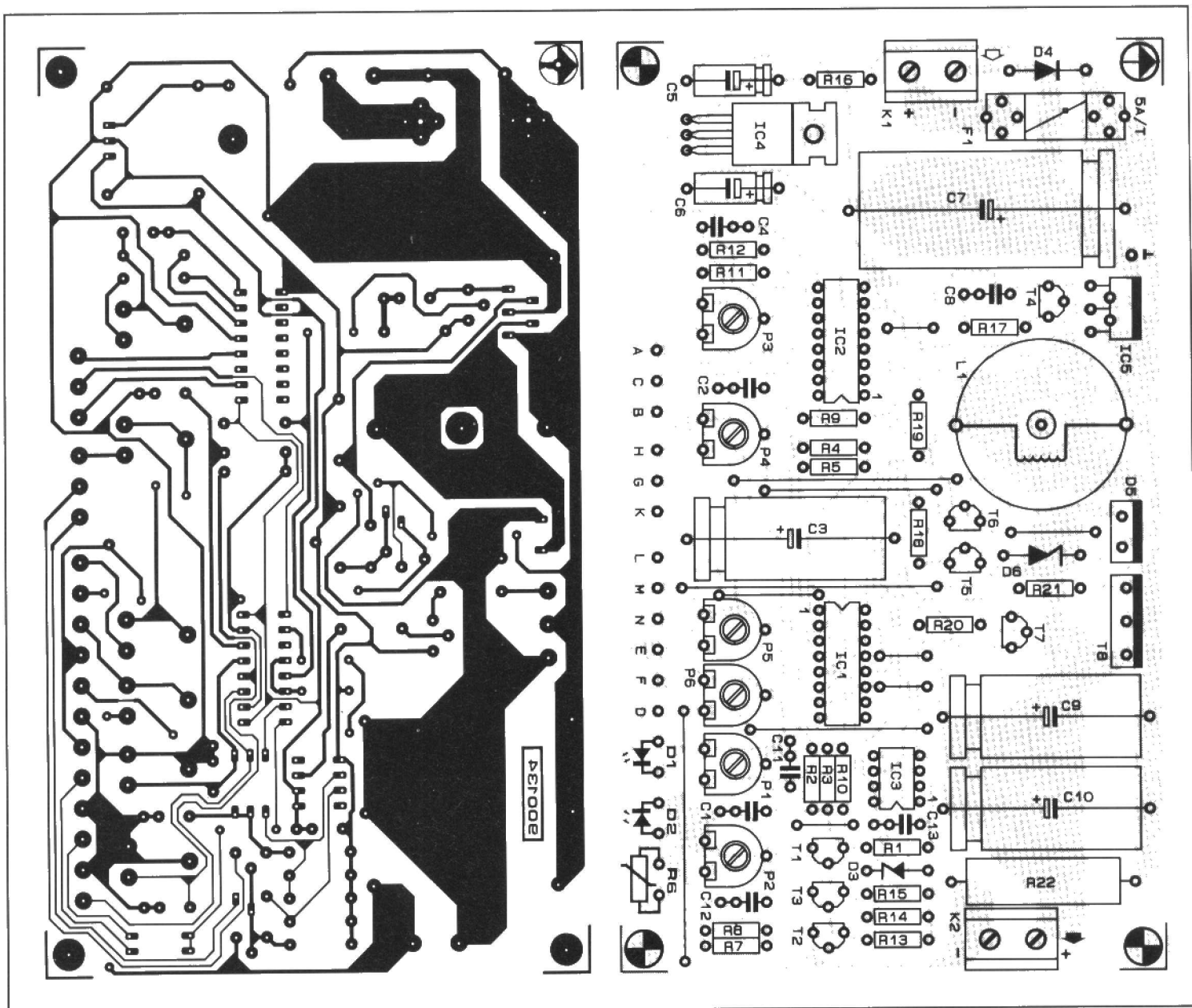


Fig. 9. Component layout and mirror image of track layout of the printed-circuit board for the Ni-Cd battery charger.

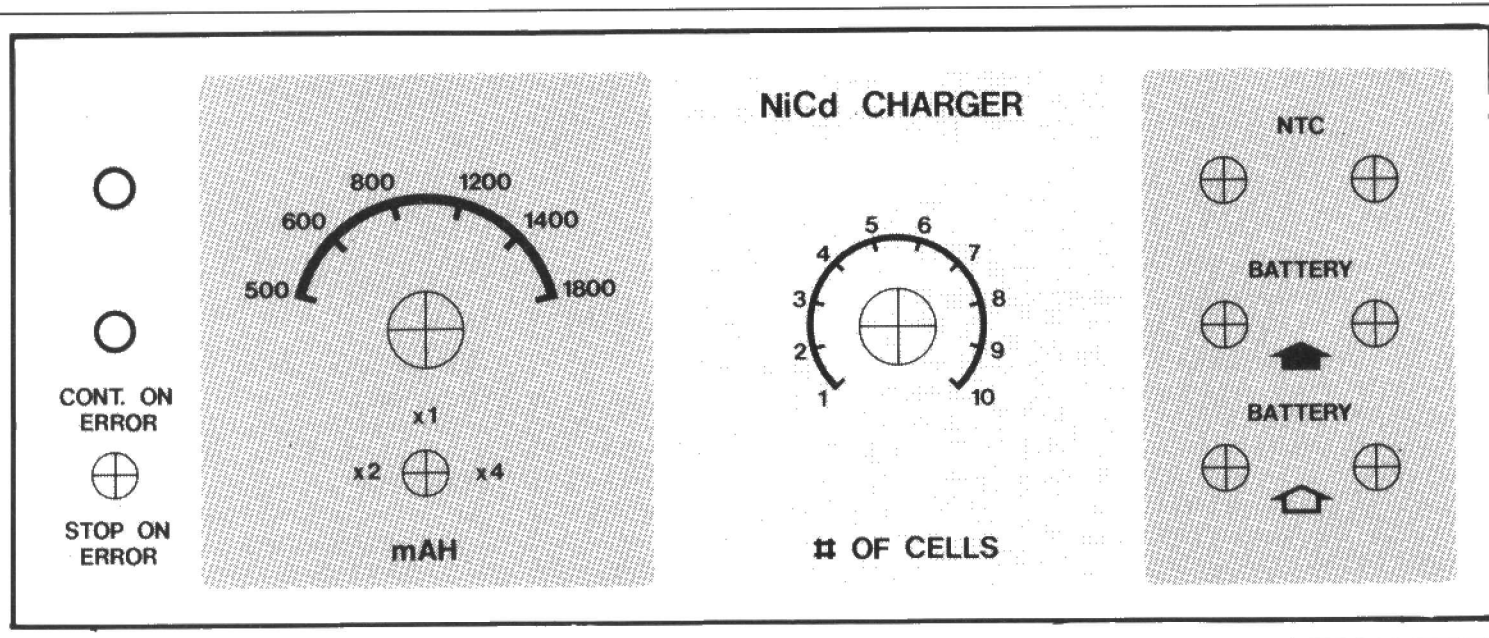


Fig. 10. A front panel foil for the battery charger (196x77 mm) is available through our Readers' Services.



ranged at 1:179, which reduces the average charging current of 1800 mA to 10 mA.

The level of the discharge and charging currents is independent of the selected charging period and may be set to six fixed values with  $S_4$ . If it is required for a battery to be charged completely in 30 minutes, the charging current selected must have twice the value of the battery capacity. The charging current in mA corresponds to the capacities shown on the front panel—see Fig. 10. That is, in position 500 mAh, the charging current is 500 mA. Independent of this, the charging current may be doubled by shunting  $R_{22}$  with a second 0.1  $\Omega$ , 1 W, resistor. This may, however, be done only if the total consumption,  $I_{load} \times U_{load}$  does not exceed 25 W, otherwise the switched-mode power supply may become overloaded. Furthermore, the maximum current through the inductor, the fuse rating (max. 8 A), and the maximum discharge current (max. 10 A) must be observed.

## Construction

The battery charger is best constructed on the printed-circuit board shown in Fig. 9.

Pay good attention to the polarity of a number of components and make sure that firm solder connections are made where large currents are likely to flow.

The components that need cooling, i.e.,  $IC_5$ ,  $D_5$ , and  $T_8$ , are located at the edge of the board to enable them to be fitted direct to a suitable heat sink ( $\geq 3.2 \text{ K W}^{-1}$  at a consumption of  $\leq 25 \text{ W}$ ).

Make sure that the rear of the LT1070 is electrically bonded to the earth connection specially provided between the supply connections for  $C_7$  and  $IC_5$ .

All presets are conveniently grouped at one side of the board.

Resistors  $R_{23}$ – $R_{43}$  are not located on the board, but are soldered direct to the rotary switches. These switches are intended to be fitted to the front panel. Their sections that must be connected to the board are marked

G/H, K/L, and M/N.

The sockets for connecting the NTC resistor,  $R_6$ , the supply ( $K_1$ ) and the batteries ( $K_2$ ) are located at the right-hand side of the front panel.

## Calibration

There are quite a few calibrations to be carried out, but fortunately they are not very critical. In the first place, do not yet fit  $IC_1$ .

1. Set  $S_4$  to 500 (mA),  $S_3$  to 8 (batteries),  $S_2$  to its centre position, and all presets to the centre of their travel.
2. Connect a 12 V, 2 A supply to  $K_1$  (observe polarity!).
3. Connect an auxiliary supply of 8 V to  $K_2$  (observe polarity!).
4. Connect a multimeter between the  $\oplus$  pin of  $K_2$  and point G on the board, and adjust  $P_4$  until the measured voltage is *exactly* the same as that between the pins of  $K_2$ .
5. Set  $S_3$  to position 10 and adjust  $P_2$  until with an auxiliary voltage of 8–8.5 V on  $K_2$ , a voltage of 0.53 V is measured between junction  $P_2$ – $R_3$ – $C_{12}$  and earth. This ensures that all batteries are first discharged to an e.m.f. of 0.8–0.85 V.
6. Set  $S_3$  to position 10 and adjust  $P_1$  until with an auxiliary voltage of  $10 \times$  the maximum specified (by manufacturer) cell voltage on  $K_2$ , a potential of 0.53 V is measured between junction  $P_1$ – $R_2$ – $C_{11}$  and earth. The maximum cell voltage is normally about 1.65 V, but may vary from 1.55 V to 1.7 V.
7. The external clock is adjusted with the aid of  $P_3$  and this is best done on an oscilloscope. The frequency of the signal at pin 6 of  $IC_2$  must be 1 Hz. If you have no oscilloscope, use a logic tester with LED indication: the flashing of the LED may be compared with the second hand of a watch.
8. Remove the auxiliary voltage from  $K_2$ , switch off the supply voltage, and fit  $IC_1$  and  $R_6$ . In an emergency, a normal 1 k $\Omega$

resistor may be used for  $R_6$ .

9. Connect a partially discharged 500 mAh battery to  $K_2$ , set  $S_4$  to 500 and  $S_3$  to 1.
10. Reconnect the 12 V supply to  $K_1$ , whereupon the red LED will come on.
11. Connect a digital multimeter (set to 1–2 A d.c.) in series with the battery. About 2 seconds after the connection with the battery is made, the red LED goes out and discharging of the battery begins. Adjust  $P_5$  till the multimeter reads 500 mA.
12. After a little while, the battery will be discharged and charging will commence, indicated by the coming on of the green LED. The current through the multimeter will then change direction: adjust  $P_6$  until it has a value of 500 mA.
13. The battery charger is now ready for use.

## Finally

Before charging is begun, always set the various switches to the correct position. The charger can then be switched on and the batteries connected to it. When a different set of batteries or battery is connected to the charger, reset the processor by briefly switching off the supply. ■

PARTS LIST			
<b>Resistors:</b>		<b>Inductors:</b>	
R1, R19 = 1.2 k $\Omega$	R26, R32 = 100 $\Omega$	L1 = choke 200 $\mu\text{H}$ , 5 A	<b>IC5 = LT1070</b>
R2, R3, R13, R18 = 10 k $\Omega$	R27, R33 = 120 $\Omega$		
R4 = 390 k $\Omega$	R28, R34 = 150 $\Omega$	<b>Semiconductors:</b>	<b>Miscellaneous:</b>
R5 = 2.2 k $\Omega$	R35–R43 = 1 k $\Omega$	D1 = LED, red	S1 = miniature C/O switch
R6 = 1 k $\Omega$ NTC	P1 = 10 k $\Omega$ preset	D2 = LED, green	S2 = miniature C/O switch with centre position
R7 = 82 $\Omega$	P2 = 25 k $\Omega$ preset	D3 = zener, 2.7 V, 400 mW	S3 = rotary switch, 1 pole, 12 positions
R8, R15 = 270 $\Omega$	P3 = 50 k $\Omega$ preset	D4 = 1N5408	S4 = rotary switch, 2 poles, 6 positions
R9 = 18 k $\Omega$	P4 = 2.5 k $\Omega$ preset	D5 = BYW 29/100	F1 = fuse, 5 A, complete with holder
R10 = 200 $\Omega$	P5, P6 = 50 $\Omega$ preset	D6 = zener, 18 V, 400 mW	K1, K2 = 2-way terminal block
R11 = 100 k $\Omega$		T1, T2, T3, T5, T6 = BC560B	Heat sink, 100×38×15 mm
R12 = 1 M $\Omega$	<b>Capacitors:</b>	T4 = BS170	PCB 900134
R14 = 2.7 k $\Omega$	C1, C11, C12, C13 = 100 nF	T7 = BC547B	Front panel foil 900134-F
R16, R25, R31 = 56 $\Omega$	C2 = 15 nF	T8 = TIP147	
R17 = 1.5 k $\Omega$	C3, C9, C10 = 470 $\mu\text{F}$ , 25 V	IC1 = U2400B	
R20 = 33 k $\Omega$	C4 = 22 nF	IC2 = 4060	
R21 = 560 $\Omega$	C5, C6 = 47 $\mu\text{F}$ , 25 V	IC3 = TLC271	
R22 = 0.1 $\Omega$ , 1 W	C7 = 200 $\mu\text{F}$ , 25 V	IC4 = 7808	
R23, R29 = 22 $\Omega$	C8 = 1 $\mu\text{F}$		
R24, R30 = 39 $\Omega$			
			Estimated cost: £45–£55

# LOGIC ANALYSER - PART 4

by K. Nischalke and H.J. Schulz

**In this penultimate instalment of the article (which was delayed by circumstances beyond our control), the power supply and the interfaces for the IBM and Atari are discussed, and that completes the hardware for the logic analyser. In the final instalment, the necessary software will be introduced.**

**T**HE DESIGN of the power supply is not revolutionary and yet it is unconventional, because the analyser, owing to the number of fast logic circuits, consumes quite a lot of power. The circuit diagram of the power supply is given in Fig. 16.

So as to keep the supply relatively simple and compact, five low-power voltage regulators, instead of one heavy-duty type, are used: one for each board contained in the analyser. This design has the advantage that when a certain board is not used, its supply can also be omitted. Furthermore, the cooling becomes a lot easier.

The supply consists of two independent sections, of which the main one is based on transformer  $Tr_2$ , bridge rectifier  $D_2$ – $D_5$ , and voltage regulators  $IC_{65}$ – $IC_{69}$ . The section based on  $Tr_1$ , bridge rectifier  $D_6$ – $D_9$ , and regulators  $IC_{70}$  and  $IC_{71}$  is intended for probes that can cope with input voltages up to  $\pm 12$  V. If such a probe is not envisaged, this section may simply be omitted.

Mains transformer  $Tr_2$  is rated at 5 A to handle the whole analyser. The rating can be reduced by 1 A for each RAM card that is omitted.

The five regulators are of the well-known 78xx type, but here rated at 2 A (S-type). This is because the current drain of the RAM cards is just about 1 A and it would be disturbing if the current limiting of the regulator would come into action regularly (low voltage).


The PCB for the supply is shown in Fig. 17. It has the same format as the bus board and the two may, therefore, if the enclosure allows, be fastened together with the aid of suitable spacers (track sides facing, of course). Such an arrangement would place the 5 V and 12 V connections of the boards close together.

## Atari interface

Communication between an Atari and the logic analyser is via the hard-disk slot emerging at the rear of the computer via a D-type connector.

The present interface is not strictly a special hard-disk interface, but a DMA interface to which a maximum of eight external apparatuses may be connected in parallel. Addressing the apparatuses separately prevents any conflict between them. This means also that the hard disk may remain connected.

The circuit diagram of the interface is

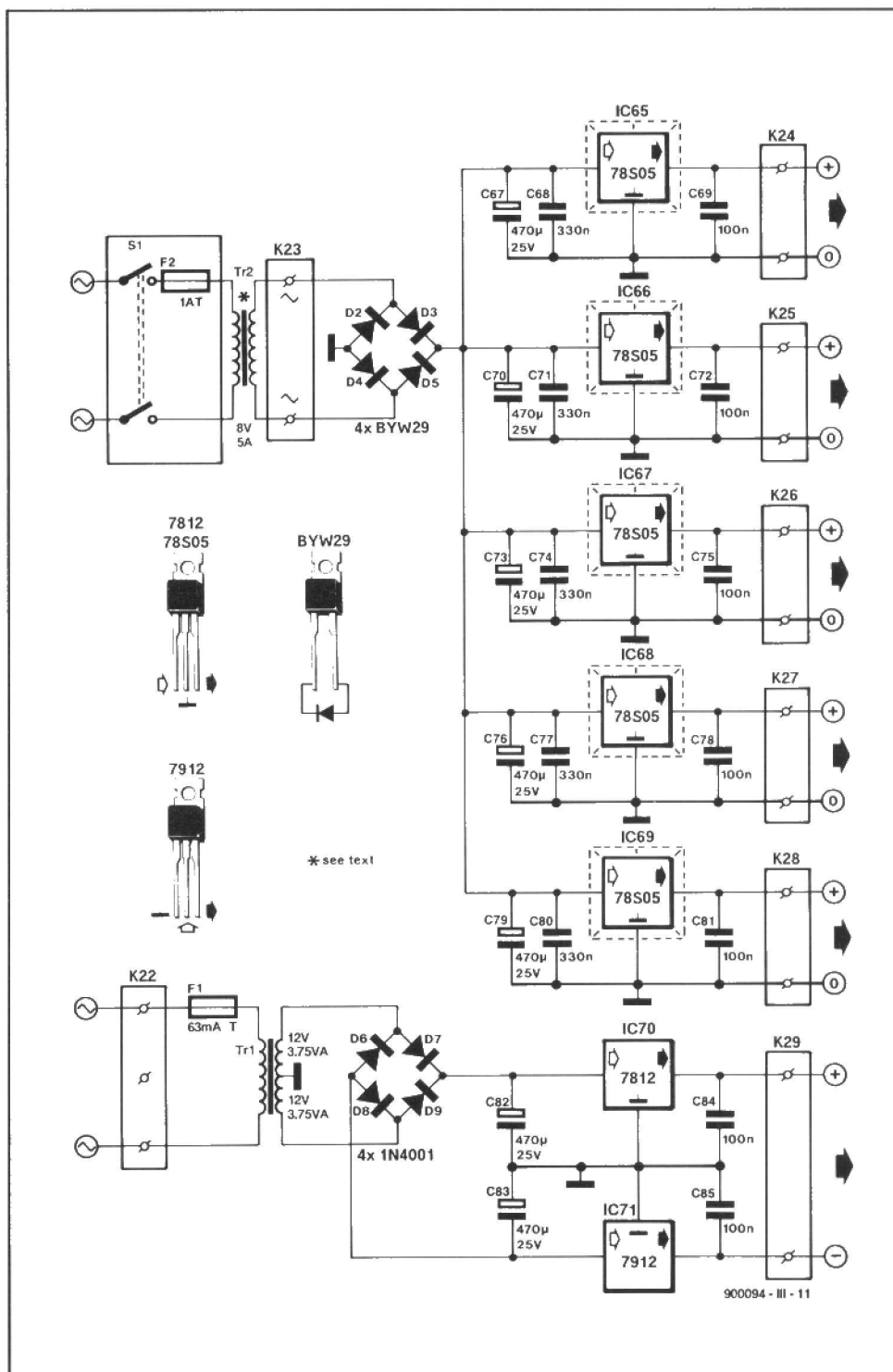

**Fig. 16. Circuit diagram of the power supply; the section based on  $Tr_1$  is for use only if probes that accommodate input voltages up to  $\pm 12$  V are to be used.**



Fig. 17. Photograph of the completed power supply board.


 


Fig. 18. The printed-circuit board for the power supply has the same dimensions as the busboard. It has no provision for Tr2.

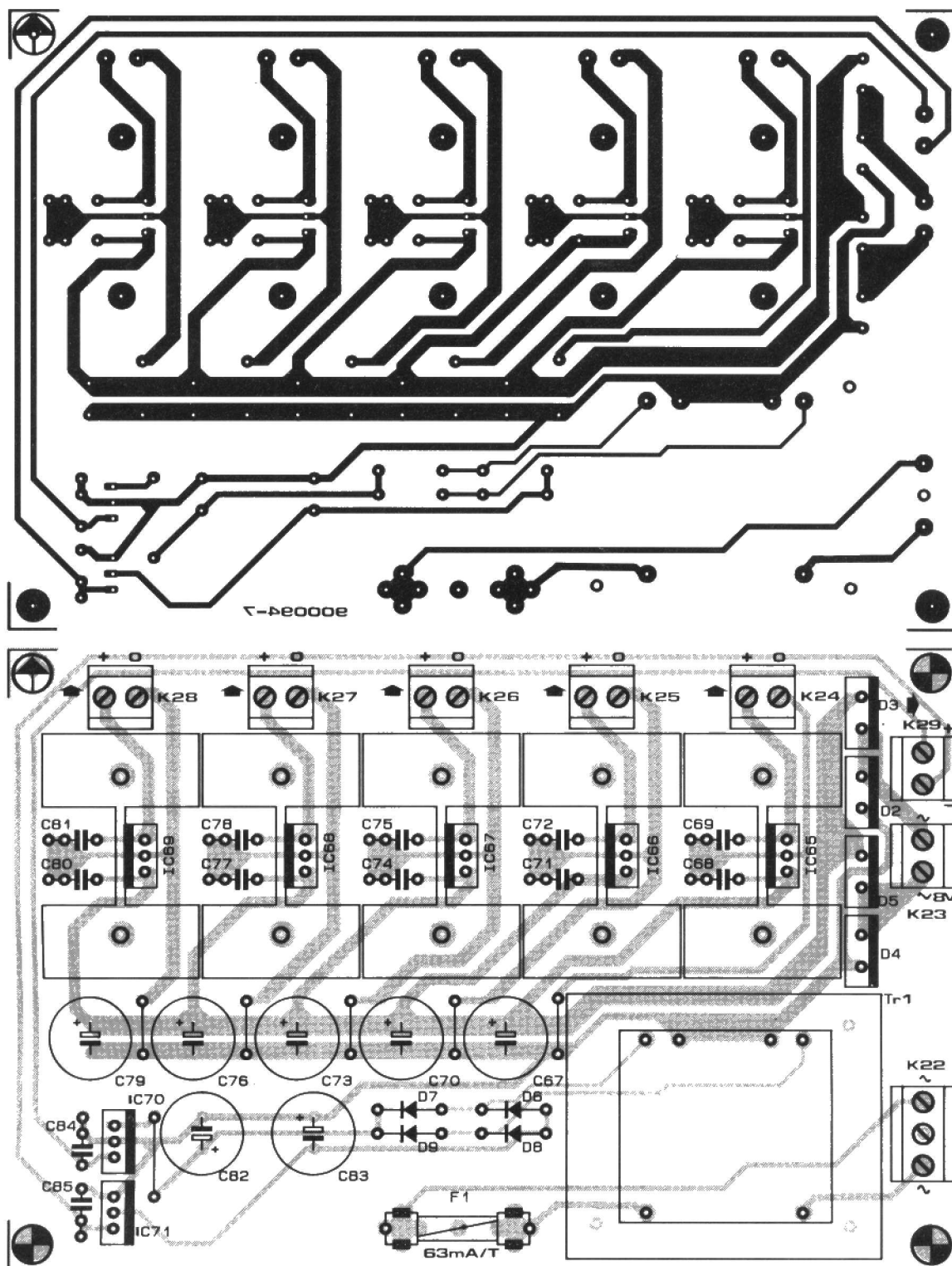



**Fig. 19. Circuit diagram of the interface for Atari computers.**



Fig. 20. The printed-circuit board for the Atari interface.



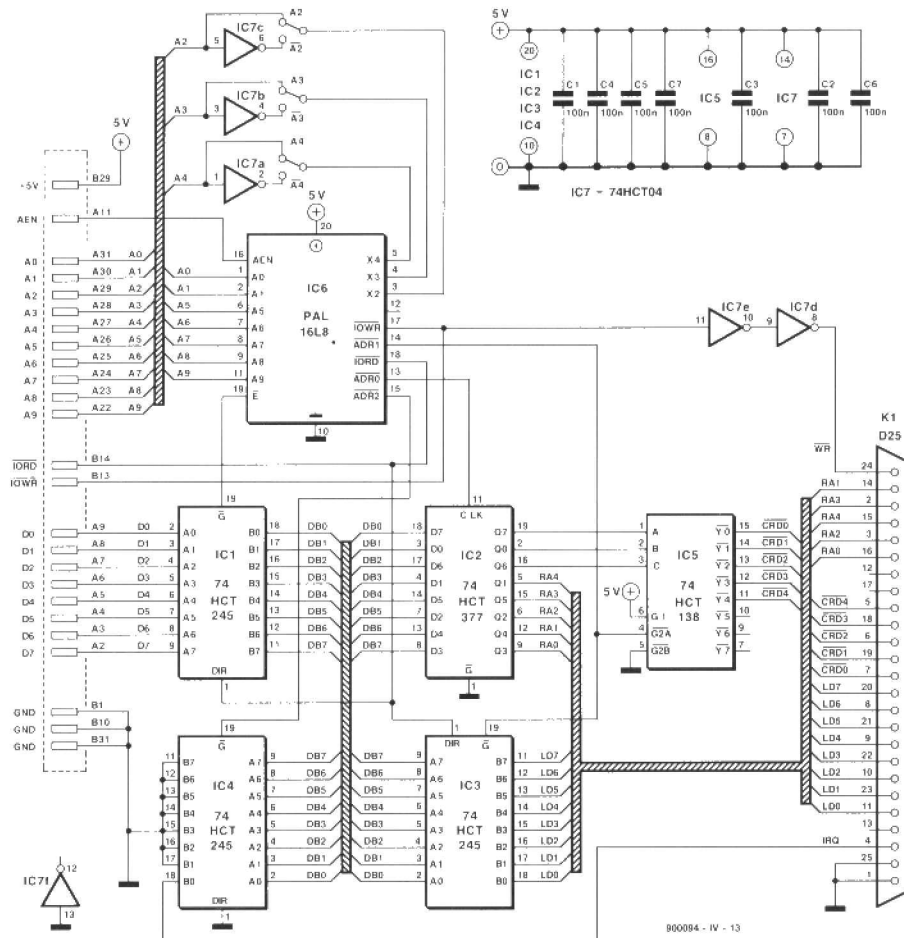


Fig. 21. Circuit diagram of the IBM interface.

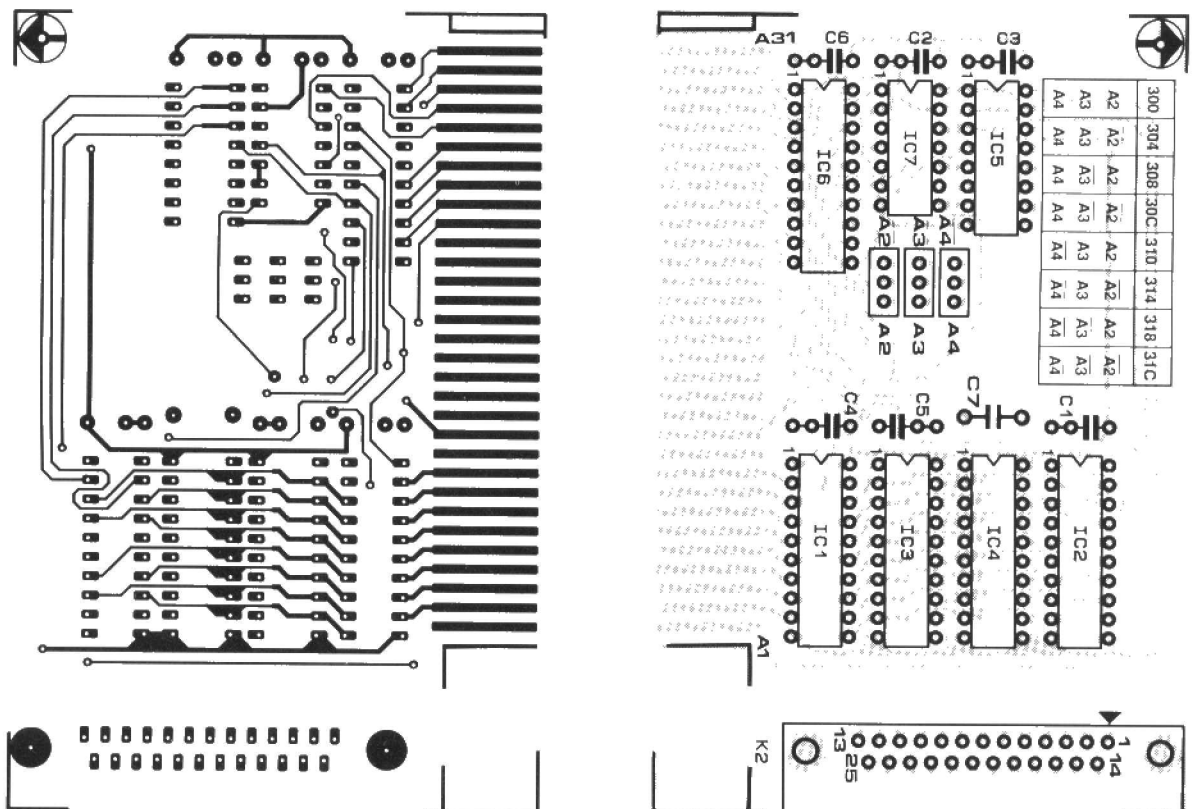


Fig. 22. The printed-circuit board for the IBM interface is designed as a slot-in card.

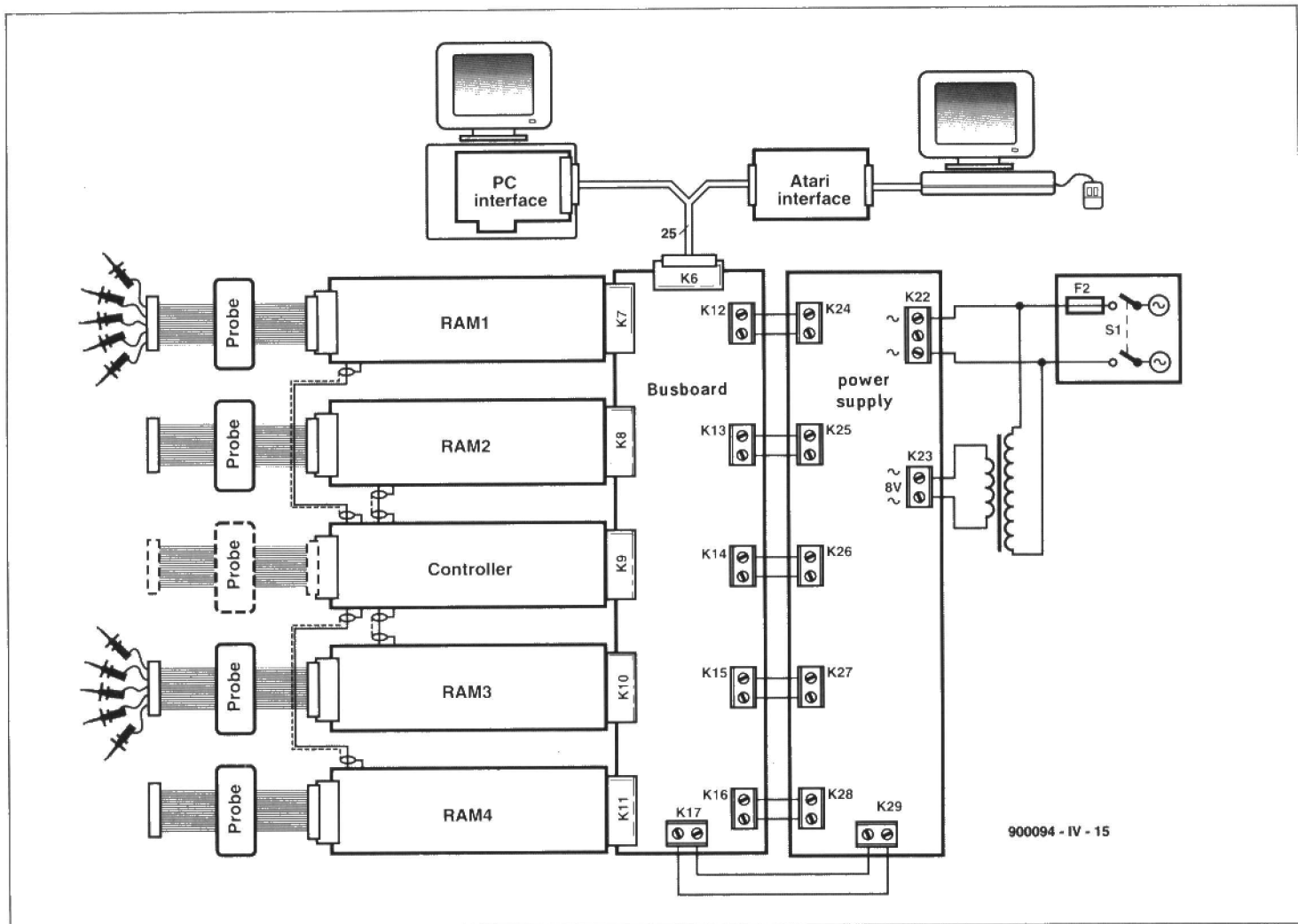


Fig. 23. Overview of the logic analyser and the wiring between the various boards.

 
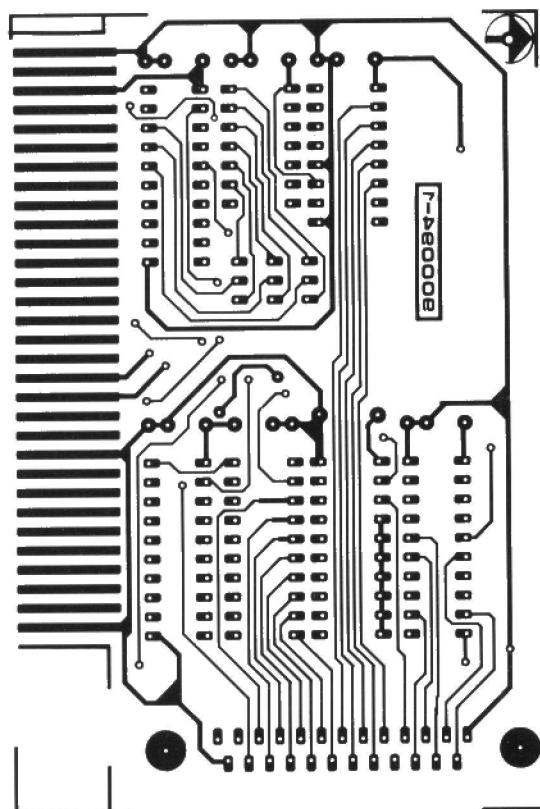



Fig. 24. The IBM interface print should be secured with a fixing plate as shown here.

ELEKTOR ELECTRONICS		
240V~	50 Hz	
No. 900094		
F1 = 125 mA		F2 = 2 AT


ELEKTOR ELECTRONICS		
110V~	60 Hz	
No. 900094		
F1 = 125 mA		F2 = 2 AT

Fig. 25. Suggested labels for the rear panel of the logic analyser.

 


Fig. 26. The front panel for the logic analyser is available through our Readers Services.

### Power supply

#### Capacitors:

C67, C70, C73, C76, C79, C82,  
C83 = 470  $\mu$ F, 25 V  
C68, C71, C74, C77, C80 = 330 nF  
C69, C72, C75, C78, C81, C84,  
C85 = 100 nF

#### Semiconductors:

D2–D5 = BYW29  
D6–D9 = 1N4001  
IC65–IC69 = 78S05  
IC70 = 7812  
IC71 = 7912

#### Miscellaneous:

K23–K29 = 2-way terminal block,  
5-cm centre  
K22 = 3-way terminal block, 5-cm centre  
Tr1 = mains transformer, 12 V, 3.75 VA  
Tr2 = mains transformer 8 V, 5 A  
S1 = mains on/off switch with  
integral fuse holder  
F1 = fuseholder and fuse, 63 mA,  
delayed action

## PARTS LISTS

F2 = fuse, 1 A, delayed action  
Five heat sinks for IC65–IC69  
PCB 900094-7

### Atari interface

#### Resistors:

R32–R34 = 2.2 k $\Omega$

#### Capacitors:

C64–C66 = 100 nF

#### Semiconductors:

IC59 = 74HCT574  
IC60 = 74HCT138  
IC61 = 74HCT00  
IC62 = 74HCT02  
IC63 = 74HCT03  
IC64 = 74HCT245

#### Miscellaneous:

K20 = 19-pole male D connector or  
20-way box header (see text)  
K21 = 25-pole female D connector for  
PCB mounting  
PCB 900094-6

### IBM interface

#### Capacitors:

C1–C7 = 100 nF

#### Semiconductors:

IC1, IC3, IC4 = 74HCT245  
IC2 = 74HCT377  
IC5 = 74HCT138  
IC6 = PAL16L8 (Order No. 5973)  
IC7 = 74HCT04

#### Miscellaneous:

K1 = 25-pole female D connector for  
PCB mounting  
Fixing plate (see Fig. 22)  
PCB 900094-1

shown in Fig. 19. The DMA interface can access two addresses in the circuit via line A1. The control register, IC<sub>59</sub>, is at one of these addresses (A1 = 0). The address of the apparatus must be written in the three most significant bits of this register in order to actuate the analyser.

The logic analyser has address 4; whether that is stored in the control register is checked by gates IC<sub>61c</sub> and IC<sub>62c</sub>.

The output signal of IC<sub>61c</sub> enables or disables the various inputs and outputs of the interface.

The remaining bits of the control register

are used to address the various registers in the analyser proper: Q0 and Q1 provide the two address lines for the register, while Q2–Q4 control address decoder IC<sub>60</sub>, which generates the five card-select signals.

When the interface is actuated by the four highest bits of the control register, data may be sent to and from the logic analyser via bidirectional buffer IC<sub>64</sub>. The buffer is addressed when A1 is high. The direction of the data transport is determined by the read/write> line.

The single-step signal is produced by IC<sub>63c</sub> and IC<sub>63d</sub> from the strobe signal for the data

bus and the WR> signal.

### Atari interface board

The board for the Atari interface has been designed as a sort of adapter plug (see Fig. 20 and 27) that can be inserted at the rear of the computer. The PCB-type 19-way male D connector for this is, however, not easily available in many locations. There is, therefore, the possibility to use a box header (which is much more readily available) in the K20 position. Starting at pin 1, the wires in the cable



 


Fig. 27. Photograph of completed Atari interface board.

 


Fig. 28. Photograph of completed IBM interface board.

are soldered or crimped as follows: 1 to 1; 2 to 11; 3 to 2; 4 to 12; 5 to 3; and so on; only pin 20 of the box header is not used.

No such difficulties are envisaged with K<sub>21</sub>. The cable between the interface and the logic analyser may be a standard computer accessory: 25-way with male and female connectors. It should, however, not be longer than one metre.

## IBM interface

The interface for IBM XT and AT computers consists of not much more than a number of digital inputs and outputs—see Fig. 21. The data bus for the computer is buffered by IC<sub>1</sub>. This is not necessary for the address lines of the computer, since most lines are connected to only one input. There are, nevertheless, three address lines that, depending on the position of the jumpers near IC<sub>6</sub>, are loaded with up to two inputs. Circuit IC<sub>6</sub> is the address decoder of the interface.

The basic address of the card may be arranged in steps of four addresses from 300<sub>hex</sub> to 31C<sub>hex</sub> with the aid of jumpers and inverters in lines A2–A4.

Four addresses emanate from the address decoder (a PAL): an enable signal for the

data bus buffer (E<>) and three select signals for controlling the three individual addresses on the interface card: ADR0–ADR2.

The address register is found at basic address +0. The address with which a card and a register are addressed on that card is written in the address register.

The data register is found at basic address +1, via which data are written to, or read from, the logic analyser. Simultaneous with the reading or writing, card select decoder IC<sub>5</sub> is enabled via the ADR1 line to ensure that the cards of the analyser are connected to the bus only when this really necessary.

The IRQ signal from the analyser enters via basic address +2 on the interface card. This is processed as data, and not as an interrupt.

## IBM interface board

The dimensions of the PCB for the IBM interface are determined solely by those of the two connectors—see Fig. 22 and 28. Since the electronics do not need much space, it has been possible to include a table on the board that indicates what jumpers are required to place a certain basic address for the card.

To prevent the card being pulled from the slot by the connecting cable, it is essential

that the board is provided with a fixing plate with which it can be fastened securely on to the computer. Such a plate can be made as shown in Fig. 24.

For the connection between the interface and the computer the same sort of cable as for the Atari may be used.

## Overview


An overview of the logic analyser and all that may go with it is shown in Fig. 23.

The control card is always connected to the centre connector of the bus board to ensure that when several RAM cards are used, the connections between these cards and the control card remain as short as feasible.

Before the RAM cards are built in, a 10 kΩ resistor must be soldered at the track side between pins 11 and 16 of IC<sub>29</sub>. This resistor suppresses any reflections that may occur at that end of the clock line to the shift registers.

There is not much wiring in the analyser because most connections are contained on the bus board. What wiring there is comes mainly from the power supply.

 10K RES ABOVE SOLDER BE  
330Ω FROM JUMP (A2) 1991  
P99



# VIDEO A-D/D-A CONVERTER

## PART 2: A 30-MHz VIDEO ADC/DAC DEVELOPMENT BOARD

Following last month's introduction into the basic operation of the two main integrated circuits in the design, the TDA8708 and the TDA8702, this second and last instalment focuses on the more practical side of things. Are you triggered? Here is a high-speed video A-D/D-A converter board aimed at helping you on the way with your own video experiments.

**P. Godon (Philips Components, Paris)**

*Continued from the May 1991 issue*

The block diagram of the development board, Fig. 8, shows the two converter ICs surrounded by quite a few sockets, switches and connectors. The switches, K1 through K9, are actually jumpers that allow different modes of operation to be selected. The BNC sockets, K10 through K17, are the analogue

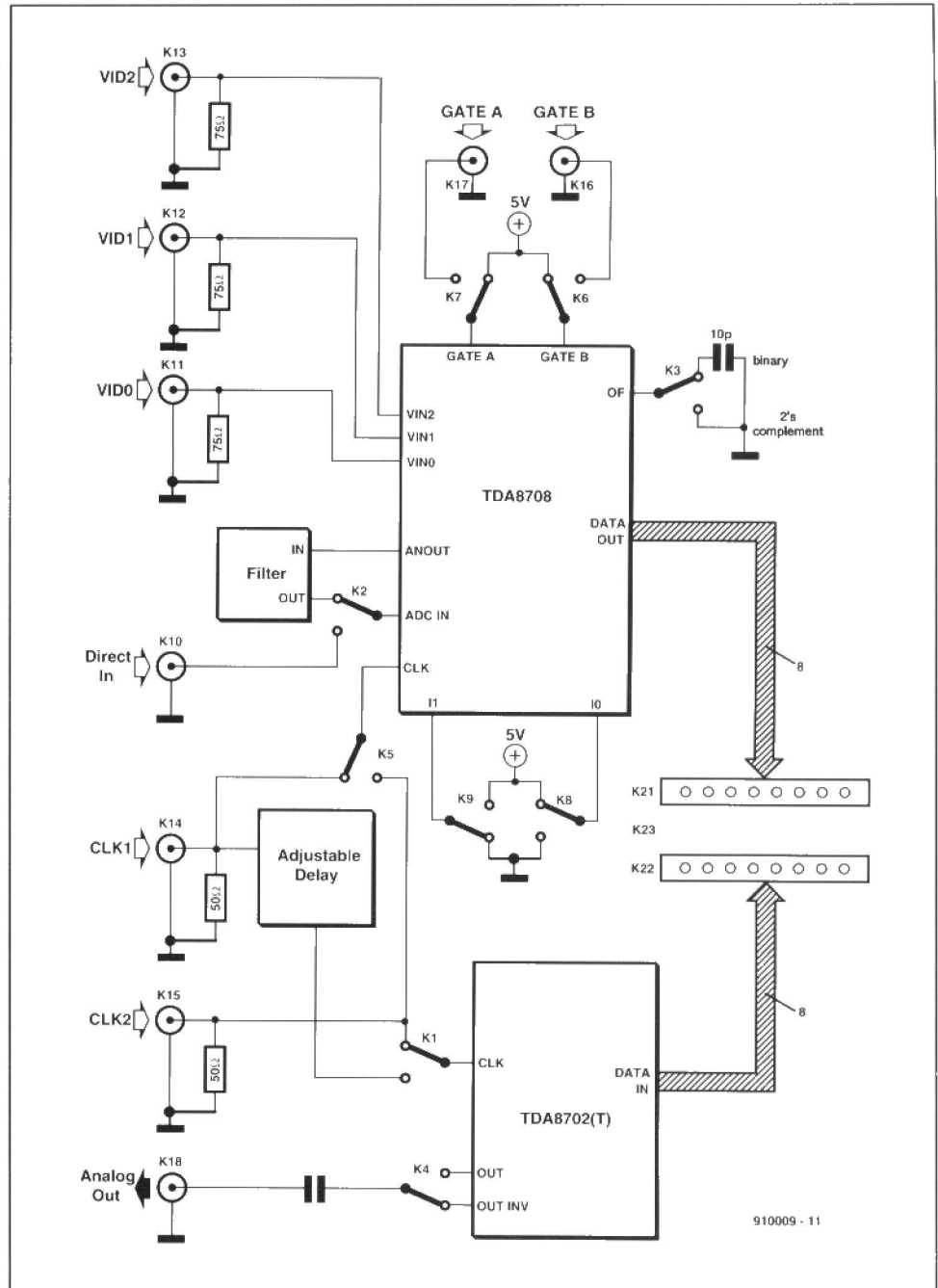


Fig. 8. Block diagram of the video processor card. Most of the switches shown here are wire jumpers to select different modes of operation.

**Table 8. Connector overview**

Connector	Type	Function	Connector	Type	Function
K1	jumper	Clock 2 / delayed Clock 1	K13	BNC socket	ADC input 2
K2	jumper	Video input / direct input	K14	BNC socket	Clock input 1
K3	jumper	ADC output: binary or 2's complement	K15	BNC socket	Clock input 2
K4	jumper	DAC output: true or inverted	K16	BNC socket	Mode gate B
K5	jumper	Clock 1 / Clock 2	K17	BNC socket	Mode gate A
K6	jumper	Gate B active / disabled (+5 V)	K18	BNC socket	DAC analogue output
K7	jumper	Gate A active / disabled (+5 V)	K19	PCB pin	Clock delay
K8	jumper	Video input selection: Bit 0=H / Bit 0=L	K20	PCB header	Supply voltages
K9	jumper	Video input selection: Bit 1=L / Bit 0=H	K21	PCB header	ADC output
K10	BNC socket	ADC direct input	K22	PCB header	DAC input
K11	BNC socket	ADC input 0	K23	32-way DIN	combined ADC output and DAC input
K12	BNC socket	ADC input 1			

video inputs and the digital control inputs. The analogue output signal of the DAC is available on socket K18. The board is linked to a computer or microprocessor system via connectors K21 and K22, or K23. All digital inputs and outputs of the board are TTL compatible.

The development board is connected to analogue and digital 5-V power supplies via K20. Two separate power supplies are required to ensure the best possible decoupling of the analogue and digital sections.

The 'adjustable delay' block is formed by an integrated circuit that has not been discussed last month. This IC, a Type 1505-5B from Data Delay Devices, contains a stepped delay line. The signal applied to the CLK1 input of the board, K14, can be delayed in steps of 1 ns to a maximum of 5 ns. The delay line has a d.c. resistance of  $0.7\ \Omega$  and an impedance of about  $100\ \Omega$ .

Finally, the resistors shown in the block diagram ensure that video sources are terminated in  $75\ \Omega$ , and the clock inputs in  $50\ \Omega$ .

## The development circuit

The circuit diagram of the video A-D/D-A card is given in Fig. 10. As discussed last month, the TDA8708 stores the current analogue value at the first leading edge of the clock signal, after the 1.5-V threshold is exceeded. You will also recall that the digital equivalent of the analogue value appears at the output after a delay,  $T_d$ , of 8 to 20 ns. At the next trailing edge of the clock signal, the DAC copies the digital information, and supplies the corresponding analogue value after the conversion delay,  $t_d$ , of 3 ns. Hence, the video input signal is subject to a total delay,  $T_v$ , of

$$T_v = T_d + 1/2f + t_d$$

At relatively high clock frequencies, say, 30 MHz, it may happen that the minimum required delay time between the A-to-D and D-to-A conversions is not available. The DAC requires that the input data remain stable for at least 0.3 ns. Since the time between the leading and the trailing edge is only 17 ns for a 30-MHz clock signal, it is readily seen that the DAC may have trouble loading stable data when the required delay,  $T_d$ , is yet to be subtracted. This potential problem is eliminated by the previously mentioned delay line, IC3, which delays the trailing edge of the clock 1 to 6 ns, depending on the selected 'tap' (jumper K19). This compensation ensures the correct operation of the conversion processes when relatively high clock speeds are used. The diagram in Fig. 9 shows the combined timing of the ADC and the DAC, along with the data setup times and associated delays.

## Construction

In view of the speed of the signals involved, the video A-D/D-A circuit is best built on a printed-circuit board of the design shown in Fig. 11. The board is double-sided, but not


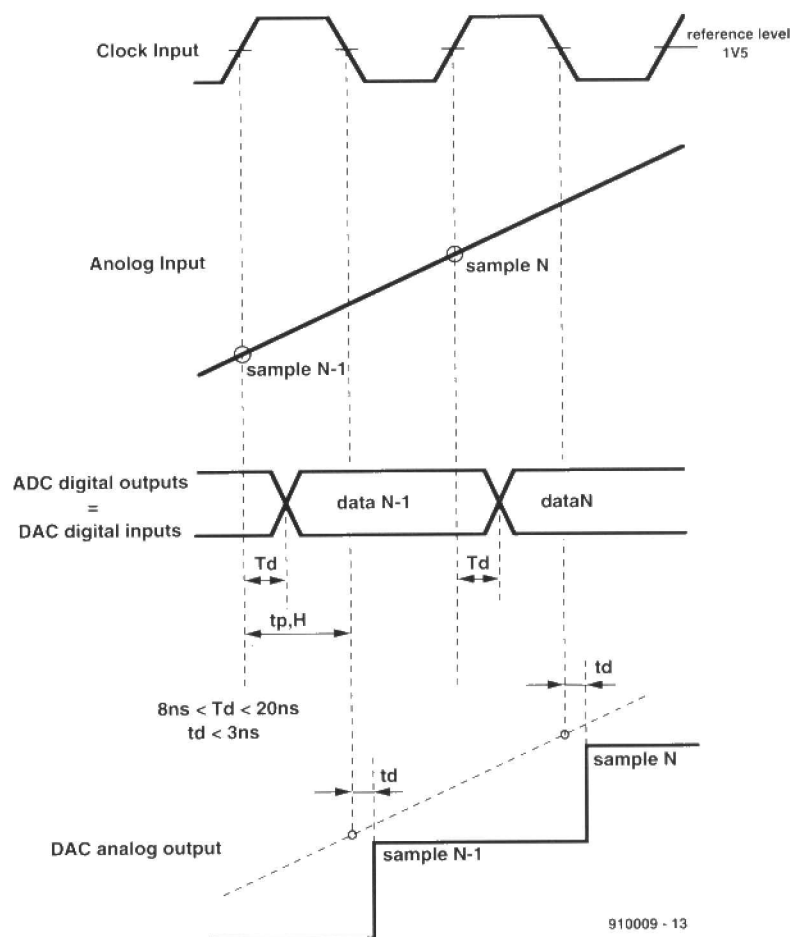


Fig. 9. Overview of conversion timing and data setup times for the ADC and the DAC.

 

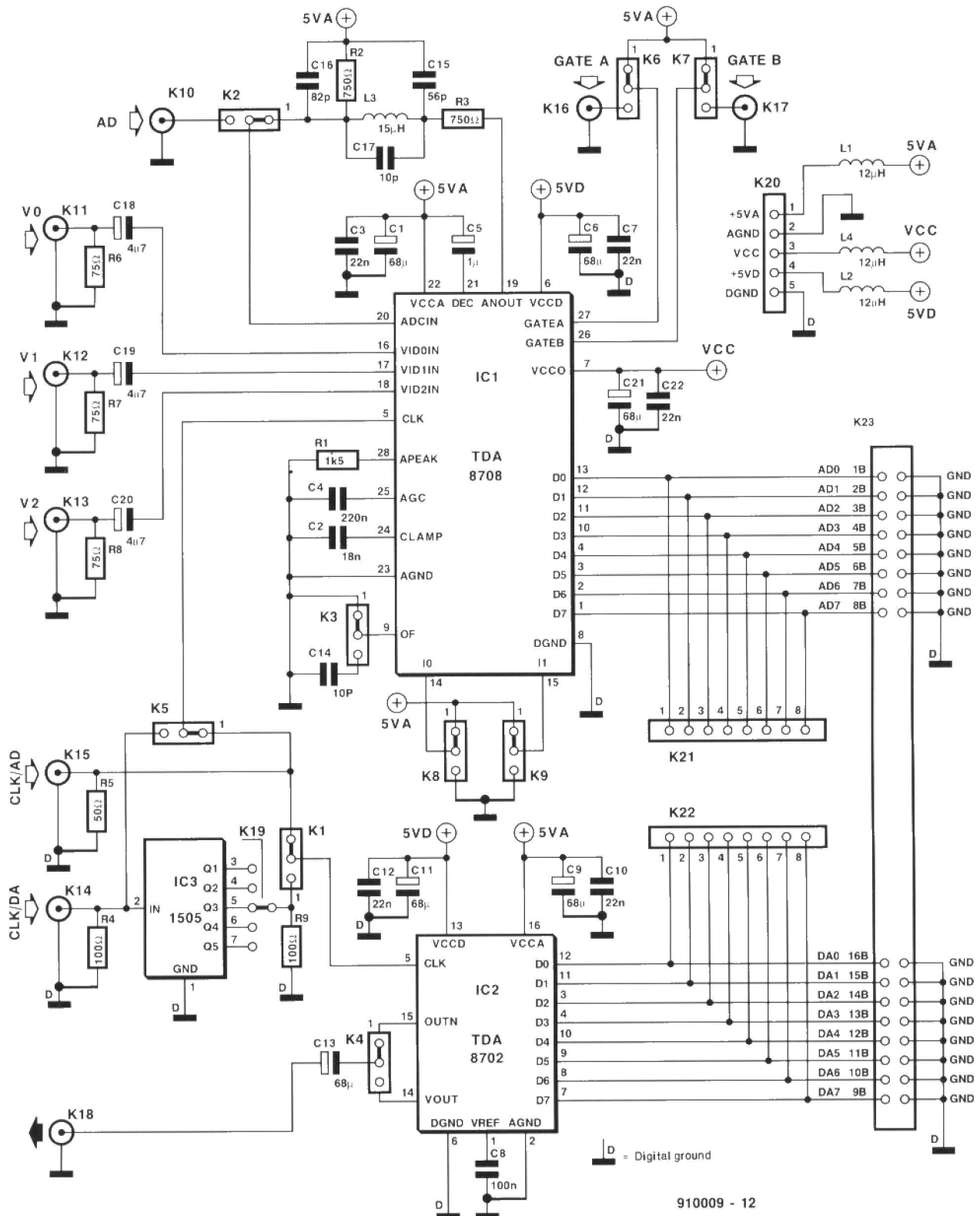


Fig. 10. Circuit diagram of the ADC/DAC converter card. You have the digitized video signal available at a resolution of 8 bits between connectors K21 and K22. A separate connector, K23, allows the card to be connected to a computer bus.

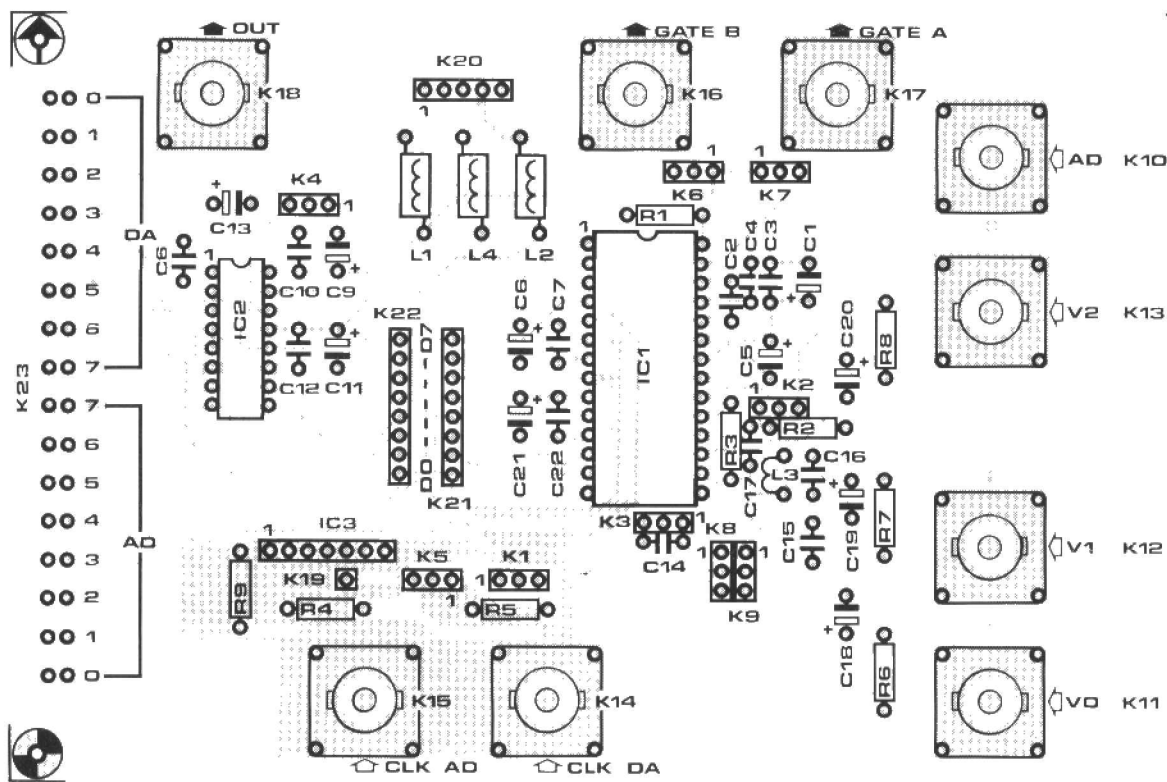


Fig. 11a. Component mounting plan of the double-sided printed circuit board. Note that the board is designed for PCB-mount BNC sockets.

through-plated. Its design allows BNC sockets to be fitted without coaxial cables, which reduces parasitic capacitance to a minimum.

Most of the PCB headers and jumper blocks on the board can be made from single-row and double-row pin headers, which are available in strips of 36 and 72 pins with a spacing of 0.1 inch. Headers K21 and K22, for instance, are 8-pin pieces cut from a larger strip.

Connector K23 is a 32-way angled type to DIN41612. It allows the digital data inputs of the DAC, and the digital outputs of the ADC, to be connected to a microprocessor system bus. For a straight link between the ADC and the DAC, interconnect the corresponding pins on K21 and K22. Finally, note that although an SMA (surface-mount assembly) version of the development board is shown in Fig. 11, all components on the board shown in Fig. 10 have standard sizes. ■

## COMPONENTS LIST

### Resistors:

1	1kΩ	R1
2	750Ω	R2;R3
2	100Ω	R4;R9
4	75Ω	R5 - R8

### Capacitors:

6	68μF 6V3	C21
1	18nF	C2
5	22nF	C3;C7;C10; C12;C22
1	220nF	C4
1	1μF 10V	C5
1	100nF	C8
2	10pF	C14;C17
1	56pF	C15
1	82pF	C16
3	4μF7 10V	C18;C19;C20

### Inductors:

3	12μH	L1;L2;L4
1	15μH	L3

### Miscellaneous:

1	TDA8708	IC1
1	TDA8702	IC2
1	1505-5b *	IC3

### Miscellaneous:

9	3-pin PCB header	K1 - K9
9	PCB-mount BNC socket	K10 - K18
1	solder pin	K19
1	5-pin PCB header	K20
2	8-pin PCB header	K21;K22
1	32-way angled connector to DIN41612	K23

0.1-inch jumpers as required

\* UK distributor: BFI Ibexsa Electronics • Burnt Ash Road • Quarrywood Estate • Aylesford • Kent ME20 7NA. Tel. (0622) 882467, Fax (0622) 882469.

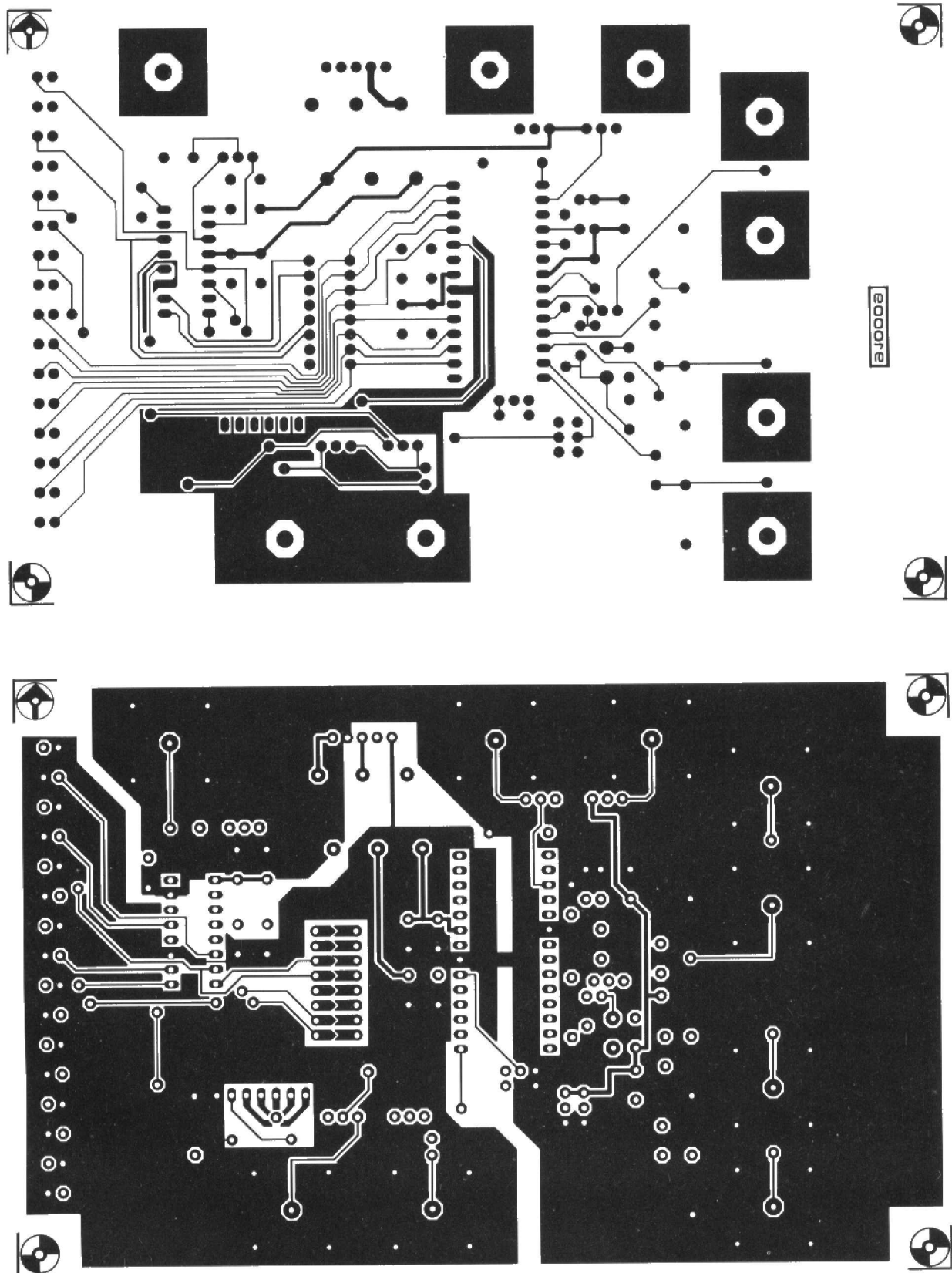


Fig. 11b. Solder side (above) and component side (below) of the PCB for the video ADC/DAC card.



# DIGITAL PHASE METER

**FRONT COVER  
PROJECT**

by R. Lucassen

Phase meters are rare instruments, even in the laboratory or workshop of audio and hi-fi engineers and enthusiasts. Perhaps that is because until the advent of reliable digital techniques it was fairly difficult to design an accurate direct-reading phase meter. In one commercial catalogue published in the 1970s, a phase meter is advertised as having "an accuracy of about 3 degrees from 10 Hz to 30 kHz". Clearly, for modern audio equipment, that is no longer acceptable. Another reason may be that a phase meter is a fairly specialized instrument: many engineers and technicians measure phase shift with the aid of Lissajous figures (which do not give very accurate results either). The phase meter presented in this article is accurate to within  $0.5^\circ$  over the frequency range 10 Hz to 20 kHz.

THE PHASE shift between two electrical signals is of great importance in most branches of electronic engineering, but more particularly in audio engineering. In all circuits containing capacitors or inductors or both, frequency-dependent phase shifts will occur and these will affect the wanted operation of many circuits. There are, of course, circuits, such as filters, where phase shift is one of the design parameters.

The basic design of the phase meter may be gleaned from the block diagram in Fig. 1. Note, however, that, for the sake of simplicity, an analogue meter has been substituted for the LED display with which the instrument is actually equipped.

The analogue signals presented to the display section are digitized before they are processed. Since alternating signals are involved, this is quite simple: the positive part of the signals is converted to a logic low (0) and the negative part to a logic high (1). The timing diagram in Fig. 2 shows the analogue input signals (A and B) together with their digitized variants (A' and B'). The use of the digitized signals as the clock for a bistable (US: flip-flop) ensures a perfectly symmetrical (i.e., duty factor is 50%) digital output signal at a frequency equal to half that of the input signal. This guarantees that differing lengths of positive and negative half periods, noise and other spurious signals have no effect on the accuracy of the measurements.

The time difference between the leading edges of the signals emanating from the bistables is a measure of the phase shift between the two input signals. The output of the XOR gate is high during this time difference. The ratio of the width of the logic high signal at the output of the XOR gate to that of the output signal of bistable FF<sub>1</sub> gives the phase shift, which only has to be converted into degrees.

The width of the output pulse of the XOR

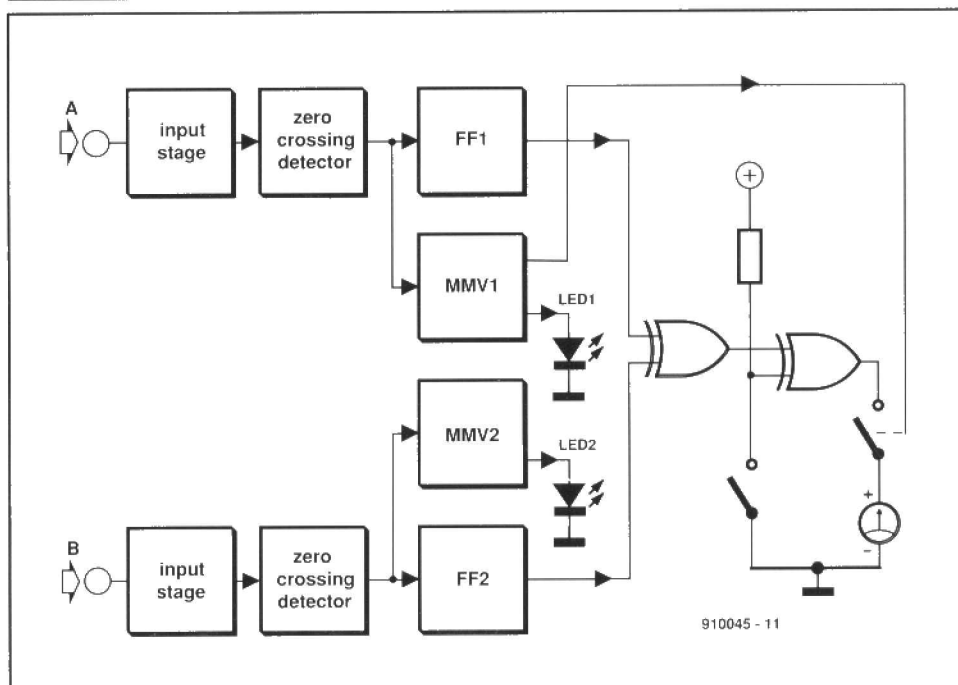
 


Fig. 1. Block diagram of the digital phase meter.

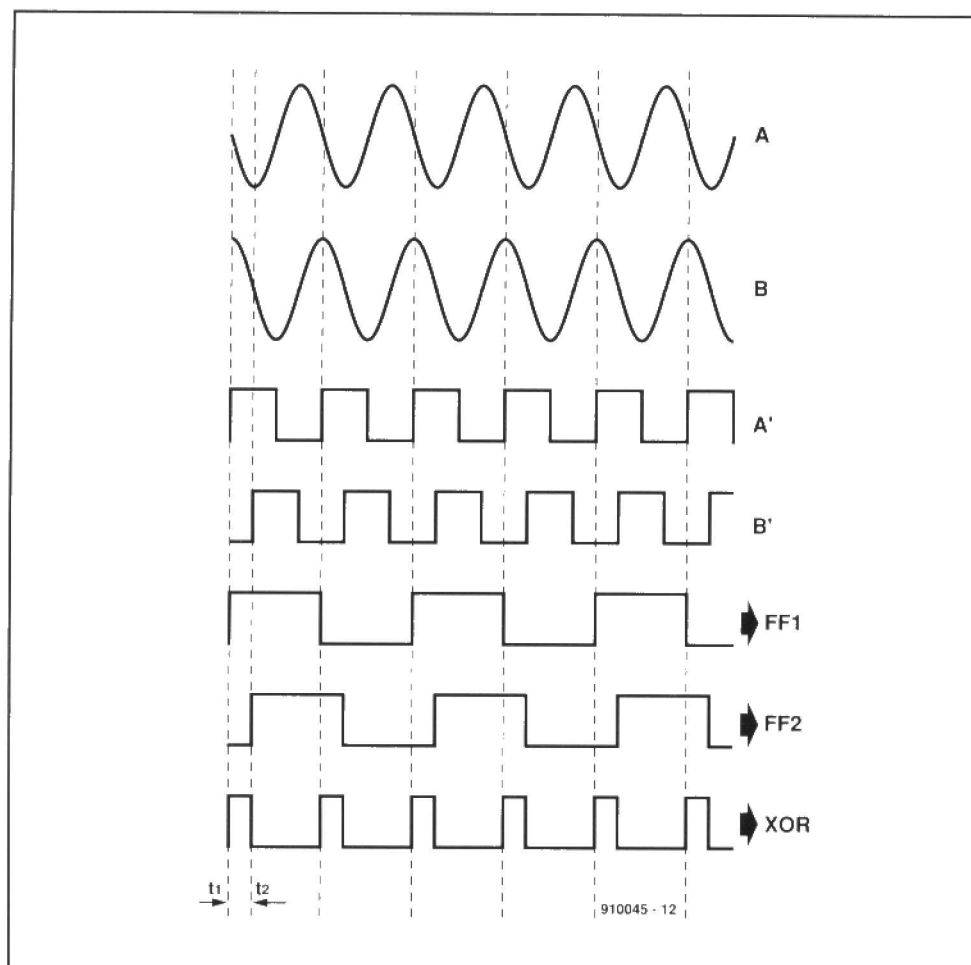


Fig. 2. Timing diagram of the analogue-to-digital conversion section.

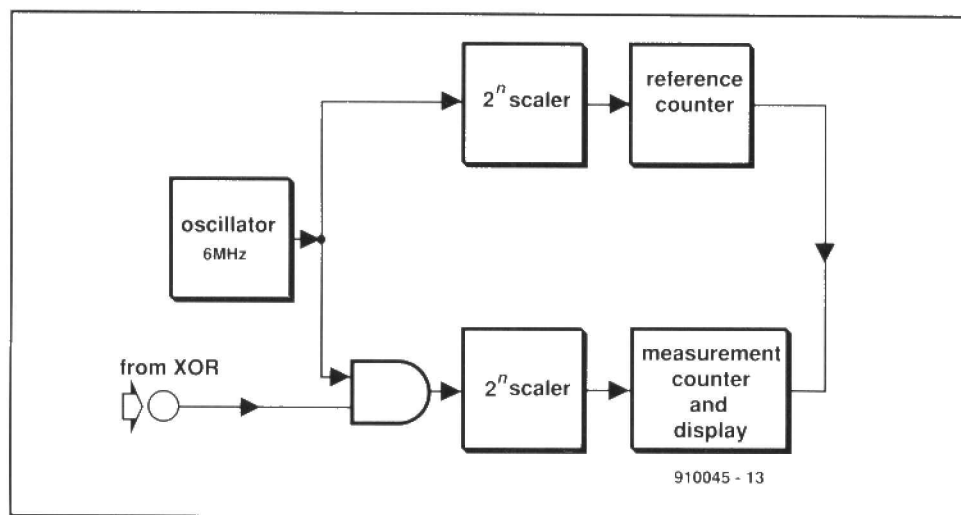


Fig. 3. Block diagram of the digital measuring section.

gate indicates at all times by how much signal B lags signal A. Therefore, the pulse represents a phase difference of 0–360°. Since it may also be of interest to measure the lag of signal A with respect to signal B, there is a second XOR gate whose output may be inverted.

Monostables MMV<sub>1</sub> and MMV<sub>2</sub> indicate by LEDs that usable signals, that is, signals whose phase difference is to be measured, exist at the associated inputs. Furthermore, the output of MMV<sub>1</sub> is used to actuate the meter. If only signal A is present, the meter

must remain stably in the centre position. If it does not, the input signal is unstable and, therefore, not suitable for measurements.

Since the width of the pulse at the output of the XOR gate is a measure of the phase shift, it would seem that a simple analogue interface in the form of an integrator would be sufficient for driving a moving meter. That would, however, present certain difficulties, such as a strong dependence on temperature and the fact that to obtain a stable meter deflection a high integration constant would

have to be used. That would make the measurement very slow and the instrument inconvenient to use.

A digital meter was therefore chosen, which can accurately indicate any phase difference between 0° and 360° with a resolution of 1°. The diagram in Fig. 3 shows how this meter operates.

A central clock frequency of 6 MHz is used, which is applied continually to one branch of the circuit, and to the other branch only when the output of the XOR gate of the phase comparator is high. In both branches, the clock pulses are divided by 2<sup>n</sup> before they are applied to the respective stage. Factor *n* is set manually. Note that since division takes place after the AND gate, this gate has no effect on the accuracy of the measurement.

As soon as the content of the reference counter has reached a value of 3,600, one output of the counter goes high to indicate that the measurement is complete and that 3,600/2<sup>n</sup> pulses were processed during it.

At the instant the reference counter has counted 3,600 pulses, the display memory is prompted to take over the contents of the reference counter. The display will then show the number of counted pulses, that is, when the phase shift is 0°, no pulses were counted; if the phase shift is 360°, 3,600 pulses were counted. The last digit of the number of pulses is omitted to make the display read the number of degrees.

Note that the accuracy of the measurement depends on the ratio of the measuring time to the frequency of the reference signal. The measurand is therefore sampled at a frequency of 6 MHz. Even at the highest signal frequency of 20 kHz, the error introduced by this is negligible.

Furthermore, the design of the instrument arranges that counting always starts at the beginning of a period. Therefore, it is never known how much of the last period is measured and steps must consequently be taken to ensure that the last period has negligible influence on the measurement. This is done by taking many periods per measurement. For instance, a measurement over 10 periods has a possible error of 10%, whereas over 200 periods the error would be only 0.5%. Because of that, the instrument contains a counter (in the error indicating circuit) that monitors over how many signal periods a measurement was spread.

## Circuit description

The instrument is constructed on three printed-circuit boards; the associated circuits are shown in Fig. 4, 5 and 6.

Figure 4 is the circuit diagram for the motherboard. The power supply is a straightforward, conventional type with a bridge rectifier and two integrated regulators.


The buffered and possibly attenuated (–20dB) signal is applied to terminals A and B. Input A is used as the reference signal and for actuating the metering section.

The incoming analogue signal is converted into a digital signal in IC<sub>12</sub> (channel A) and IC<sub>14</sub> (channel B). The offset of these



ELEKTOR ELECTRONICS JUNE 1991



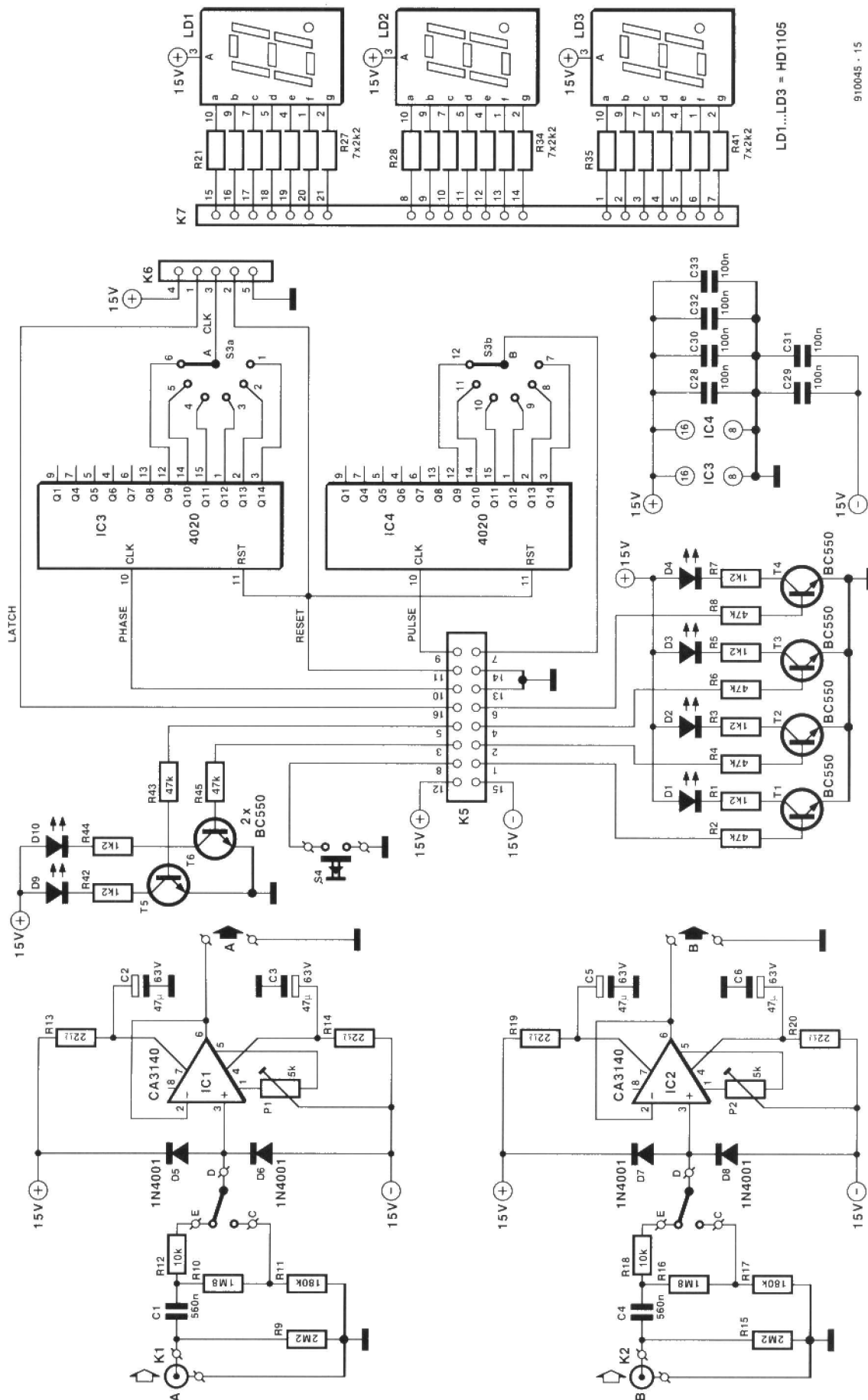

910045 · 15

Fig. 5. Diagram of the circuit containing the displays, input stages, and selector switches.

opamps is compensated by presets P<sub>3</sub> and P<sub>4</sub> respectively. Bistables IC<sub>13a</sub> and IC<sub>13b</sub> split the digitized signal into a symmetrical signal (duty factor = 50%) that is suitable for measurements.

Monostables IC<sub>15a</sub> and IC<sub>15b</sub> actuate the LEDs (D<sub>9</sub> and D<sub>10</sub>) on the front panel to indicate that suitable signals are input. At the same time, IC<sub>15b</sub> enables the reference counter via its Q output.

The outputs of IC<sub>13a</sub> and IC<sub>13b</sub> are combined via XOR gate IC<sub>16a</sub>. Another XOR gate, IC<sub>16b</sub>, and switch S<sub>4</sub> on the front panel make it possible to invert the phase difference as discussed before.

Finally, IC<sub>17a</sub> combines the output of the phase comparator with the clock frequency (6 MHz). When the output of XOR gate IC<sub>16a</sub> is high, the clock is passed on and the measurement may be carried out.

The clock signal is generated by a crystal oscillator based on IC<sub>16c</sub> and buffered by IC<sub>16d</sub> before it is applied to the relevant stages.

At the end of the measurement, a reset cycle is started by IC<sub>24</sub>. As soon as this IC has counted 3,600 pulses, IC<sub>23b</sub> is set via IC<sub>25a</sub> and OR gate D<sub>11</sub>–D<sub>12</sub> and in its turn resets decade scaler IC<sub>26</sub>. This actuates the latch signal, whereupon the counter state is transferred to the display drivers (further discussed later on). Subsequently, IC<sub>22</sub> receives a clock pulse and stores data concerning any measurement error, after which IC<sub>21</sub> is reset. All relevant measurement data are then stored and the remainder of the circuit is reset via bistable IC<sub>23a</sub>. When the reset cycle is over, IC<sub>23a</sub> is returned to the relevant output state via AND gate IC<sub>17b</sub>. At the same time, IC<sub>24</sub> is reset by the clock pulse that appears at the Q<sub>9</sub> output of IC<sub>26</sub>. The circuit is then ready for the next measurement.

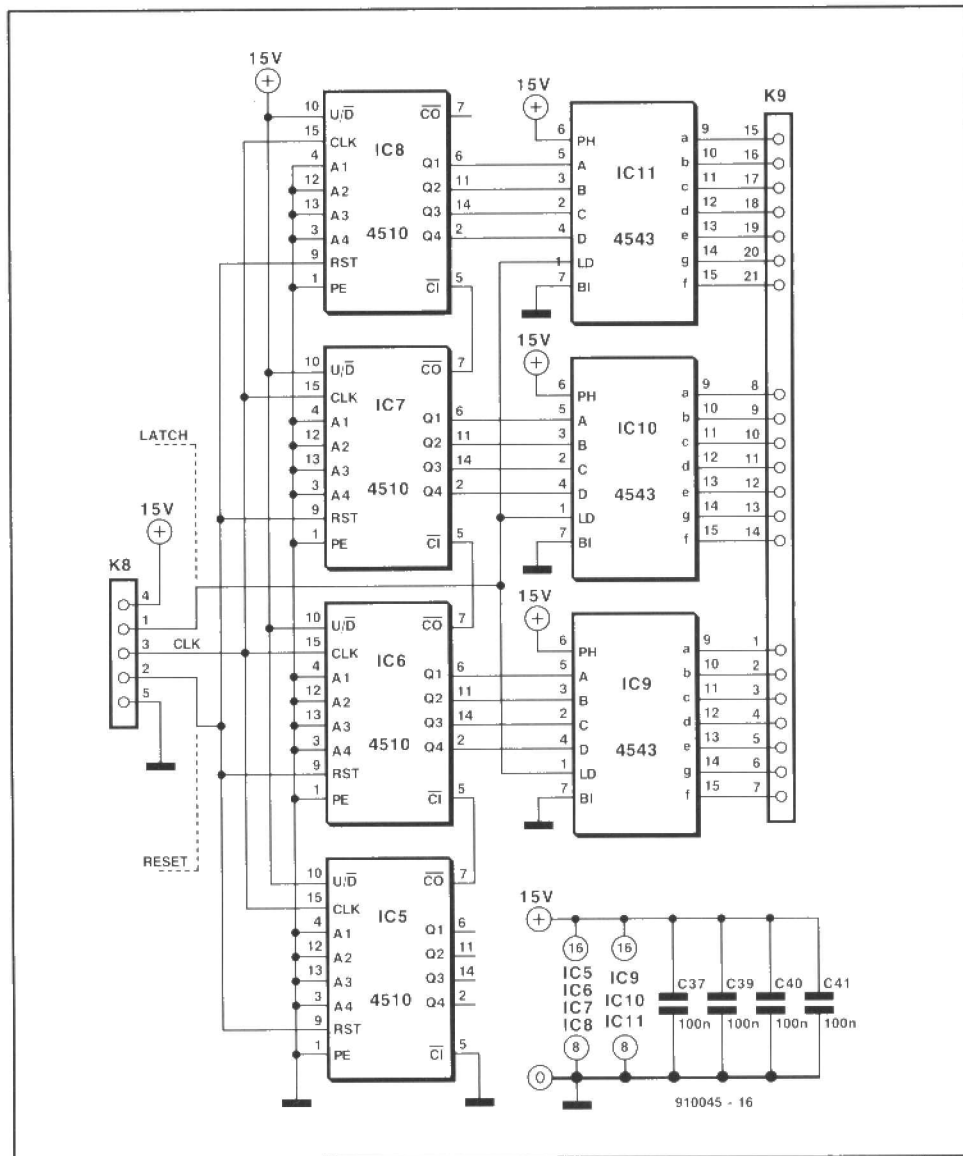


Fig. 6. Diagram of the logic circuits for the LED displays.

#### Resistors:

R1, R3, R5, R7, R42, R44 = 1.2 kΩ  
 R2, R4, R6, R8, R43, R45 = 47 kΩ  
 R9, R15, R59 = 2.2 MΩ  
 R10, R16 = 1.8 MΩ  
 R11, R17 = 180 kΩ  
 R12, R18, R46, R47, R51, R52 = 10 kΩ  
 R13, R14, R19, R20 = 22 Ω  
 R21–R41 = 2.2 kΩ  
 R48, R53 = 3.3 kΩ  
 R49, R55 = 4.7 MΩ  
 R50, R54 = 4.7 kΩ  
 R56, R58 = 1 MΩ  
 R57 = 100 kΩ  
 R60 = 22 kΩ  
 R61 = 1.8 kΩ  
 P1–P4 = 5 kΩ preset

#### Capacitors:

C1, C4 = 560 nF  
 C2, C3, C5, C6, C20, C21,  
 C26 = 4.7 μF, 63 V, radial  
 C7–C15, C17, C19, C28–C44 = 100 nF  
 C16, C18 = 820 pF  
 C22, C23 = 100 pF  
 C24 = 2200 μF, 40 V  
 C25 = 1000 μF, 40 V

## PARTS LIST

C27 = 47 μF, 40 V, radial

#### Semiconductors:

D1–D4, D9, D10, D13 = LED, 3 mm  
 D5–D8 = 1N4001  
 D11, D12 = 1N4148  
 B1 = B80C-1500  
 T1–T6 = BC550  
 IC1, IC2 = CA3140+  
 IC3, IC4 = 4020  
 IC5–IC8 = 4510  
 IC9–IC11 = 4543  
 IC12, IC14 = LM311DP  
 IC13, IC23 = 4027  
 IC15 = 4528  
 IC16 = 4070  
 IC17 = 4081  
 IC18, IC24 = 4040  
 IC19, IC20, IC25 = 4082  
 IC21 = 4043  
 IC22 = 4042  
 IC26 = 4017  
 IC27 = 7815  
 IC28 = 7915

#### Miscellaneous:

K1, K2 = BNC audio socket  
 K3 = 2-way terminal block,  
 7.5 mm centre  
 K4, K5 = 16-way box header  
 K10 = mains entry plug with integral  
 fuse holder  
 S1, S2 = single-pole change-over switch  
 S3 = rotary switch, 2 poles, 6 positions,  
 for PCB mounting  
 S4 = SPST switch  
 X1 = crystal, 6 MHz  
 LD1–LD3 = HD1105, common anode  
 Tr1 = mains transformer, 15 V, 18 VA  
 F1 = fuse, 100 mA, delayed-action  
 Mains on-off switch  
 Enclosure (ABS)  
 Knob for S3  
 Heat sinks for voltage regulators  
 PCB 910045-1  
 PCB 910045-2  
 PCB 910045-3  
 Front panel foil 910045-F

 


Fig. 7. Printed-circuit mother board.

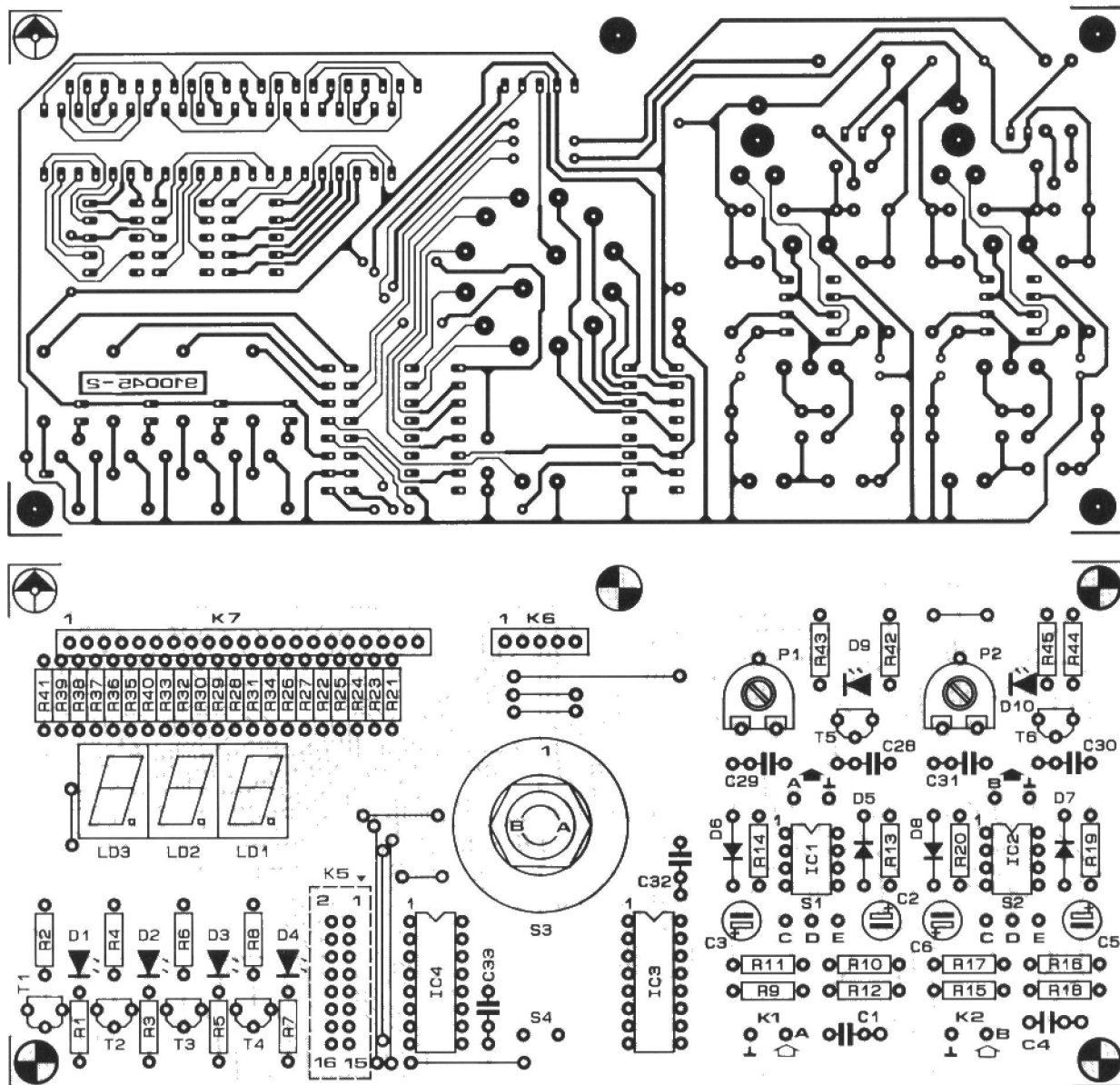



Fig. 8. Printed-circuit board for the displays, input stages, and selector switches.

Elektor Electronics	
110V~ 60 Hz	
No. 910045	
F = 100mAT	


Elektor Electronics	
240V~ 50 Hz	
No. 910045	
F = 100mAT	

Fig. 9. Suggested labels for the rear panel of the digital phase meter.

 


Fig. 10 Printed-circuit board for the logic circuits for the LED displays.



 


Fig. 11. The front panel foil for the digital phase meter is available through our Readers Services.

As mentioned before, the more periods are used, the more accurate the measurement. The counter in error detector IC<sub>18</sub> counts the number of periods between the onset of the measurement and the generated latch pulse. Four AND gates decode the result at 360, 180, 90 and 36 periods in one measurement cycle; these counts correspond to errors of 0.5°, 1°, 2°, and 5° respectively. Depending on the number of counted periods, one or more LEDs light; when they all light, the error is negligibly small.

Figure 5 shows the circuit of the displays, the indicators, the input stages and the stage for selecting the measurement duration. The indicator LEDs are driven by transistors; the control lines are connected to relevant points on the mother board via K<sub>5</sub>.

The input impedance is about 1 MΩ. Large input signals may be attenuated by 20 dB (S<sub>1</sub> and S<sub>2</sub>). All input signals are buffered by Type CA3140 opamps before they are applied to the comparator on the mother board. The inputs of these buffers are protected against overvoltage by diodes. Presets P<sub>1</sub> and P<sub>2</sub> serve to minimize the offset at the outputs of the opamps.

Circuits IC<sub>3</sub> and IC<sub>4</sub> are programmable 2<sup>n</sup> dividers. IC<sub>3</sub> counts the clock pulses passed by AND gate IC<sub>17a</sub>, that is, the pulses that indicate how long the output of XOR gate IC<sub>16b</sub> has been high. The number of these

pulses depends entirely on the phase shift between the two input signals. IC<sub>4</sub> is the reference counter that receives clock pulses continually.

The scaling factor is set with S<sub>3</sub>; it enables the user to select a measurement time that is most suitable for the frequency of the input signal. The error indicators on the display show whether the correct time has been selected.

Figure 6 shows the circuit contained on the third PCB: the seven ICs form the display counter and interface for the LED displays.

The clock pulses to be counted are applied to cascaded counters IC<sub>5</sub>–IC<sub>8</sub> via pin 3 of K<sub>8</sub>.

As soon as the latch signal is active, the counter state is stored in display drivers IC<sub>9</sub>–IC<sub>11</sub>. The displays, connected with this part of the circuit via K<sub>9</sub>, light to show the correct value measured.

The facilities of setting a pre-determined value and choosing up- or down-counting in the Type 4510 ICs are not used.

At the reset command at pin 2 of K<sub>8</sub> the counters are returned to zero and a new measurement cycle can be started. The previous measurement value is retained on the displays because the display drivers are not reset. The next measurement is thus carried out while the displays show the previous result.

## Construction

The three PCBs are shown in Fig. 7, 8, and 10. Their population is straightforward, but it is best to begin with boards 2 and 3. Note that the box header on board 2 must be soldered at the track side. Connectors K<sub>8</sub> and K<sub>9</sub> on board 3 may be replaced by right-angle print headers. As a bonus, such headers would ensure a firm mechanical link between boards 2 and 3. In any case, the boards are provided with holes to enable corner braces to be used for strong mechanical interlinking.

Mount the LED displays on board 2 about 1 cm (3/8 in) above the board with the aid of wire-

wrap IC sockets.

Connect switches S<sub>1</sub>, S<sub>2</sub>, and S<sub>4</sub>, to the board with short lengths of wire; fit S<sub>3</sub> directly to the board.

Cut the terminal wires of D<sub>1</sub>–D<sub>4</sub>, and D<sub>9</sub> and D<sub>10</sub> to about 2 cm (13/16 in); this will ensure that they will be located exactly behind the windows in the front panel.

Fit soldering pins at A and B and adjacent earth points at the track side of board 2.

The power-on indicator, D<sub>13</sub>, is best fitted to the front panel with the aid of an LED clip or superglue.

Fit board 2 on suitable spacers directly behind the front panel. Just prior to tightening the screws, connect the input sockets to the board via short wires. Next, screw the three toggle switches to the front panel.

Finally, mount board 3 at right angles to the track side of board 2 as shown in the photograph in Fig. 12.

Mount the mother board on the bottom plate of the enclosure, after which all necessary electrical connections to the other boards, the power-on LED, and on-off switch to mains entry plug can be made.

Finally, interlink points A and B, and the associated earthing points, on the mother board and board 2 by single screened audio cable.

## TECHNICAL DATA

Measuring range	10 Hz – 20 kHz
Reading	0–360°
Input sensitivity	6 mV peak
Max. input voltage	100 V peak
Attenuation	0 dB or 20 dB
Measurement time	0.3–10 s
Input impedance	1.1 MΩ
Measuring error	±0.5°

## Calibration and use

Calibration of the phase meter is confined to adjusting the four presets.

Short-circuit inputs A and B and adjust P<sub>1</sub> and P<sub>2</sub> for zero output of IC<sub>1</sub> and IC<sub>2</sub>.

Remove the short-circuit from the inputs and apply a sinusoidal a.f. signal at a level of about 10 mV to the inputs. Adjust P<sub>3</sub> until comparator IC<sub>12</sub> toggles exactly at the zero crossing point; check this on an oscilloscope.

Finally, adjust P<sub>4</sub> until the display shows a phase difference of 0°.

Start measuring a phase shift by applying the two signals to the inputs and turning S<sub>3</sub> (gate time) fully clockwise. Then turn the switch anti-clockwise step by step (when the accuracy increases). When the indicator marking a measuring error of 0.5° lights, the optimum position for this measurement has been reached. Since the measurement period increases all the time, it may take a few seconds at low frequencies before the indicator lights. That is, however, the price to be paid for accuracy at low signal frequencies. ■

 


Fig. 12. This photograph of the completed digital phase meter shows how the PCB of Fig. 9 is fitted to the PCB in Fig. 8.

# THE QTC LOOP ANTENNA

The quest for ever reduced sizes of efficient HF transmitting antennas is a compulsive exercise which one has great difficulty in dropping once 'bitten by the bug'. The antenna described here is a new challenge: a directional, compact, table-top loop design with proven excellent performance in the 80-m band.

Richard G. Marris, G2BZQ

THE lower the HF frequency, the more challenging the idea of being able to use a small antenna. For instance, in the 80 m (3.5 MHz) amateur band, a dipole antenna would be around 42 m long. Many do not have the real estate to accommodate such a dipole, apart from possible planning permission difficulties, and difficulties with leases or neighbours. For apartment dwellers an outside antenna is invariably impossible. For non-amateur applications there are various requirements for discrete and easily portable antennas. As a result, a compact table-top antenna as described here becomes most attractive for many applications.

## Small and efficient

Over the years, a number of small table-top HF antennas have been designed, built and air-tested. By far the best has been the spiral loop (Ref. 1) to cover the 3.5 to 3.8 MHz amateur band. This was a very simple 23-inch (approx. 59 cm) diameter octagonal experimental model which I used over the last year with a 7-watt CW transmitter.

It has been useful and fortunate during my experiments that there has been a regular daily 2-way schedule, between 05.00/05.30 a.m. on 3,560  $\pm$  5 kHz, with a friend in Stuttgart, Germany. He has entered into the spirit of these experiments, which have proved to be essential, though, of course, much longer distances have been achieved. His transmitter has a power output of about 100 watts feeding an outdoor dipole. As against this, I have been using a spiral loop on a table alongside my low-power transmitter. Strangely enough, looking back over the months, there has been little difference in signal strength reports either way.

 


Fig. 1. Electrical circuit of the loop antenna and the associated relative field strength

The tiny amount of textbook information (Ref. 2) available on spiral loops is concerned with direction finding (DF) and not transmission. It is stated that the reception advantages of the spiral loop over a standard box loop, with the turns side-by-side, are mainly greater sensitivity/gain, and a narrower directional polar diagram. Based on experience with the 23-inch diameter spiral loop, and seeking greater efficiency and transmission range, further experiments produced the much more sophisticated and efficient QTC spiral loop. Just in case you do not remember your Q-codes: QTC means "I have a message for you".

## The message

is that the new loop antenna has a 30-inch (approx. 76 cm) octagonal configuration,

which, although giving as much as 50% increase in loop area, still fits into the table top space available.

The circuit (Fig. 1) shows a  $5\frac{1}{8}$  turns loop, L1, plus impedance matching coil, L2. The inductors are resonated by variable capacitors C3 and C4. C3 sets the band segment to be used, and C4 is a small bandspread tuner.

A 48-inch (approx. 122 cm) length of RG58 coax cable is fed via C1 and C2, in parallel, to the junction of L1 and L2. Capacitor C2 is a preset variable type providing a fine coupling adjustment.

Maximum radiation is on the outer turns of L1 ( $H_i-I$ ), and minimum radiation on the inner turns ( $H_i-E$ ). The radiation pattern (polar diagram) is shown in Fig. 2. It will be realized that the large lobe has to be pointed towards the station to be contacted. In the

 


Fig. 2. Theoretical polar radiation pattern of the QTC loop.

author's shack the loop usually stands on a small turntable for simple manual rotation.

The antenna has a built-in tuning meter seen at the bottom of the circuit. This is basically a RF probe of which the sensitivity is reduced to an absolute minimum, so that a 'sample' of the transmitted signal can be taken from the outer turn of L1. The sensitivity of the probe is controlled by the value of resistor R, as well as by the length and position of the mini-antenna.

All components are neatly located in a plastic control box as shown in Figs. 3 and 4. The RF meter assembly is mounted in a Terry clip on top of the box, with the diode, the resistor and capacitor C5 wired behind the meter. This method was adopted to enable the tuning assembly to be used on other experimental antenna models.

The complete loop assembly is shown in Fig. 4. When designing such a loop, it is essential that metal parts be avoided, which means that you have to use wood and plastic construction throughout.

## Construction

As shown in Figs. 1 and 4, the loop frame consists of eight 'spokes'. These are made of four lengths of moulded hardwood, each 30 inch long,  $\frac{5}{8}$ -inch wide and  $\frac{1}{4}$ -inch thick (approx.  $76.2 \times 1.6 \times 0.6$  cm). A 2BA (5 mm) clearance hole is drilled in the centre of each spoke, and after an application of glue, the spokes are clamped together with a 2BA bolt, overlapping in the order illustrated. The whole is given a polyurethane varnish. A 6-way 2-amp polythene terminal block is screwed to the end of each spoke. These provide the necessary spacing and insulation of the wire turns.

A  $23 \times 0.8 \times 0.8$ -inch (approx.  $58.4 \times 2 \times 2$ -cm) vertical wooden support is glued and bracketed to a suitable wooden base, the whole being teak wood stained. The loop frame is then glued and bolted to the top of the vertical support.

The loop winding, L1, uses PVC-covered stranded 7/0.2 mm wire with an outside diameter of 1.2 mm and an electrical rating of 1 kV/1.5 A. After loosening all grub screws in the terminal blocks, the wire is threaded through, turn by turn, for  $5\frac{1}{8}$  turns starting at the outer left-hand lower frame spoke, and threading through all blocks in a

 


Fig. 3. Mechanical outline of the antenna tuning unit and the field strength indicator.

## COMPONENTS LIST

C1 = 3750 pF 500V silver-mica capacitor.

C2 = 100 pF preset capacitor (Jackson C803).

C3 = 75 pF variable capacitor (Jackson C809), plus knob.

C4 = 12.7 pF variable capacitor (Jackson C16), plus knob.

C5 = 22 nF mica capacitor.

M = 250  $\mu$ A f.s.d. 40  $\times$  40 mm moving coil meter (Maplin LB808).

D = HF silicon diode.

R = 1 k $\Omega$  resistor (see text).

L1 =  $5\frac{1}{8}$  turns of PVC covered stranded 7/0.2 mm wire. Outside diameter: 1.2 mm, 1 kV/1.5 A rating (see text).

L2 = 13 turns 16SWG tinned wire, 1 inch internal diameter (see text).

Feedline = 48 inch RG58 coaxial cable, plus plug to suit transmitter.

Box = ABS box type MB3, 118  $\times$  96  $\times$  45 mm. Maplin ref. LH22.

Terminal blocks = qty. 4 12-way 2 amp terminal block. Maplin ref. FE78.


Spacers = qty. 3 insulated spacer type M3, 30 mm long. Maplin ref. FS40T.

Spokes = qty. 4 8-foot lengths of  $\frac{5}{8} \times \frac{1}{4}$  inch moulded hardwood (DIY store).

Vertical support =  $23 \times 0.8 \times 0.8$  inch wood (DIY store).

Wood base =  $12 \times 8 \times 0.5$  inch plywood or similar.

 $2\frac{1}{2}$  inch steel support bracket.



910078-14

1. 4 lengths moulded hardwood 30" x 5/8" x 1/4". Varnished. 2BA holes drilled in the centre. Glued and bolted together.
  2. 8 off 6-way 2-amp polythene terminal blocks used as insulated wire spacers.
  3. 5 1/8 turns of PVC stranded wire (for specs see components list).
  4. See Fig. 3.
  5. Wood vertical support 23" x 0.8" x 0.8", wood stained.
  6. 2" x 2BA bolt.
  7. Box front vertical support, 4 1/2" x 1 1/2" x 3/4", wood stained.
  8. Wood base 12" x 8" x 1/2" (or similar), wood stained.
  9. 2 1/2 steel support bracket behind wood vertical support.
  10. Drilled and secured with glue and c/s wood screws.
- Note: " = inch = 2.54 cm.

Fig. 4. The construction of the antenna is based on commonly available parts and materials. The 'spokes' are bolted and glued together in the centre.

reducing anti-clockwise spiral. The loop is terminated at the inner of the lower right-hand spoke, as shown in Fig. 4. Wire tails are left at the loop ends for cutting and connecting later. After tightening the loop turns, the insert screws in the terminal blocks are tightened sufficiently to keep the turns straight.

After fitting the variable capacitors and insulating pillars in the box (Fig. 3), the box is bolted to the main vertical support. An extra, smaller, vertical wood member secures the box front to the wood base with screws and glue. The meter assembly is secured to the front lid of the box lid with the aid of a large plastic-coated Terry clip. The RG58 coaxial feedline enters the box at the rear (Fig. 3), and is cleated down to the vertical support and along the wood.

Inductor L2 is soldered to tags on the two left-hand insulated pillars. It consists of

13 turns of 16SWG (16AWG, approx. 0.6 mm dia.) tinned copper wire wound to 1 inch (2.54 cm) diameter. The turns are then spaced to about 1.5 times the wire thickness. The whole loop assembly is now wired as shown in Figs. 1, 3 and 4.

## Testing and operation

Initial tests are made with a receiver. On the prototype with the bandspread, C4, at mid capacity, it was found that by rotating C3 the frequency range was 2,500 kHz to 4,500 kHz, which adequately covers the 80-m band (3,500 to 3,800 kHz), with some overlap. In the USA and elsewhere, the 80-m band is extended to 4,000 kHz. Resonance is indicated by a peak of noise and signal strength in the receiver. The radiation pattern can be checked on a selected signal by

rotating the loop for maximum signal strength. From Fig. 2 it will be seen that this coincides with the large lobe. Further rotation of the loop through 360 degrees gives a radiation pattern as shown.

In practice, C4 is set to minimum capacitance, and C3 is tuned to start of the selected band segment. For instance, if the required operating segment is 3,500 to 3,800 kHz, C3 is set to about 3,600 kHz (with C4 at minimum capacitance). Bandsread control C4 is then used to tune the loop, giving fine tuning over 3,500 to 3,600 kHz, and so on.

The transmitter adjustment is as follows:

1. Connect the transmitter to a 50-Ω dummy load. Set the transmitter to the selected frequency and adjust the P.A. for optimum loading.
2. Remove the dummy load and substitute the loop.
3. Resonate C4 to the transmitter frequency, and peak the coupling preset adjustment, C1.
4. It should be possible to use the transmitter at  $\pm 20$  kHz of the setting up frequency without retuning the loop with C4. Minor adjustments of C4 will easily retune the loop outside this bandwidth, as required.

Proceed with the adjustment of the tuning meter. The mini-antenna consists of a few turns of stiff wire wound around a pencil. Remove the wire from the pencil, and position the end of it directly under the bottom turn of L1. The mini antenna is manipulated up and down so that the meter reads about 3/4 full-scale when the transmitter is correctly loaded. When retuning the transmitter during operation, the meter should always peak around this point, provided the transmitter power is unaltered. Note, however, that the sensitivity of the meter depends also on the value of resistor R and the transmitter power. The value shown, 1 kΩ, is satisfactory for a transmitter power of about 5 to 10 watts. For higher or lower power transmitters, the value of R is changed experimentally.

When operating the antenna it should be kept a loop diameter away from walls, pipes and electrical wiring. It will be noticed that due to the loop directivity the received level of interference is well down on a normal antenna. Best results will be obtained when the large radiation lobe is pointed directly at the station being contacted.

Finally, note that the loop antenna is intended as a low-power device for indoor use. In the interest of safety, a transmitter power of 20 watts should not be exceeded. No doubt the design could be re-engineered for higher power and outdoor use. ■

## References:

1. "The Miser's T/R loop antenna" by R.Q. Marris, *Elektor Electronics* November 1990.
2. The Admiralty handbook of Wireless Telegraphy, Volume 2, 1938.

## For further reading:

- The ARRL Antenna Book, 14th edition.
- Antennas (2nd edition), 1988, by John D. Kraus (McGraw-Hill).



# INTERMEDIATE PROJECT

**A series of projects for the not-so-experienced constructor. Although each article will describe in detail the operation, use, construction and, where relevant, the underlying theory of the project, constructors will, none the less, require an elementary knowledge of electronic engineering. Each project in the series will be based on inexpensive and commonly available parts.**

## LIGHT TRANSMITTER/RECEIVER

**This month we present an experimental circuit to demonstrate that visible light can be modulated and used as a carrier to convey information. Depending on the power of the bulb you use, and the optics for the transmitter and the receiver, this low-cost communication system will carry speech signals over distances of tens to hundreds of metres.**

**T. Giffard**

**I**N principle, the intensity of a light beam from an electrical source, such as a bulb, can be used as a carrier to convey an audio signal from one point to another. This type of amplitude modulation (AM) can be achieved by using the audio signal to vary the voltage applied to the bulb. The light transceiver described here is intended as an introduction to wireless communication using amplitude modulation. The circuits have been kept simple and can be assembled

and put to use in single evening or a rainy afternoon. When used for an experiment rather than a fixed communication link, the transceiver can be even simpler than shown here because existing amplifiers may be used.

Compared to, say, an infra-red emitter there are certain restrictions to the use of common low-voltage bulbs as light sources for an AM-based communication link, and the modulation will not be perfect. Still, the

quality of the system will be good enough for a reliable voice link.


### On modulation and filaments

Modulating the light intensity of a bulb is not so difficult. However, the relation between the intensity and the filament voltage is not quite as linear as we would like. In practice, the best results are obtained with low-voltage bulbs that have a thin, straight filament. These bulbs, which are used in bicycle rear lights, have a relatively rapid response to filament voltage variations, and are therefore capable of 'following' a speech or music signal.

The response of a bulb to sine-wave modulation can be significantly improved by applying a direct voltage to the filament, and superimposing the sine-wave. In practice, the best results are obtained with the fixed voltage set such that the bulb lights at half the nominal intensity. This also sets the maximum value of the applied alternating voltage, whose peak value may not exceed the direct voltage. When the voltages are equal, the modulation depth is 100%. In the absence of an alternating voltage component, the modulation depth is 0%.

### The light transmitter

The circuit of the light transmitter is shown at the left in Fig. 1. It supplies the light source, bulb La1, with a direct voltage as well

 

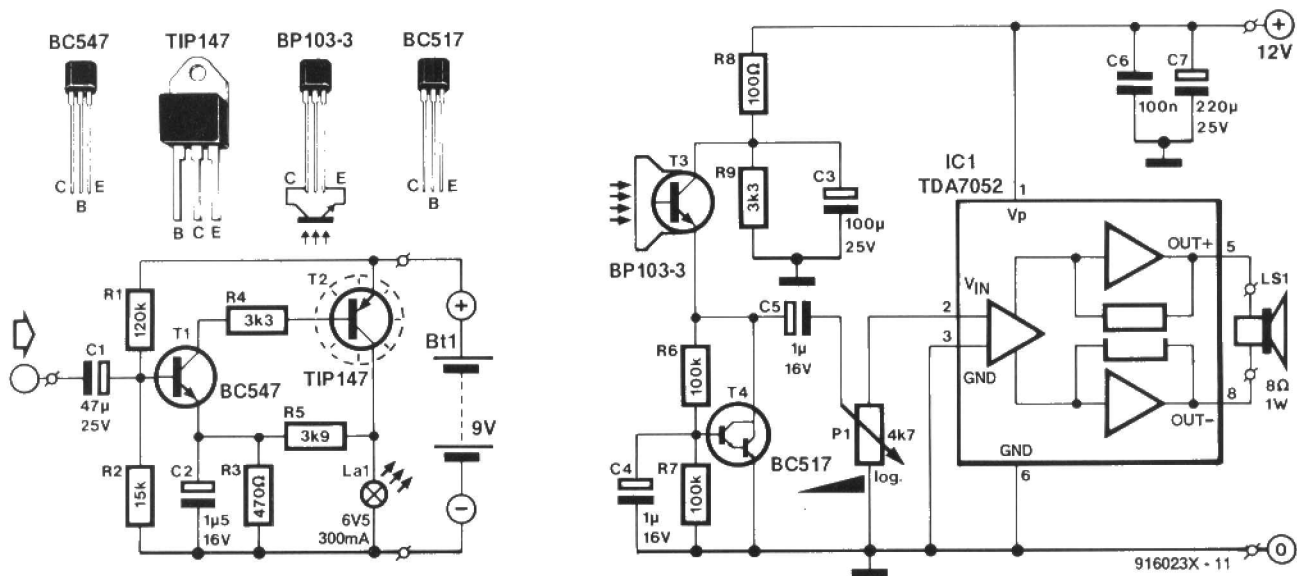


Fig. 1. Circuit diagram of the light transmitter (left) and the associated receiver (right). The IC-based audio amplifier in the receiver, a TDA7052, is optional and may be replaced by any other amplifier you may have available.

as with the modulation signal. The bulb is connected in the collector line of a medium-power transistor, T2, which functions as an amplifier. When there is no input signal, the collector of T2 is at about half the supply voltage. An audio input signal applied to the base of T2 causes the collector voltage to

swing between 0 V and the supply voltage. This ensures that La1 is supplied with the optimum voltage for amplitude modulation.

Transistor T1 raises the audio input signal and at the same time keeps the quiescent voltage across La1 at about half the supply voltage. The transistor monitors the collector

voltage of T2 via resistor R5, and controls the base voltage of T2 accordingly. A decoupling capacitor, C2, prevents T1 acting on the modulation voltage at the collector of T2. The voltage control is effective only when the average collector voltage of T2 is no longer correct. The operation of this type of feed-

## COMPONENTS LIST

### Resistors:

1	120k $\Omega$	R1
1	15k $\Omega$	R2
1	470 $\Omega$	R3
2	3k $\Omega$ 23	R4;R9
1	3k $\Omega$ 29	R5
2	100k $\Omega$	R6;R7
1	100 $\Omega$	R8
1	4k $\Omega$ 27 log. potentiometer	P1

### Capacitors:

1	47 $\mu$ F 25V radial	C1
1	1 $\mu$ F 16V radial	C2
1	100 $\mu$ F 25V radial	C3
2	1 $\mu$ F 16V radial	C4;C5
1	100nF	C6
1	220 $\mu$ F 25V radial	C7

### Semiconductors:

1	BC547	T1
1	TIP147	T2
1	BP103-3	T3
1	BC517	T4
1	TDA7052	IC1

### Miscellaneous:

1	8 $\Omega$ 1W loudspeaker	LS1
1	6.5V 0.3A bulb	La1
1	Heat-sink for T2	
2	Printed-circuit board	UPBS-1

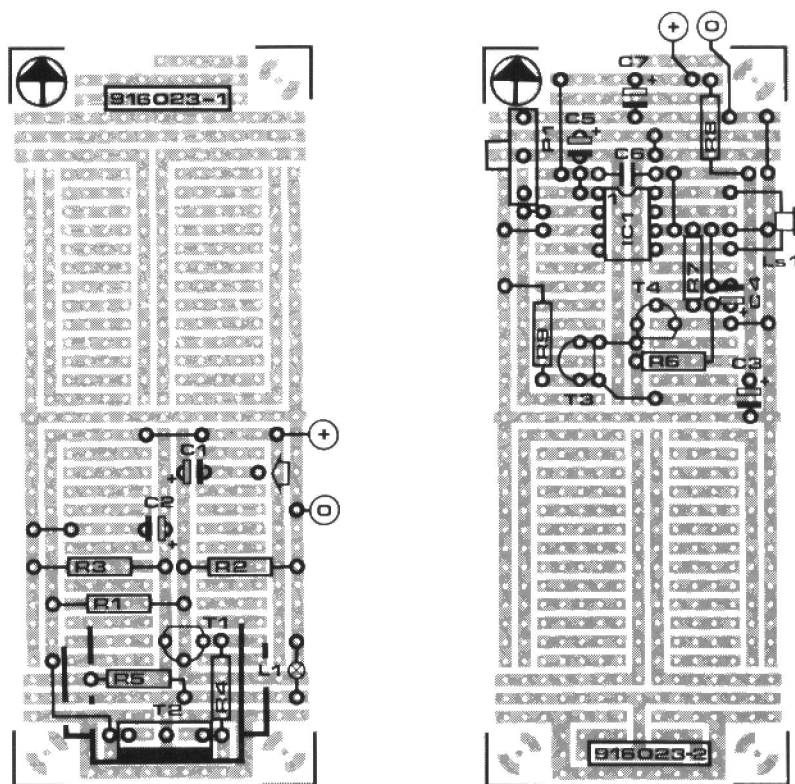


Fig. 2. Component mounting plans of the transmitter (left) and the receiver (right). Both are built on ready-made prototyping boards (see the components list).

back is fairly simple. Assuming that the collector voltage of T2 drops, R5 supplies a lower voltage at the emitter of T1. Since the base voltage of T1 is fixed with the aid of a voltage divider, R1-R2, the transistor starts to draw more collector current, resulting in more current fed into the base of T2. Consequently, the collector current of T2 rises, so that the collector voltage rises also. In this way the initial voltage drop is counteracted and the bulb voltage held constant at about 4.5 V.

## The light receiver

The main component in the circuit of the light receiver (shown at the right in Fig. 1) is a photo transistor, T3. The collector current of this transistor is a function of the intensity of the light incident on the device. If the incident light is produced by the light transmitter, the emitter voltage of T3 is a copy of the modulation signal applied to the transmitter. The demodulated signal is fed to a small a.f. amplifier, IC1, via coupling capacitor C5 and volume control P1. The a.f. amplifier, a TDA7052, has a voltage gain of about 100.

Returning to the phototransistor, the emitter potential is held constant by a volt-

 


Fig. 4. The transmitter uses a plastic reflector from a pocket torch, while the phototransistor in the receiver is fitted in a reflector of a type normally used for infra-red emitters.

age source based on T4. Assuming that the emitter voltage of T3 rises, the base current of T4 rises via resistor R6. Consequently, the collector current of T4 rises, so that the collector voltage drops. This keeps the emitter voltage of the photodiode in check. Like C2 in the transmitter, C4 prevents the voltage stabilizer acting on the modulation signal, which changes much faster than the average emitter voltage of the photodiode.

## Construction and use

The transmitter and receiver circuits are so simple that they are easily constructed on prototyping boards as shown in Fig. 2. If you want to make a duplex system where each 'station' consists of a transmitter and a receiver, you will require two prototyping boards (order code UPBS-1). For a one-way light link, a single board may be cut in two to accommodate the transmitter and receiver circuit. The photographs in Fig. 3 show the transmitter and the receiver built on two prototyping boards.

There are several options for the construction of the optics. At the transmitter side, you may use a reflector from a torch (see Fig. 4). At the receiver side, a concave reflector is used of the type found on infra-red remote controls. In most cases, the BP103 phototransistor will fit in the opening for an infra-red LED. It will be clear that the distance covered by the system will depend on the size of the optics used. In general, the larger the diameter of the reflectors, the better (an example of the use of car headlight and a magnifying glass for a long-range infra-red communication system is given in Ref. 1). A few prototypes with different coverage were built in torches as shown in the introductory photograph.

You may also want to experiment with the wattage of the bulb used in the transmitter. Note, however, that relatively high bulb

powers require T2 to be fitted with a heat-sink.

The transmitter draws a relatively high current, and is best powered by a regulated supply or a rechargeable 9-V battery block. The receiver has a very modest power consumption, and can be supplied from a small mains adapter. In some cases, however, such an adapter may produce an unacceptable hum level in the receiver. Fortunately, the hum is simple to suppress by fitting larger supply decoupling capacitors in positions C3 and C7.

Finally, note that the bulb in the transmitter will emit visible as well as infra-red light. This allows you to use an infra-red sensitive phototransistor such as the BPW40 if the BP103 proves difficult to obtain. ■


## Reference:

1. "Long-range infra-red transceiver". *Elektronika* November 1987.

Fig. 4. Prototypes built on two boards type UPBS-1
 
# VARIABLE A.C. POWER SUPPLY

Stabilized and regulated d.c. power supplies are readily available in many shapes and sizes. By contrast, a regulated and perhaps even stabilized a.c. power supply is difficult to find at a reasonable price. The adjustable transformer is in many cases the only alternative, but it, too, is pretty expensive. In this article we present a simple 25-V 1-A a.c. power supply that deserves a fixed place on any electronics workbench.



**L. Lemon**

**A**N alternating voltage is much more difficult to stabilize than a direct voltage. In fact, there are two quantities that must be stabilized: the voltage proper (or its amplitude), and the frequency. Since it was intended to keep the present supply as simple as possible, frequency stabilization is not provided. The mains frequency is used here because it is fairly stable and suitable for most applications.

## Block diagram

The operating principle of the present supply is to stabilize an alternating voltage with the aid of an adjustable potential divider. As shown in the block diagram in Fig. 1, the potential divider is controlled electronically, and forms part of a regulation loop. A power transistor is used as an adjustable resistor in a diode bridge. The bridge is required because the transistor can handle direct current only. Unfortunately, it has two disadvantages: first, it introduces a voltage loss of two times the forward diode voltage; second, because of their threshold voltage, the diodes do not conduct around the zero crossing of the alternating voltage. As shown in the oscilloscope photograph in Fig. 2, the thresholds cause small flattened parts around the zero crossing of the output voltage. In amplifier terminology this effect is known as cross-over distortion. Fortunately, the effect is of little consequence here, and it can be tolerated bearing in mind that we set out to de-

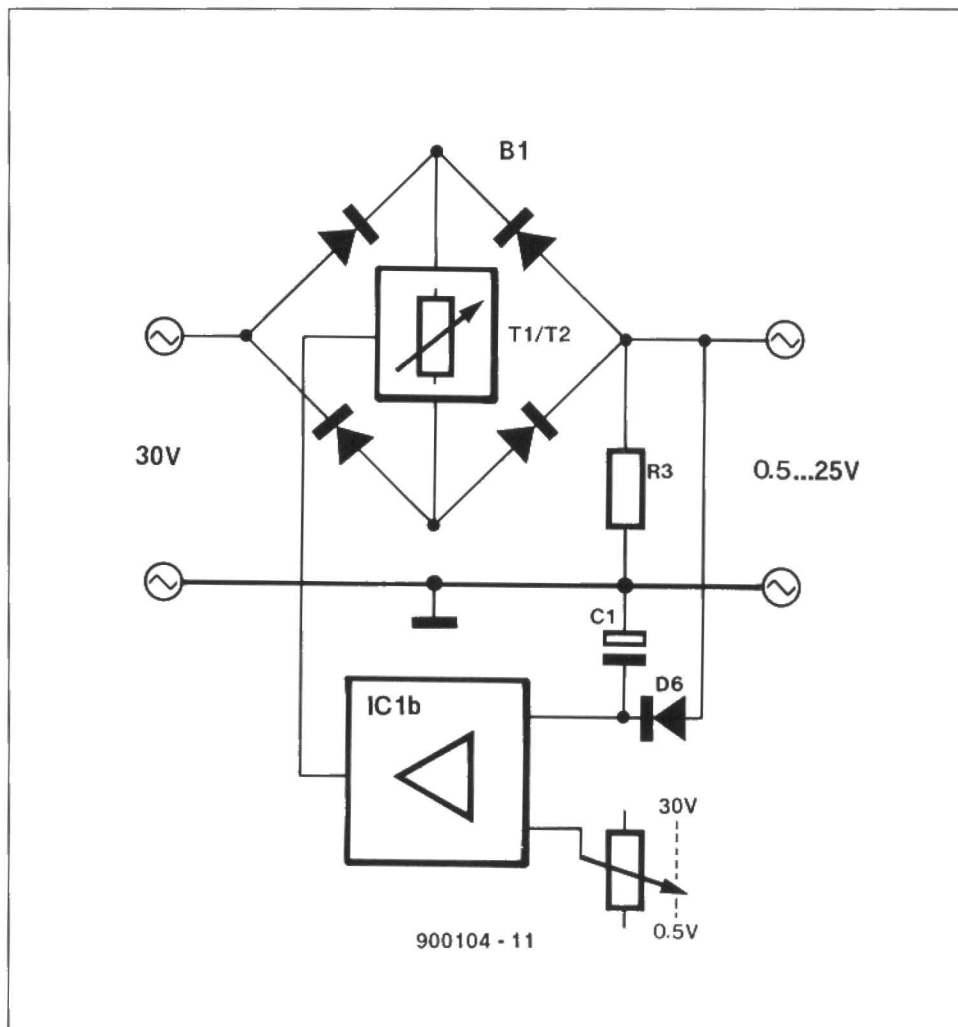


Fig. 1. The alternating voltage is stabilized by comparing the peak value with a preset voltage. The resulting error signal is used to control a variable resistor in a diode bridge.



 


Fig. 2. Output waveform of the power supply. The cross-over distortion is caused by the small forward drop across the diodes in the rectifier bridge.

sign a simple a.c. power supply. Along this train of thought, the supply is based on measuring the peak value of the output voltage, rather than the instantaneous voltage, which is far more difficult. The peak voltage exists across  $C_1$ , which is charged by rectifier  $D_6$ . A difference amplifier compares the measured peak value with the value set by the output voltage control, potentiometer  $P_2$ . Differences between the two voltages cause an error signal that serves to adjust the output voltage until the difference is zero, i.e., until the set output voltage is achieved.

### Circuit description

The circuit diagram of the variable a.c. power supply is fairly simple — see Fig. 3.

The alternating voltage circuit is almost identical with the block diagram. The diode bridge is formed by a bridge rectifier Type B80C3200/2200 (80 V p.i.v., 3.2 A peak, 2.2 A continuous), and the adjustable resistor by transistors  $T_1$ - $T_2$ . Resistor  $R_3$  completes the potential divider.

The voltage control circuit is a little more complex than suggested by the block diagram. The peak voltage rectifier,  $D_6$ - $C_1$ , is followed by a potential divider,  $R_4$ - $R_5$ . This prevents the voltage across  $C_1$  exceeding the supply voltage of  $IC_{1a}$  (the peak value of a 25-V alternating voltage is much greater than 12 V). The output voltage is indicated by a moving-coil meter,  $M_1$ , which is calibrated for 25-V f.s.d. (full-scale deflection) by preset  $P_1$ .

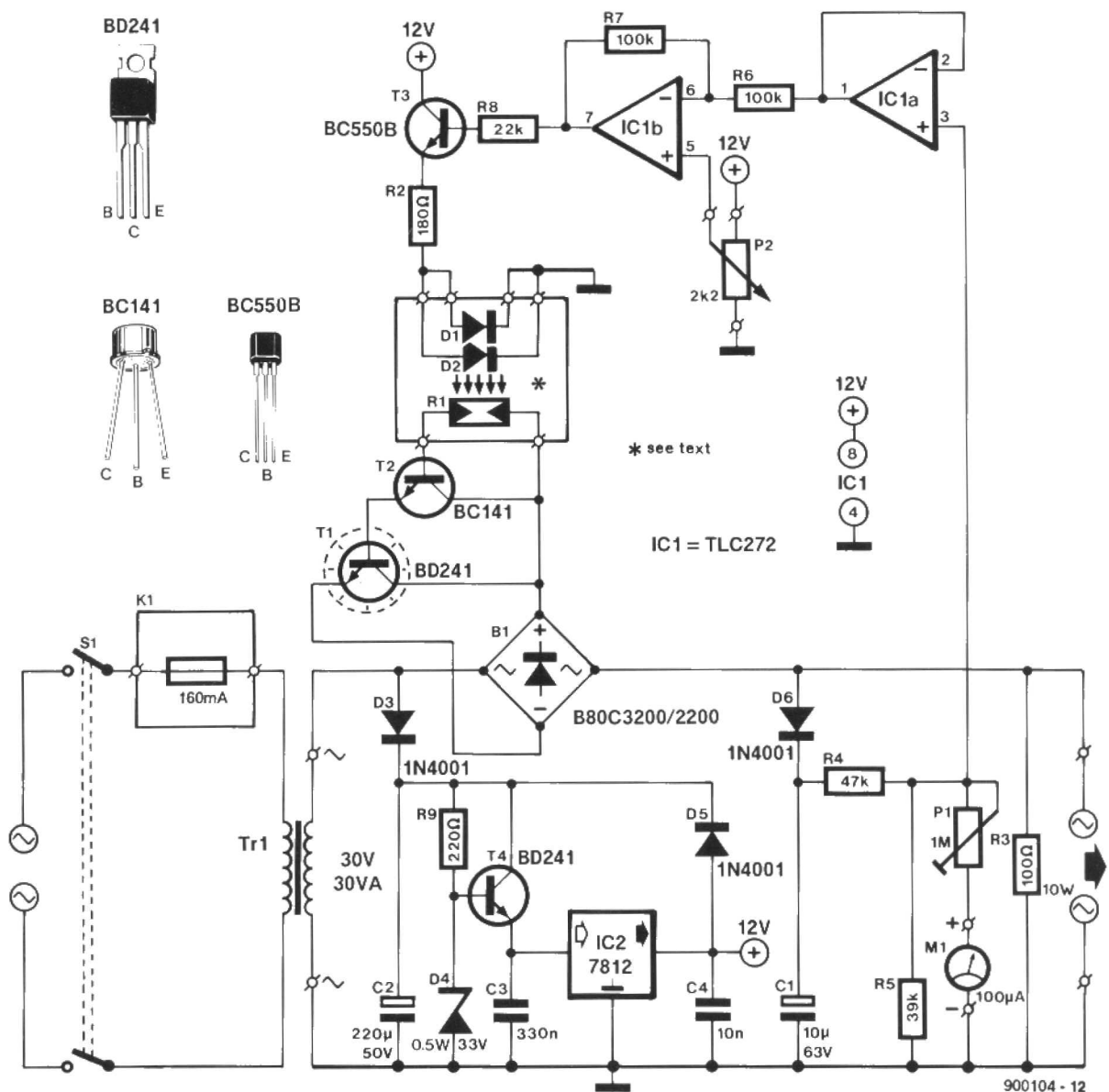


Fig. 3. Circuit diagram of the a.c. power supply. The optocoupler shown here is a home-made type consisting of two LEDs and an LDR.

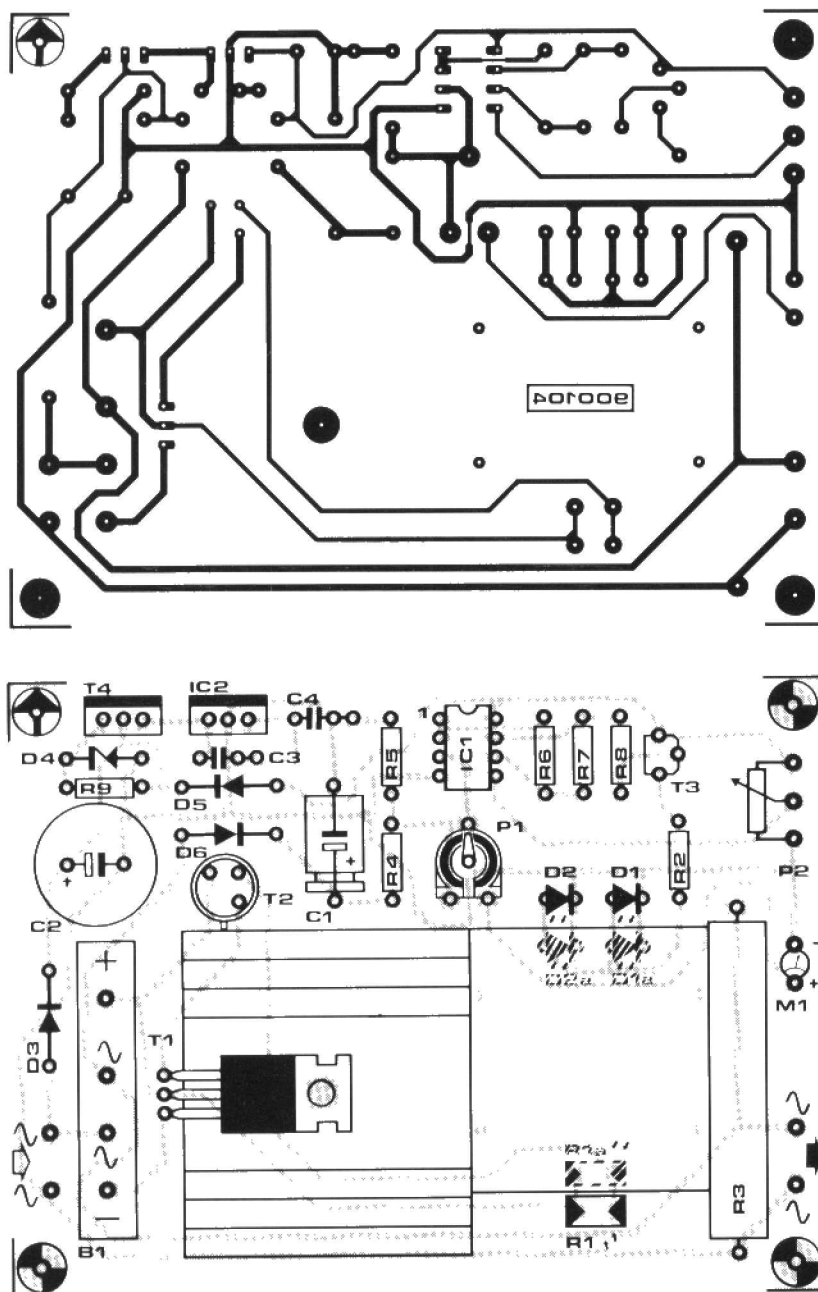


Fig. 4. Single-sided printed circuit board for the a.c. power supply.

 


Fig. 5. Basic construction of the home-made optocoupler.

## COMPONENTS LIST

### Resistors:

1	LDR	R1
1	180Ω	R2
1	100Ω 10W	R3
1	47kΩ	R4
1	39kΩ	R5
2	100kΩ	R6;R7
1	22kΩ	R8
1	220Ω	R9
1	1MΩ preset H	P1
1	2kΩ lin. potentiometer	P2

### Capacitors:

1	10μF 63V axial	C1
1	220μF 50V radial	C2
1	330nF	C3
1	10nF	C4

### Semiconductors:

2	red LED	D1;D2
3	1N4001	D3;D5;D6
1	33V 0.4W zener diode	D4
1	B80C3200/2200	B1
2	BD241	T1;T4
1	BC141	T2
1	BC550B	T3
1	TLC272	IC1
1	7812	IC2

### Miscellaneous:

1	double-pole mains switch	S1
1	mains appliance socket with integral fuseholder	K1
1	mains transformer 30V @1A, e.g., ILP 11013 (220V mains) or ILP 13013 (240V mains)	Tr1
1	100μA moving-coil meter	M1
1	160mA fuse (slow)	
1	heat-sink for T1; 7K/W	
2	heat-sink for T4 and IC2; 30K/W	
1	printed-circuit board	900104
1	front-panel foil	900104-F
1	enclosure LC850 (manufacturer: Telet; supplier: C-I Electronics)	

Opamp IC1a buffers the voltage supplied by R4-R5, and drives IC1b, the difference amplifier proper. Potentiometer P2 forms the output voltage control. The voltage at its wiper is compared with the voltage supplied by IC1a. The error voltage supplied by IC1b is buffered by T3, and used to control the intensity of two parallel-connected LEDs in an optocoupler. The LDR (light-dependent resistor) at the other side of the optocoupler determines the resistance formed by T1.

Unfortunately, the power supply has some shortcomings because of the use of a power transistor as an adjustable resistor in the regulating circuit. For one thing, the resistance can not become nought since T1 will introduce a minimum drop of about 2.5 V. Add that to the drop across the diodes, and you will realize that the total voltage loss introduced by the regulator is about 4 V. Similarly, T1 can never be turned off completely.

 


Fig. 6. Layout of the front panel foil (shown here at about 70% of true size). This foil is available ready-made through the Readers Services.

This means that the supply can not be set to an output voltage of 0 V. Fortunately, the actual minimum output voltage is quite low at a value smaller than 0.5 V.

The regulation circuit is powered by the mains transformer via rectifier D3-C2. Components R9, D4 and T4 reduce the rectified voltage to about 33 V, which can then be safely applied to the input of a 12-V regulator, IC2.

## Construction

The construction of the power supply is straightforward if you use the printed-circuit board shown in Fig. 4. The optocoupler

is a home-made device. The construction is shown in Fig. 5. Use a length of PVC tubing, a (black) spool of a photographic film, or cut a piece of thin, black decoration cardboard to size and roll it into a tube.

The printed-circuit board enables the LDR and the LEDs to be connected in two ways, allowing you to determine where the respective component terminals exit from the optocoupler assembly.

The heat-sinks of T4 and IC2 need not be large — in most cases, two pieces of aluminium of an area of about 15 mm<sup>2</sup> will do. Make sure that the heat-sinks do not touch. Alternatively, IC2 and T4 may be mounted on a common heat-sink, provided both com-

ponents are fitted with insulating washers.

The power supply is housed in a metal enclosure Type LC850 from Telet. The dimensions of the blue-and-grey self-adhesive front-panel foil for the supply (Fig. 6) are geared to this type of enclosure.

The two toroid transformers stated in the components list have two 15-V secondary windings, which must be connected in series to obtain the required 30 V.

The power supply has only one adjustment. Connect an a.c. voltmeter to the supply and set an output voltage of 25 V. Next, adjust P1 until the moving-coil meter indicates the same value. ■

## 6-metre band converter

April 1991, p. 38-43

The components list and the inductor overview in the top left hand corner of the circuit diagram should be corrected to read:

L1, L2 = 301KN0800.

Capacitor C16 (4.7 pF) must not be fitted on the board.

Finally, a few constructional tips:

- Fit a 10 nF ceramic decoupling capacitor at junction L7-R36.
- Fit a 18 kΩ resistor between the base of T3 and ground. This reduces the Q factor of L2, and prevents too high signal levels at the base of T3.
- For improved tuning, inductor L9 may be replaced by a Toko Type 113KN2K1026HM.

## Multifunction measurement card for PCs

January and February 1991

We understand that the 79L08 (IC17) is no longer manufactured and, therefore, difficult to obtain. Here, the IC may be replaced by a 7908, which, although physically larger

## CORRECTIONS

than the 79L08, is pin-compatible, and should fit on the PCB.

## Dimmer for halogen lights

April 1991, p. 54-58

In the circuit diagram of the transmitter, Fig. 2, pin 14 of the MV500 should be shown connected to pin 13, not to junction R1-R2-C2. The relevant printed-circuit board (Fig. 6) is all right.

## RDS decoder

February 1991, p. 59

Line A0 between the 80C32 control board and the LC display is not used to reset the display, but to select between registers and data.

We understand that the SAF7579T and the associated 4.332 MHz quartz crystal are difficult to obtain through Philips Components distributors. These parts are available from C-I Electronics, P.O. Box 22089,

6360 AB Nuth, Holland. For prices and ordering information see C-I's advertisement on page 6 of the May 1991 issue.

## S-VHS-to-RGB converter

October 1990, p. 35-40

Relays Re1 and Re2 must be types with a coil voltage of 5 V, not 12 V as indicated in the components list. Constructors who have already used 12-V relays may connect the coils in parallel rather than in series.

Suitable 5-V relays for this project are the 3573-1231.051 from Günther, and the V23100-V4305-C000 from Siemens.


The components list should be modified to read:

6 33nF

C57-C62

# LASER
 
## PART 2: CONTROL UNIT LSI7000 (CIRCUIT DESCRIPTIONS)



Following last month's description of the laser exciter and the mirror galvanometer assembly we now turn to a state-of-the art electronic control unit for the show laser.

*Continued from the May 1991 issue.*

The laser control unit described here is a fairly complex design capable of producing attractive laser patterns. The complete control unit contains some 250 resistors, 100 capacitors and 40 integrated circuits. Fortunately, the assembly of the kit is pretty easy, although it will require several hours of careful soldering work. More about this next month, though, as the present instalment deals mainly with circuit descriptions.

### Pretty sine-waves

Many of you will be familiar with Lissajous patterns on an oscilloscope. Being rather static, Lissajous patterns would appear to be less suitable as show effects for a laser as discussed here. Bear in mind, however, that an oscilloscope produces such patterns when fed with two fixed signals only. A first step towards the creation of moving Lissajous patterns is simply to replace one of the fixed signals by a music signal (or, more generally, an audio signal). The result is a pretty erratic type of pattern on the scope. Some static patterns can be interesting, too, and are simple to produce by increasing the number of sine-waves. The present laser control unit supplies four sine-waves that allow a wide variety of patterns to be created.

The block diagram in Fig. 8 is fairly com-

plex, and indicative of the number of components used to build the laser control unit. The output of the circuit is formed by two 1-watt a.f. power stages that drive the coils in the mirror galvanometers. An electronic double-pole changeover switch fitted ahead of the power output stages allows you to swap the drive signals produced by the two audio interface channels, left and right.

Since the right and left channels are virtually identical, the circuit description will refer to one channel only, in this case, the left one. The input signals for the power output stages are supplied by an electronic potentiometer that allows you to control, independently, the signal frequency (i.e., the shape of the pattern) and the signal amplitude (i.e., the size of the pattern).

There are three sources for the amplitude control signal, which is selected via electronic switches. When the constant voltage source is selected, you can control the size of the pattern via the LEVEL potentiometer. The level information is obtained from an envelope detector when the LINE, LS (loudspeaker) or microphone signal is selected. The LEVEL potentiometer then enables you to set the maximum pattern size reached at a certain level of the input signal.


The LINE, LS and microphone signals may be used to create the laser patterns. In addition to these sources, two sine-wave generators are available of which the output

frequency can be set manually as well as by means of a timer circuit. Before these signals are applied to the electronic potentiometer, they are taken through a frequency compensation circuit that serves to correct the frequency response of the mirror galvanometers. Additionally, the audio signals are taken through a 150-Hz low-pass filter that suppresses signal components that can not be reproduced anyway.

The audio signal may be supplied by the microphone contained in the laser control unit. This microphone is used to drive both channels via a compressor circuit that ensures a fairly constant drive level. The same goes for the LINE and LS signals, which are also taken through a compressor. The difference between the LINE and the LS input is mainly the required signal level. The LINE inputs accept relatively small signals (line level), while the LS inputs can be driven with higher voltages as supplied, for instance, by the loudspeaker output of an a.f. power amplifier.

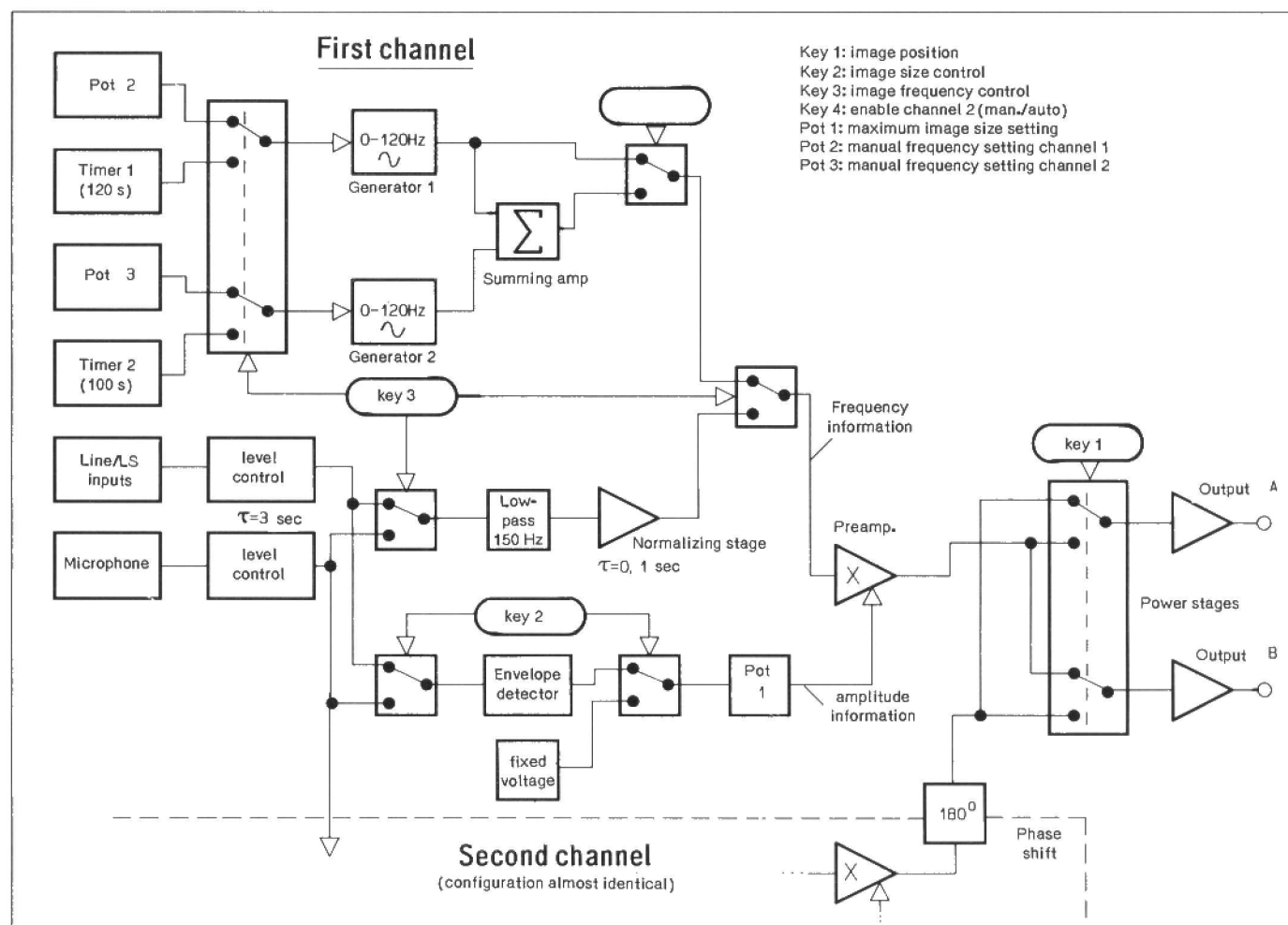Two sine-wave generators are available on each channel of the laser control unit. A switch, marked CHANNEL 2 ON/OFF, is used to select one sine-wave or the sum signal of two sine-waves. The frequency of these is determined by applying a control voltage to the generators. The control voltages can be set manually or by means of a generator that supplies a slow triangular voltage. The





909522 - II - 14

Fig. 8. Block diagram of the laser control unit.

period time of the triangle is about 100 s, but the actual value is slightly different for each of the four generators in the control unit. The differences are such that it takes more than 24 hours (theoretically) before the same pattern is repeated.

## Circuit diagram

The circuit diagram, Fig. 9, of the laser control unit follows the block diagram quite closely. For the sake of simplicity a few blocks are drawn in Fig. 2 that contain circuits discussed in detail further on.

The LINE and LS signals are applied to the circuit via sockets Bu1 to Bu4, which are connected via a potential divider for the right and left channel. This means that the LS socket and the LINE socket next to it can not be used simultaneously. Fortunately, the high impedance of the potential divider prevents damage to equipment when the LS and LINE inputs are accidentally used at the same time. The input signals are first fed to a compressor, whose operation is discussed further on.

The microphone is a small electret type with a built-in FET amplifier. It is connected to terminals ST1, ST2 and ST3. The microphone signal is amplified by IC1 before it is

applied to the compressor. The three compressors are followed by the input selection switches that enable the signals to be routed in one of two directions: to the frequency-determining circuits, or to the amplitude-determining circuits.

In the frequency-determining branch, the signal is first applied to a 150-Hz filter set up around T1 (T3 for the right channel). Then follows another switch, this time for the selection between the audio source and the generator. After the frequency compensation the signal arrives at electronic potentiometer IC4.

In the amplitude-determining branch the audio signal is fed to T2 and T4, which form an envelope detector. The switch contact that follows the detector allows the size of the patterns to be controlled manually or by the envelope waveform of the audio signal. The latter function requires a constant voltage, which is obtained from a regulated supply voltage with the aid of a potential divider. The amplitude control signal is subsequently amplified to allow the final size of the laser pattern to be set by the LEVEL control, R26-R40. Next, the level information is applied to the control inputs of an electronic potentiometer, IC4. The output signal of IC4 is buffered by IC2b and IC3b before it arrives at the

switch contacts that allow you to determine the channel assignment (left/right; L/R) for the horizontal and vertical (H/V) deflection of the laser beam. From the poles of the H/V-L/R switches the signal is taken to the inputs of the two power amplifiers that drive the mirror galvanometers.

## The generators

There are two almost identical generators in the laser control unit. The difference between them is the value of a single resistor. Figure 10 shows the circuit diagram of the generator for the left channel. All components are numbered from 100 onwards. For the right channel, the corresponding components are identified as 2xx. Note, however, that resistor R62 in the left channel appears as R64 in the right channel.

The heart of the generator is formed by two integrated circuits Type XR2206, a well-known function generator from Exar. The frequency of the output sine-wave produced by the generator is determined by a control voltage obtained either from potentiometer R141-R147 via an amplifier, or from a generator.

The circuit for the automatic frequency control of the sine-wave generator may look

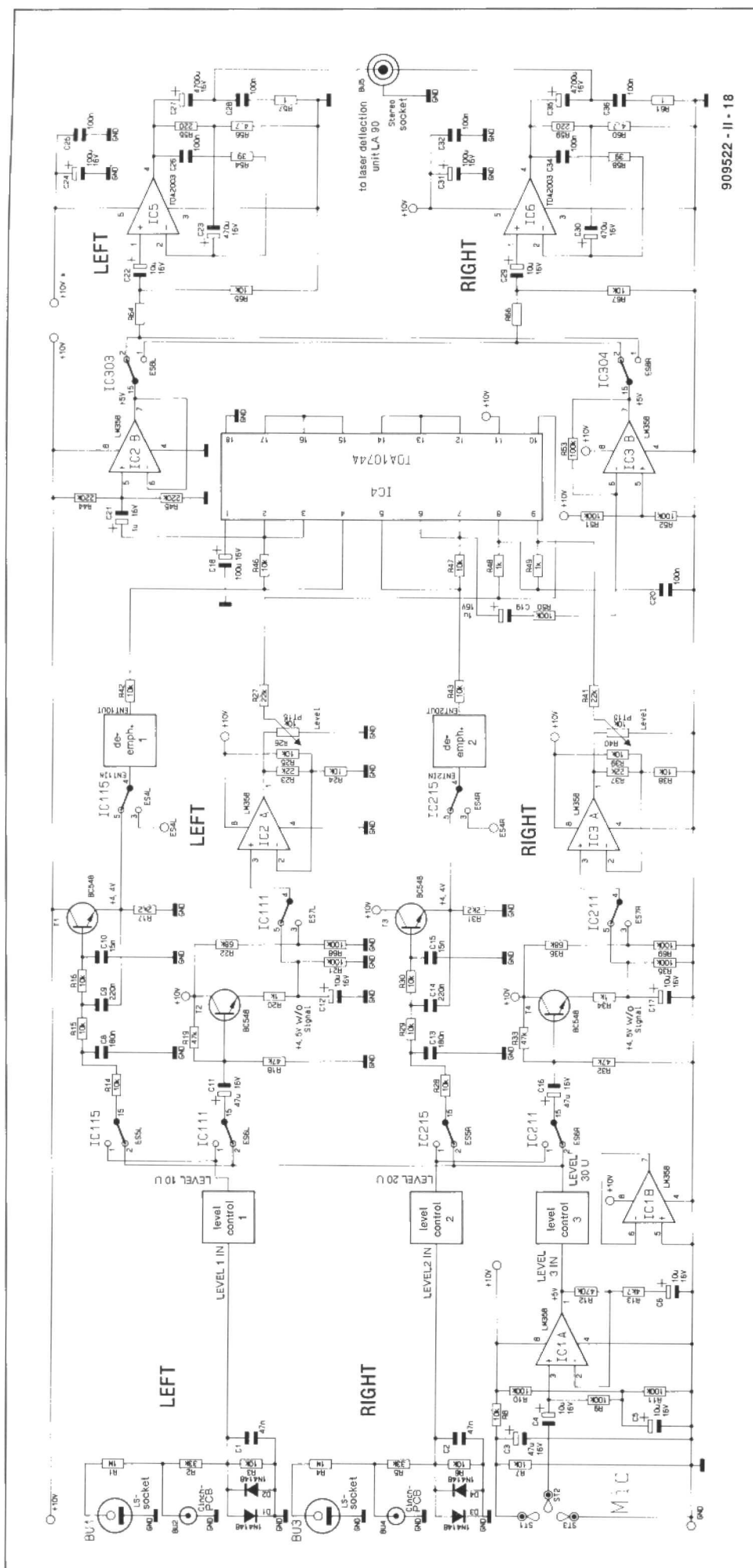


Fig. 9. Main circuit diagram of the laser control unit. Some circuit sections are shown as modules here.

unusual at a first glance. Fortunately, it operates in a rather simple way. Opamps IC103a and IC103b form two Schmitt-triggers set up as square-wave generators. Concentrating on IC103a for the moment, we see that the opamp is wired to function as a Schmitt-trigger by means of resistors R137, R138 and R139. The Schmitt-trigger is turned into a square-wave generator by components R140 and C119. A square wave is, however, not what we are after if we want the sine-wave generator to produce a continuous frequency range. Fortunately, the capacitor, C119, has on it a triangular waveform that does allow a true, linear, VCO (voltage-controlled oscillator) function to be realized. The capacitor voltage, which is a triangular waveform with a period time of about 100 s, is buffered by opamps IC103c and IC103d. Note that the period time is chosen slightly differently for the other generator. This is done to prevent the laser repeating the same pattern after 100 s when the 'automatic' mode is used. The differently set period times ensure that it takes at least 24 hours before a pattern is repeated (this is based on the assumption that component tolerances have no effect).

The generator circuit is followed by a summing amplifier, IC107, that serves to add the two sine-waves. Electronic switch IC115 allows you to select either the output signal of IC107 only, or the mixed output of the two sine-wave generators.




## The compressor

The circuit diagram of the compressor is shown in Fig. 11. The component numbers refer to the left channel — the circuit of the right channel compressor is identical, with component numbers in the '200' range. The component numbers in the microphone compressor start at 300.

Opamp IC101b supplies a stable and adequately decoupled reference voltage to the circuit. The a.f. input signal is applied to the compressor via capacitor C101. Opamp IC101a forms an amplifier whose gain is determined by FET T101, which functions as a voltage-controlled resistance. The output signal level of IC101a is monitored with the aid of a further opamp, IC101d, whose output is connected to a rectifier, D101-D102-C104. To close the a.f. level control loop in the compressor, the direct voltage supplied by the rectifier is fed to the gate of FET T101. The gate voltage determines the a.c. resistance of the drain-source junction, and thus the gain of IC101a. The compressor has an inverse level control characteristic, which means that its gain is reduced as the input signal level increases. In this manner, the compressor ensures that the mirror driver circuits are provided with a reasonably constant input signal.
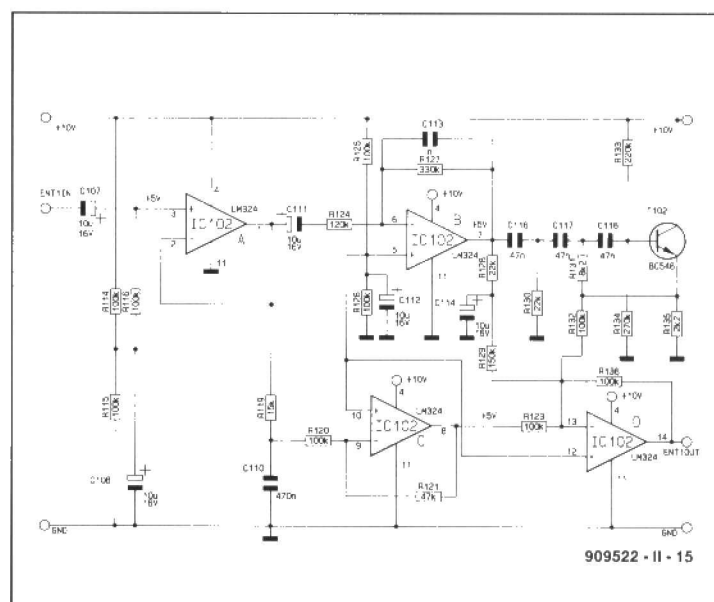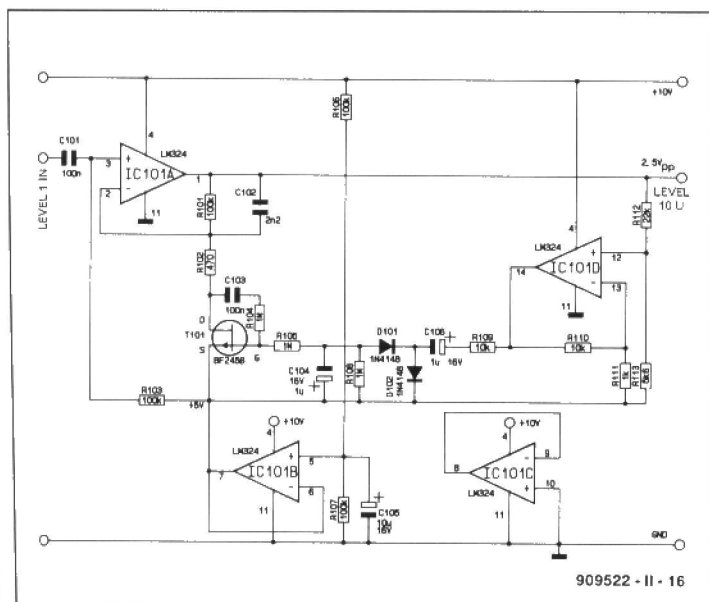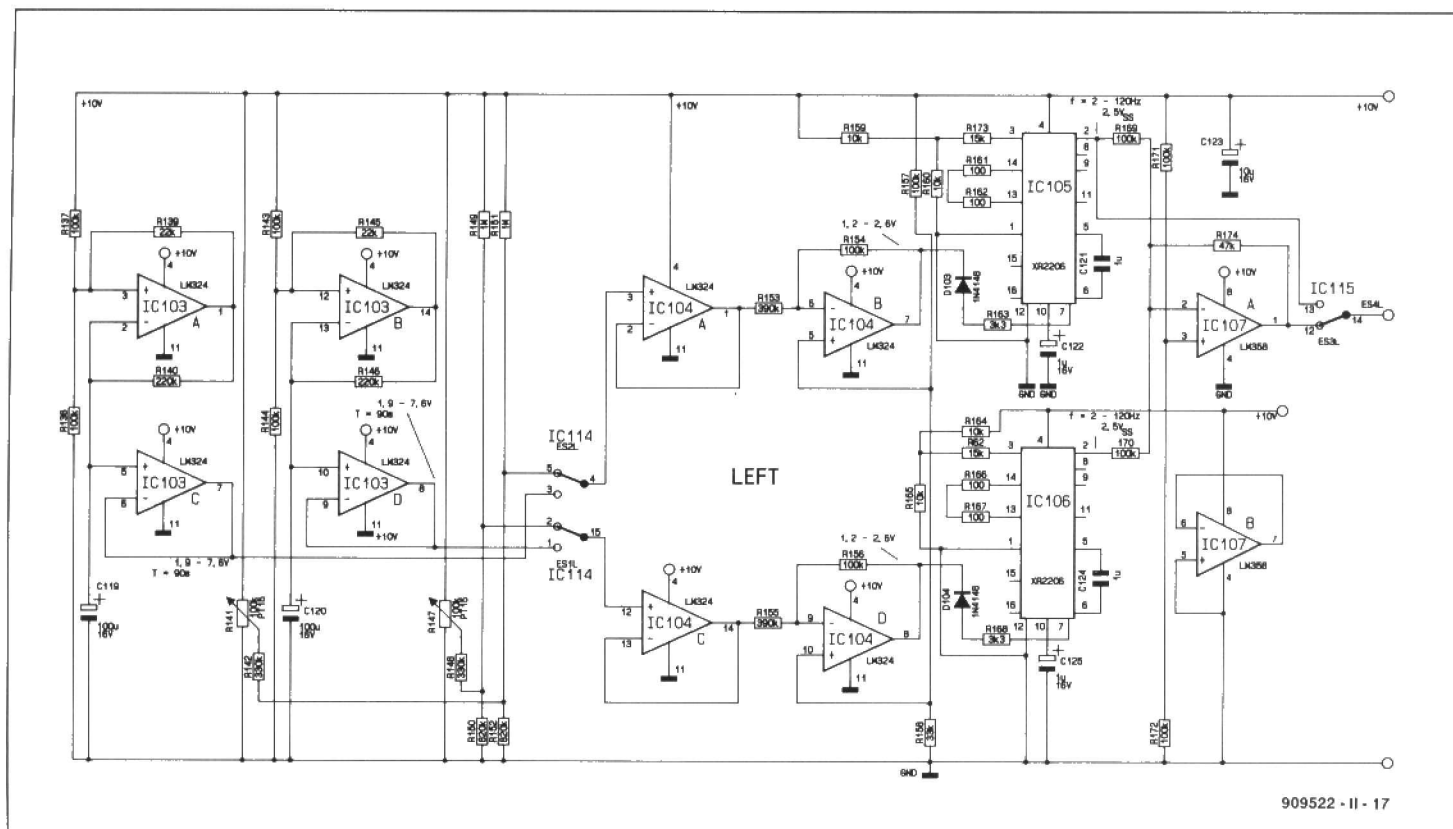
## Frequency compensation

As discussed last month, the deflection of the mirror galvanometers is frequency dependent, i.e., not linear. To linearize the response, a frequency compensation circuit is used —



# LIGHT SWITCH WITH TV REMOTE CONTROL

**Why not use the infra-red remote control, that magic little box supplied with every TV set these days, for applications other than channel hopping and turning the volume up when your favourite pop group appears on the screen? The simple IR receiver discussed here responds to most types of TV remote controls, and can be used to switch lights and other appliances on and off.**

**J. Ruffell, from an idea by M. Dupessey**

**P**RACTICALLY all TV sets these days are supplied with an infra-red remote control. Provided they have not been dropped too often, or chewed on by our beloved pets (we mean domestic animals including parrots and budgerigars), these handy little boxes allow us to remain comfortably seated in front of the 'tube' and exercise total control over the channel selection and a plethora of other settings of the TV set.

As shown in this article, it is perfectly possible to use a remote control box for an application not foreseen by the manufacturer. The general idea is illustrated in Fig. 1: here, the IR remote control is used to switch a light on and off. In some cases, it is even

possible to switch the TV set on and off as well, although this requires a small change in the receiver. Note, however, that many modern TV sets already have a standby/active function controlled via the IR box.

## Single-chip IR receiver

The IR receiver is based on an integrated circuit Type TDE4061 from Siemens. The internal diagram of the chip is given in Fig. 3. The main technical characteristics are:

- Low stand-by current: 650  $\mu$ A;
- Supply voltage range: 4 V to 6.5 V;
- Frequency range up to 200 kHz

- Available with and without demodulator output (TDE4061/TDE4060);
- No inductor required in external circuit;
- High ambient light rejection;
- Bipolar technology couples good high-frequency behaviour with a low current consumption;
- Suitable for battery supply.

The input of the TDE4061 (see Fig. 3) is connected to an infra-red photodiode, which unfortunately not only 'sees' the signal from the IR remote control box, but also visible light, 100-Hz interference from incandescent bulbs, and a part of the light spectrum emitted by fluorescent tubes.

The input stage is followed by a bandpass filter that serves to extract the IR remote control signals from the interference. The demodulator block drawn in Fig. 3 is not available in the TDE4060.


A current sink circuit is provided to suppress low-frequency currents supplied by the photodiode, and stabilize the bias at the input of the IR preamplifier at 1.4 V. The gain of the preamplifier is automatically controlled to ensure optimum drive of the bandpass filter.

The IFR (infra-red) input of the TDE4061 forms a high impedance, and is suitable for input currents in the nano-ampere range. Hence, the anode of the photodiode is connected direct to the IFR input.

The output of the TDE4061, Q, supplies a demodulated digital signal. An example of an output signal is shown in Fig. 2 for the Aristona (Philips) remote control Type RC4520. Note that the pulse lengths, T1 to T4, shown in the diagram depend on the IR remote control used.
 
## Circuit description

As shown in Fig. 4, very little is required to build an IR receiver based on the TDE4061. In the following description, some points will be noted that may be of interest to those of you who want to use the TDE4061 for their own applications.





The IR photodiode, D3, is a Type BPW41N from Telefunken. It is forward biased via resistor R5, and supplies a photocurrent to the IFR input of the TDE4061.

Capacitor C1 and resistor R5 form a low-pass filter at the IFR input that serves to suppress interference. The capacitor at the C<sub>REG</sub> input of the TDE4061, C5, determines the time constant of the preamplifier. The value of this capacitor is set to 470 nF to suit the bi-phase-coded signals emitted by most modern IR remote controls. The capacitor must be made smaller when an IR system is used that does not supply run-in signals for the gain control circuit of the receiver. In these cases, C5 may be reduced to about 10 nF. Do not go lower than this value to prevent oscillation.

The capacitor at the C<sub>S</sub> input of the TDE4061, C7, gives the preamplifier a high-pass characteristic, and works in conjunction with G<sub>REG</sub> and the double-T network at the RC1 and RC2 connections of the IC. These components determine the settling behaviour of the TDE4061 following fast signal changes. The C<sub>S</sub> capacitor tunes the receiver to the carrier emitted by the IR remote control. Depending on the carrier frequency, C7 is 100 nF (for 30 kHz systems) or 10 nF (for 120 kHz systems).

The bandpass filter that follows the IR preamplifier improves the signal-to-noise ratio of the IR signal and reduces the jitter on the digital output signal. The external double-T R-C bandpass filter connected to the RC1 and RC2 pins of the TDE4061 must provide a d.c. path, and have a band-stop (notch) characteristic. The notch frequency,  $f_c$ , is made equal to the IR carrier frequency. It is given by

$$f_c = 1/(RC) \quad [\text{Hz}]$$

where  $R=R_6=R_7$ , and  $C=C_9=C_2$ . Note that  $R_8=R/2$ , and  $C_8=2C$ . To keep the voltage drop across the filter within reason, R must not be made larger than 100 kΩ. The values

 


Fig. 1. The remote control supplied with the TV set is used to control a light.

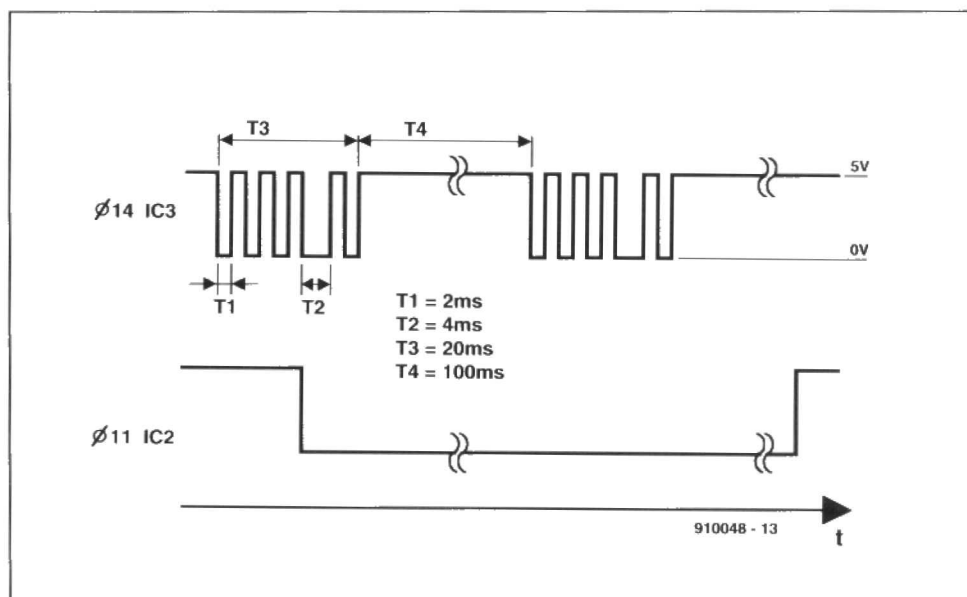


Fig. 2. Response of the TDE4061 to a typical datastream produced by a TV remote control.

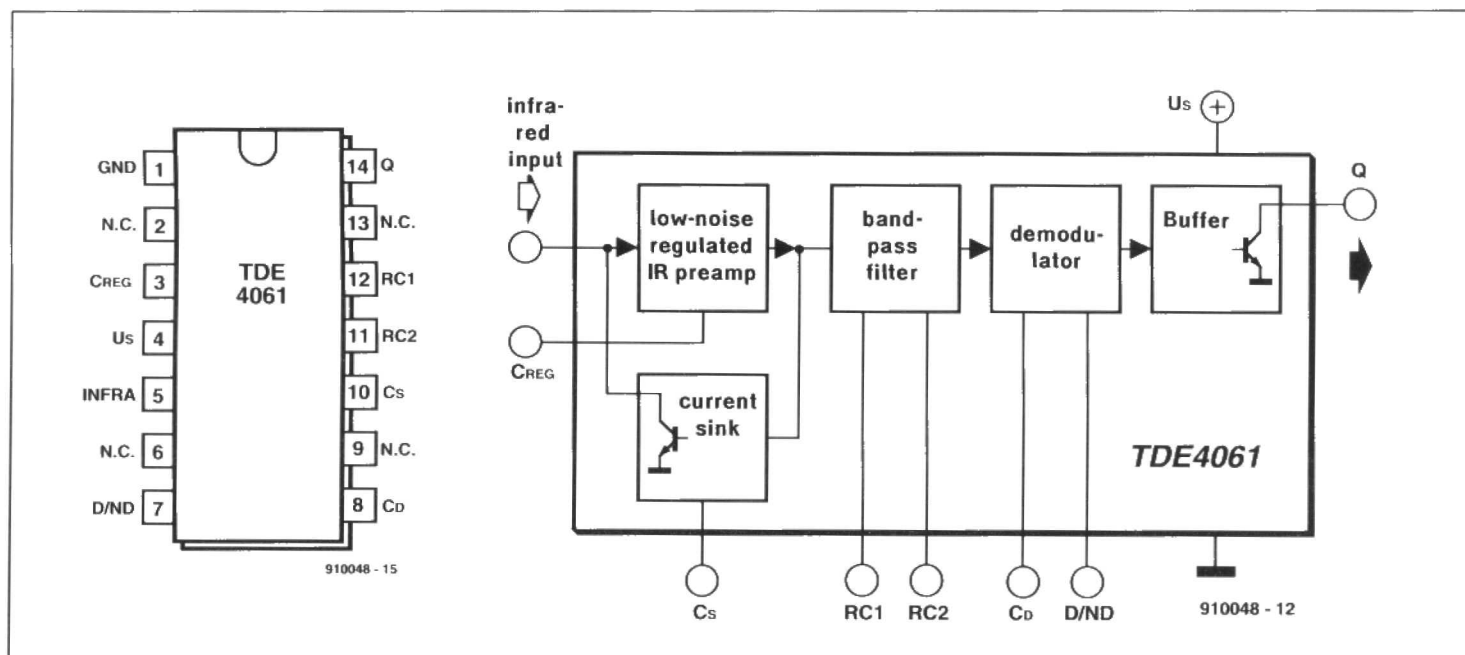


Fig. 3. Functional diagram and pinning of the TDE4061 infra-red receiver IC from Siemens.

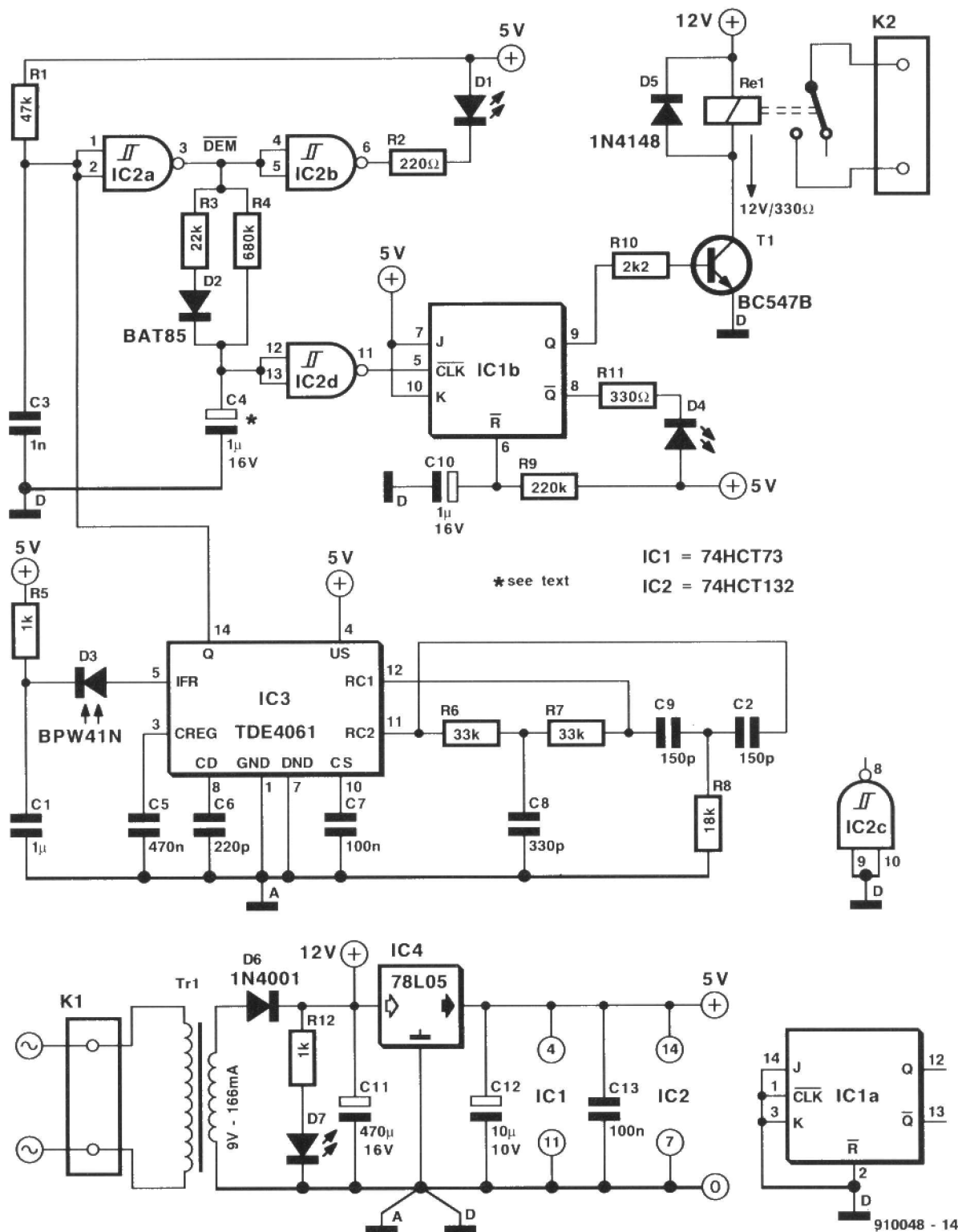


Fig. 4. Circuit diagram of the remote control receiver. The load to be switched is connected to the contact of relay Re1.

of the external filter components may have to be changed experimentally to suit the previously mentioned pulse lengths supplied by the IR remote control.

The output of the TDE4061, Q, is of the open-collector type. When the output transistor is switched on, the maximum collector current is 1 mA. In designs where the output signal is fed back to the input, oscillation may occur if the output current is not kept smaller than about 200  $\mu$ A. Note that this

type of feedback is not applied in the present circuit.

The digital pulse train supplied by the TDE4061 is inverted by a Schmitt-trigger gate, IC2a, and subsequently rectified by D2-C4 to obtain an on/off control signal. Every trailing edge of the switching signal supplied by IC2a causes J-K bistable IC1b to toggle, so that the relay, Re1, is actuated or de-actuated. This creates a simple on/off toggle function.

The load controlled via the IR system is connected to the contact of Re1. LED D1 lights in the rhythm of the pulses when an IR signal is received. When the Q output of IC1b is logic high, transistor T1 conducts, and the relay is actuated. The complementary output,  $\bar{Q}$ , of the bistable is then low, and LED D4 lights to indicate the relay status.

The response of the receiver to IR control signals is determined by the value of C4. This capacitor effectively turns the pulse train

 


Fig. 5. Single-sided printed circuit board for the IR remote control receiver.

## COMPONENTS LIST

### Resistors:

1 47k $\Omega$	R1
1 220 $\Omega$	R2
1 22k $\Omega$	R3
1 680k $\Omega$	R4
2 1k $\Omega$	R5;R12
2 33k $\Omega$	R6;R7
1 18k $\Omega$	R8
1 220k $\Omega$	R9
1 2k $\Omega$	R10
1 330 $\Omega$	R11

### Capacitors:

1 1 $\mu$ F solid	C1
2 150pF	C2;C9
1 1nF	C3
1 1 $\mu$ F 16V (see text)	C4

1 470nF	C5
1 220pF	C6
2 100nF	C7;C13
1 330pF	C8
1 1 $\mu$ F 16V	C10
1 470 $\mu$ F 16V	C11
1 10 $\mu$ F 10V	C12

### Semiconductors:

1 green LED dia. 3mm	D1
1 BAT85	D2
1 BPW41N (Telefunken)	D3
1 yellow LED dia. 3mm	D4
1 1N4148	D5
1 1N4001	D6
1 red LED dia. 3mm	D7
1 BC547B	T1

1 74HCT73	IC1
1 74HCT132	IC2
1 TDE4061 (Siemens)	IC3
1 78L05	IC4

### Miscellaneous:

1 3-way 5mm pitch PCB terminal block	K1
1 2-way 5mm pitch PCB terminal block	K2
1 12V/330 $\Omega$ PCB mount relay, e.g., Siemens V23127-B2-A101	Re1
1 9V/166mA PCB-mount mains transformer, e.g., Monarch VTR-1109/IV	Tr1
1 Printed circuit board	910048

into an on/off pulse with a much longer period. This is achieved by a relatively small resistor and a diode, R3-D2, through which the capacitor charges, and a relatively large resistor, R4, through which the capacitor discharges.

The receiver is completed by a standard 5-V regulated supply based on an 78L05, IC4.

## Construction

The IR receiver is a compact unit because all components are fitted on a single printed-circuit board, which is shown in Fig. 5. Start the construction by fitting the three wire links on the board. Next, fit the resistors, the diodes, the capacitors, and the active components. Use sockets for the ICs, which are not

plugged in until the board is completely assembled.

Complete the construction of the board by mounting the transformer, the relay and the soldering pins. The three LEDs are fitted such that their faces protrude from holes in the plastic enclosure. The infra-red diode, D3, is fitted on the front panel of the case. It is secured such that its light-sensitive area can 'see' the remote control. The light-sensitive area of the BPW41N is located at the centre of the flat front side of the device.

After finishing the construction of the PCB, connect the mains cable to K1, a 3-way PCB mount terminal block of which the centre pin is cut off. Next, connect the load to K2.

To enable you to experiment with differ-

ent values, the PCB allows capacitors with two different lead spacings to be fitted in positions C3, C7 and C13.

## Practical use

With most remote control boxes the usable range of the receiver will be greater than 5 metres. Since the response time of the receiver is relatively short at a few tens of milliseconds, the unit must be installed at some distance from the TV set to prevent it being triggered by control commands intended for the TV set. If you still want to locate the receiver close to the TV set, increase the value of C4 to, say, 47  $\mu$ F. This results in a much longer response time to remote control commands.

# APPLICATION NOTES

The contents of this article are based on information obtained from manufacturers in the electrical and electronics industry and do not imply practical experience by *Elektor Electronics* or its consultants.

## UHF AUDIO/VIDEO MODULATOR TDA5664X (Siemens Components)

**T**HE new TDA5664X from Siemens Components is an integrated circuit that contains all functions required to mix and modulate video and audio signals at frequencies between 30 MHz and 860 MHz. The new TV modulator IC is intended for use in video recorders, cable network converters, video pattern generators, closed-circuit TV systems, amateur TV transmitters and personal computers.

The advantages of the TDA5664X over its predecessor, the TDA5660P, are:

- 5-V supply voltage;
- no circuit adjustment required;
- reduced external circuit;
- smaller package (DIP14);
- also available in SMA package (SO14);

In addition to these advantages, the TDA5664X has the following specific features:

- FM sound modulation;
- sync-pulse clamping circuit at video input;
- clipping at peak white level;
- continuously adjustable modulation depth for positive and negative video modulation;
- high residual carrier suppression;
- low spurious radiation.

### Block diagram

The composite video signal with negative-going synchronization pulses is applied to pin 8 via a coupling capacitor (see Fig. 1). The on-chip clamping circuit fixes the video signal level relative to the synchronization pulses. When the video signal exceeds 1 V, the peak white level is clipped. Negative AM video signal modulation is selected by leaving pin 9 of the IC non-connected. When pin 9 is connected to ground, the RF carrier is positively modulated. If desired, a variable resistor may be connected between pin 9 and ground to enable the modulation depth to be controlled.

The TDA5664X is capable of modulating video as well as sound. The audio signal is capacitively coupled to the AF input of the IC, pin 13. A pre-emphasis network may be connected externally. The output signal of the audio input amplifier is frequency-

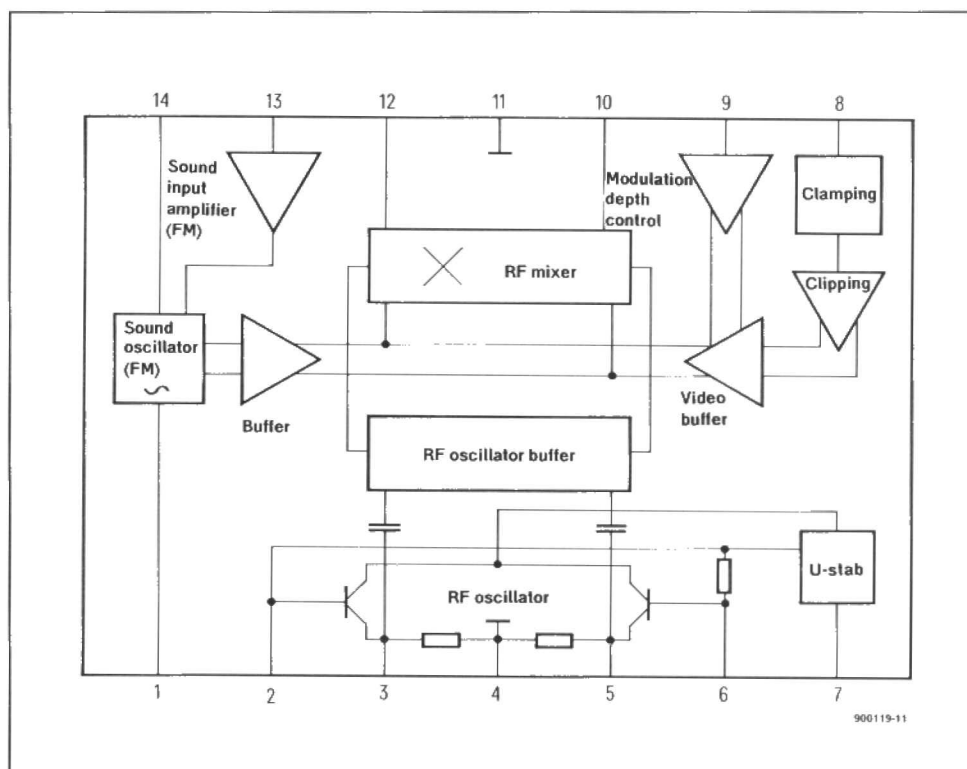


Fig. 1. Block diagram of the TDA5664X modulator IC.

modulated on to a 6.0 MHz (UK) or 5.5 MHz subcarrier. The output signal of the subcarrier oscillator is mixed with the output signal of an on-board RF oscillator. The operating frequency of the sound subcarrier oscillator is determined by an external L-C parallel tuned circuit connected between IC pins 1 and 14. This tuned circuit may be damped by an external resistor, R5, to set the sound subcarrier amplitude with respect to the vision carrier amplitude.

The amplifier that forms part of the RF oscillator is connected to external frequency determining components via pins 2 and 6 of the IC. At the resonant frequency, the capacitive reactance,  $X_c$ , must be  $70 \Omega$  between pins 2-3 and pins 5-6, while  $X_c = 26 \Omega$  must be observed between pins 3-5. The ground connection of the RF oscillator, pin 4, must be connected to the screening can of the inductor. An external oscillator signal may be applied to the TDA5664X via pins 2 and 6.

Table 1. Application circuit specification

Parameter		Min.	Max.	Unit
Supply voltage	$U_s$	4.5	5.5	V
Video input frequency	$f_{VID}$	0	6	MHz
Audio input frequency	$f_{AF}$	0	20	kHz
Output frequency	$f_o$	30	860	MHz
Operating temperature	$T_a$	0	70	°C
Subcarrier frequency	$f_{osc}$	4	7	MHz



This signal may be coupled inductively or capacitively.

For optimum operation and minimum spurious radiation, the oscillator pins (2 to 6) must be screened from the modulator output pins (10, 11 and 12). The RF attenuation of this screening must be 80 dB or greater.

## Application circuit

The circuit diagram of a TDA5664X-based UHF TV modulator is shown in Fig. 2. The balanced mixer outputs, pins 10 and 12, are connected to a wideband balanced-to-unbalanced (balun) transformer, which ensures a phase difference of exactly 180°. The basic construction of this balun on a two-hole ferrite core is shown in Fig. 3. The attenuation of the device must be smaller than 3 dB at the

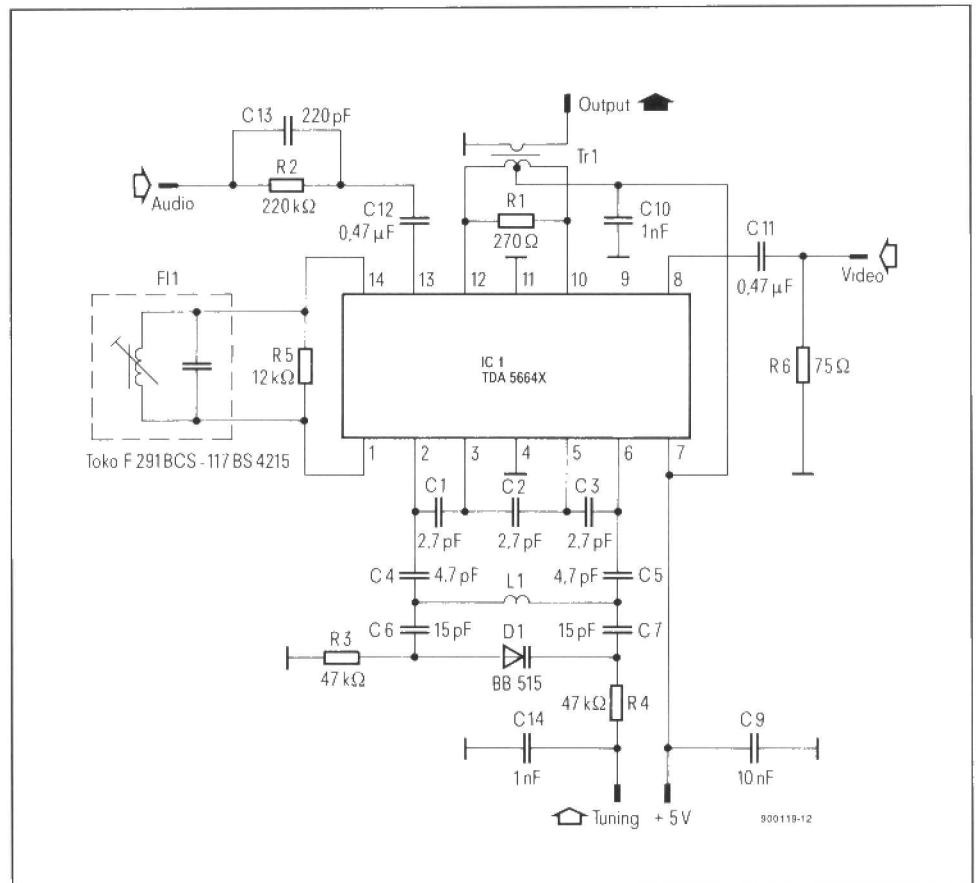
 


Fig. 2. Application circuit of the TDA5664X: a UHF audio/video modulator. The circuit is tuned to the desired TV channel by applying a tuning voltage to the varicap diode, D1.

frequency of operation.

Because of the impedance change from 270  $\Omega$  balanced to 50  $\Omega$  unbalanced, the RF output voltage of the modulator is about 1.5 times the RF voltage across R1. This is based on the assumption that the balun has an attenuation of 0 dB.

Finally, a suggested PCB design for the modulator based on the SMA version of the TDA5664X is shown in Fig. 3. The design of

this PCB meets the requirements as regards decoupling and minimum stray inductance in the oscillator as well as the modulator output circuitry. The modulator is tuned to a TV channel between 30 and 40 (i.e., between 543.25 MHz and 623.25 MHz) by applying a voltage to the TUNING input. ■

Source:  
Siemens Components issue 28 (3/90).

## COMPONENTS LIST

### Resistors (SMA):

1	270 $\Omega$	R1
1	220k $\Omega$	R2
2	47k $\Omega$	R3;R4
1	12k $\Omega$	R5
1	75 $\Omega$	R6

### Capacitors:

3	2pF7 SMA	C1;C2;C3
2	4pF7 SMA	C4;C5
2	15pF SMA	C6;C7
1	10nF SMA	C9
2	1nF SMA	C10;C14
2	470nF 5mm	C11;C12
1	220pF SMA	C13

### Semiconductors:

1	BB515	D1
1	TDA5664X SMA	IC1

### Miscellaneous:

1	B62152-A0008-X017 balun (Siemens)	Tr1
1	F291BCS-117BS4215 (Toko)	F1

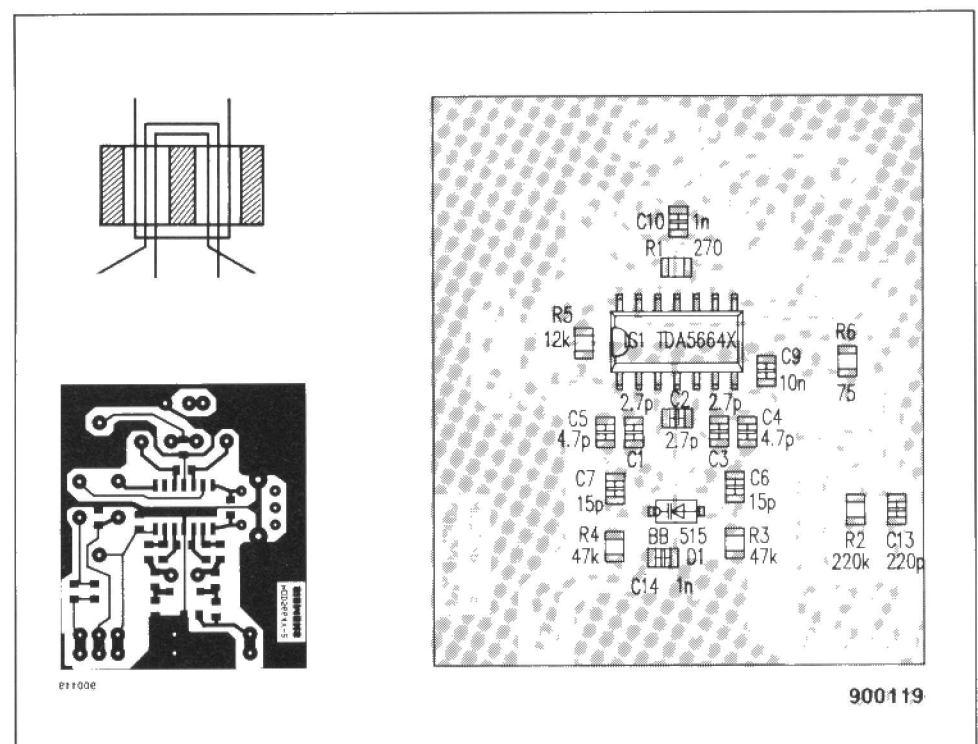


Fig. 3. PCB track layout (1:1), component mounting plan (2:1) and balun construction.

# REAL-TIME CLOCK FOR ATARI ST

**The Atari ST is a user-friendly computer supported by a massive amount of excellent software. Unfortunately, early models of the ST lack a clock circuit that keeps ticking when the computer is switched off. The circuit presented here overcomes this problem.**

**F. Dossche**

**A**LTHOUGH the design of the Atari ST computer is modern by any standard, a real-time clock (RTC) is provided only on the latest models. This is surprising because the main rival of the ST, the IBM PC or compatible, has had an RTC as an option or a standard feature longer than many of you will care to remember. Owing to the absence of an RTC, many Atari ST users are forced to set the date and time, every time the computer is switched on. To help out the thousands of faithful owners of older ST models, we have developed a real-time clock that is inexpensive and simple to build.

One of the most attractive features of the Atari ST is the number of interfaces. One of these interfaces, the printer port, is used here to connect the real-time clock to the computer. We hasten to add that you will be able to use the printer as before, since the RTC is inserted between it and the Centronics port, for which only a very small modification is required.

## Up-to-date with the RTC

Of the real-time clock ICs currently available, the MSM5832 from OKI and the MC146818 from Motorola are probably the best known and widest used. The Motorola IC has an advantage over the MSM5832 in offering an 8-bit wide databus, and a 50-byte non-volatile RAM (random access memory). The data retention is achieved with an external rechargeable battery.

Here, the Motorola IC is used, although no use is made of its internal RAM. The 8-bit databus of the RTC chip allows the control software to be kept fairly simple, and in addition affords the possibility to implement further extensions circuits on the Centronics port. The control software for the present project is supplied on disk in the form of a source listing written in C. This program may be used as the basis for further hardware or software functions that you may wish to add. The hardware presented here, and the object code compiled with the aid of the C program, can be used to develop a 'desk accessory' to support the new clock function.

Returning to the hardware, the circuit diagram of the clock extension is shown in Fig. 1. The heart of the circuit is the RTC chip from Motorola. Besides four logic gates and


two bistables, the circuit contains a handful of discrete parts used mainly to implement a battery back-up function for the RTC. The two bistables and one I/O line on the computer's main board serve to direct the data on the Centronics bus either to the printer or the real-time clock. In addition, one of the bistables indicates whether the 8-bit word sent to the clock circuit is intended to select an address location, or to be stored as data in the RTC.

The real-time clock sits between the Centronics port on the computer and the Centronics input of the printer. Hence, it has an input an output connector.

At the left in the circuit diagram we find connector K1 which links the circuit to the computer. Two new signals appear on this connector on pins 16 and 17. Pin 16, normally the RESET line, is not used by the Atari

ST, and now carries the computer's 5-V supply voltage. Since the RESET signal is active low according to the Centronics standard, placing +5 V on pin 16 has no effect on the printer (anyway, the ST is not capable of issuing a reset via this line).

Pin 17 of K1 is connected to an unused I/O line in the computer, and serves to direct data either to the RTC or to the printer. The I/O line is found on pin 14 of the sound generator IC in the ST, the Yamaha YM-2149. Although not used in the hardware of the ST, this I/O line is supported by the BIOS (basic input/output system), which makes it perfect for the present application. Pin 17 on the Centronics connector is chosen because it is not used on the ST or the printer. Do, however, check that the cable between the computer and the RTC has a wire for the signal on pin 17. In general, most serial cables for

 

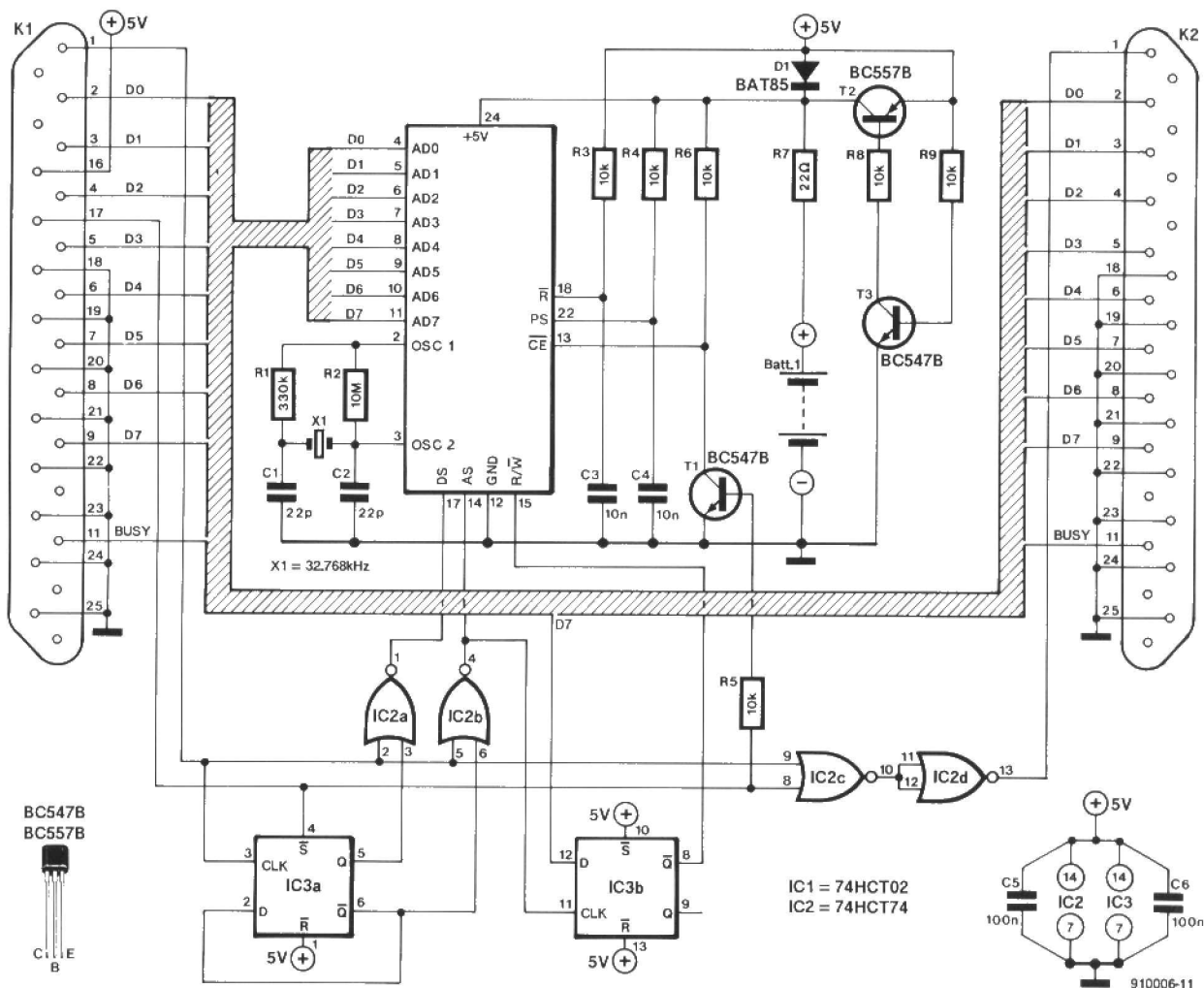


Fig. 1. Circuit diagram of the real-time clock.

PCs have a wire for each of the 25 pins, and will, therefore, meet our requirement. You may also decide to make your own 25-way cable, which has the advantage that it can be made shorter than most ready-made cables. These are usually 1 m or 2 m long, and quite bulky for our application. A home-made cable may be produced by a short length of 25-way ribbon cable terminated in an IDC-style male 25-way D-connector at one end, and a female D-connector at the other end.

Returning to the circuit diagram, the signal at pin 17 of K1 enables bistable IC3a by making the  $\bar{S}$  line logic high. This results in any changes at the set and the reset inputs of IC3a being ignored, so that the bistable remains in the 'set' state because the SET line was active last. Also, the strobe signal for the printer (connected to K2) is blocked by gates IC2c and IC2d, and the enable input of the RTC is actuated via transistor T1. Next, an RTC address is passed to the circuit via the Centronics datalines. The most-significant bit, D7, indicates a read or a write operation to or from the RTC registers.

A pulse on the strobe line (pin 1 of K1) is fed to the AS input of the RTC chip via bistable IC3a and gate IC2b. This pulse is used to transfer an 8-bit word on the Centronics datalines to the RTC, or vice versa, as indicated by the level of databit D7. After the

strobe pulse, the inverted level of D7 is applied to the R/W input of IC1. When the next strobe pulse occurs, IC3a toggles because the Q output of this bistable is connected to its D (data-) input. The pulse is subsequently fed to the DS (data strobe) input of IC1 via IC2a. Data may be read before the end of the second strobe pulse. When this is finished, the computer will de-actuate the 'select' line (pin 17 on K1). The printer can then be used again, and the clock operates. The above sequence is used to store the time and date in the RTC, and also to read these back into the computer, allowing the system clock in the ST to copy the RTC information. Gone are the days when you had to set the system clock every time the ST was switched on.

The rest of the circuit is fairly simple. The PCB has two options for charging the battery. The simplest is by means of diode D1. When the ST is switched on, the battery is charged via D1 and R7. The RTC is also powered via the diode. This must be a Schottky type to ensure a low voltage drop. Remember, the charge current can become too small when the computer supply voltage is on the low side, when the battery voltage is on the high side. This is prevented by a diode with a low voltage drop.

If you can not secure the BAT85 or an equivalent Schottky diode, add the circuit

based on T2 and T3. When the computer is switched on, T3 starts to conduct and switches on T2. By virtue of the relatively low collector-emitter voltage of T2, the charge current for the battery is sufficiently high. When the computer is switched off, T3 blocks and turns off T2, so that the battery takes over the supply of IC1. Note that the transistor-based supply is an alternative to the single Schottky diode — components T2, T3, R8 and R9 are not fitted if you use a BAT85.

The RESET and PS inputs of IC1 are taken logic high briefly after the supply is switched on. This ends the low-power standby state of the RTC, and causes it to switch to normal operation.

A quartz crystal, X1, together with C1, C2, R1, R2 and two gates in IC2 form an oscillator that supplies a clock of 32.768 kHz to the RTC. This frequency is used in most battery-powered clocks and electronic wrist-watches.

## Construction

The construction of the real-time clock unit will present little difficulty if the printed-circuit board shown in Fig. 2 is used. Start the construction by fitting the wire links and the connectors. Note that K1 is a male type, and K2 a female type. If you swap them acciden-

 


Fig. 2. Single-sided printed circuit board for the real-time clock.

tally, you will be unable to connect the circuit properly to the input and output cables.

Proceed with fitting the remaining parts on the board. IC sockets are not strictly required. If you do decide to use them, be sure to buy good quality types.

The completed printed circuit board fits into an ABS enclosure of dimensions 120×70×30 mm. The side panels of the enclosure are cut to allow the connectors to protrude.

A small modification is required in the computer before the RTC can be connected. Although the 'operation' is really no more than soldering two wires, it may still take you an hour or so to complete because the computer has to be disassembled. After removing the floppy disk drive and the switching power supply module, you should be able to see the printer connector and the Yamaha chip. Take the main board out of the enclosure, and remove the metal screen at

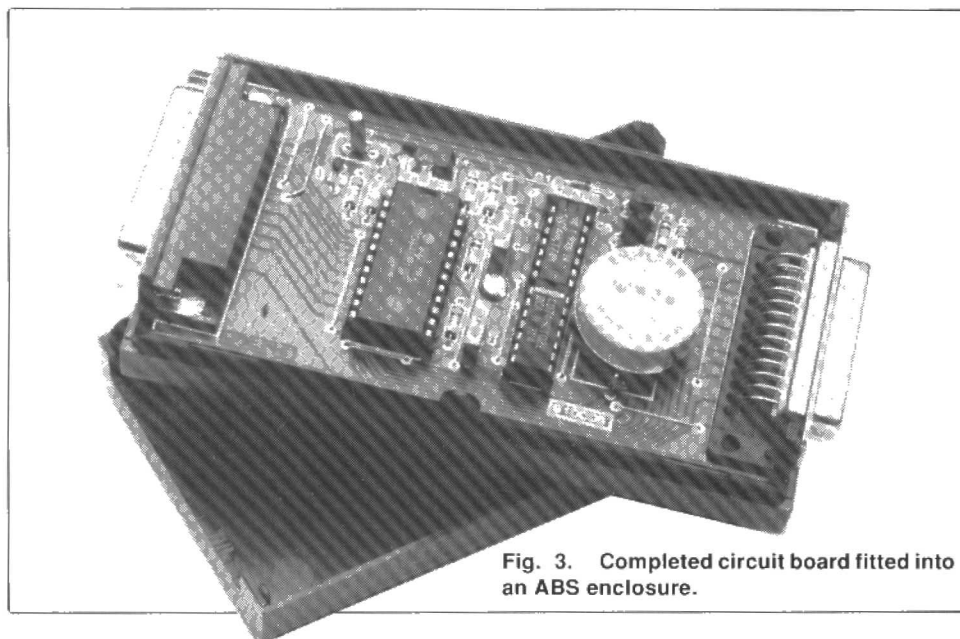


Fig. 3. Completed circuit board fitted into an ABS enclosure.

## COMPONENTS LIST

### Resistors:

1	330kΩ	R1
1	10MΩ	R2
6	10kΩ	R3-R6;R8;R9
1	22Ω	R7

### Capacitors:

2	22pF	C1;C2
2	10nF	C3;C4
2	100nF	C5;C6

### Semiconductors:

1	BAT85	D1
2	BC547B	T1;T3
1	BC557B	T2
1	MC146818	IC1
1	74HCT02	IC2
1	74HCT74	IC3

### Miscellaneous:

1	25-way male sub-D connector with angled pins, for PCB mounting	K1
1	25-way female sub-D connector with angled pins, for PCB mounting	K2
1	32.768 kHz quartz crystal	X1
1	3.6V NiCd battery	Batt.1
1	ABS enclosure; size approx. 120×70×30mm	
1	Printed circuit board	910006
1	Diskette with control software	ESS1621

both sides. This means that you have to bend a couple of small metal brackets with the aid of tweezers. After turning the main PCB, you should have access to the sound generator connections. Run a wire from pin 14 of the Yamaha chip to pin 16 of the printer connector, and another wire from pin 40 of the Yamaha chip (+5 V) to pin 17 of the printer connector. This completes the modification. Re-assemble the computer.

## Software

As usual, hardware is never complete without the appropriate software. The clock unit described here is supported by a control program on disk, which may be ordered through our Readers Services. The disk contains the ready-to-go desk accessory for the clock, as well as the source listing used to compile the machine code. As already mentioned, this listing is intended for those of you who want extra features for the clock, such as a programmable alarm. You may also want to use the 50-byte non-volatile RAM area in the RTC chip.

The source code can be converted into a control program with the aid of, for example, the Mark-Williams C compiler. This is not strictly required, though, since you can simply copy the control program on the floppy disk (supplied by us) to your system disk. Every time the computer is switched on, the program will automatically copy the RTC data to the system clock. Now, is that up-to-date or not?



# STEPPER MOTOR BOARD

## PART 1: PC INSERTION CARD AND CONTROL SOFTWARE

**Getting a stepper motor to work properly invariably seems to require either a lot of discrete electronics, or an expensive dedicated integrated circuit. However, since the actual commands for stepper motors are almost always supplied by a computer, it is a challenging idea to economize on the hardware, and have the software do the work.**

**H. Kolter**

**S**TEPPER motor controls are available in many shapes and sizes, ranging from complex to ultra-simple, and based on a variety of integrated circuits, including the MC3479, the L297/298 and the TDA1024, all of which have been used in projects described in this magazine. By contrast, the control described here is not based on any of these ICs. None the less, it is versatile, simple to build and relatively cheap.

The circuit described has evolved as part of a PC-controlled professional milling machine that accepts CNC-format data to the Gerber standard. CNC stands for computer numerical control.

### The concept

The above application was aimed at developing a complete milling machine for very ac-

curate processing of aluminium, steel and plastic workpieces. When the project was initiated, there was the choice between (1) 'intelligent' motor control with relatively simple control software, and (2) a simpler controller with powerful, complex, software. To ensure the best possible results in regard of speed and accuracy of the system, the first option requires the motor control to be geared accurately to the specific features of the milling machine.


The second option has the advantage that changes to the machine, or extensions, are easier to support with appropriate software extensions. Since the electronics and the milling machine were developed roughly at the same time, the choice of the stepper motor control was clearly in favour of the second option: simple hardware and complex software.

In practice, the computing power required for the system can only be provided by a PC-AT or a compatible machine with a clock speed of at least 16 MHz. The computer program consists of an interpreter that reads drill and fraise data produced to the Gerber standard, and converts these into stepper motor commands.

The interpreter uses a configuration file that contains various system parameters such as the type of stepper motor (bipolar or unipolar, rotation per step, maximum step rate, etc.), and the main properties of the milling machine (spindle pitch, number of idle steps on spindle reversal, etc.). These parameters can be changed easily and allow the control system to be rapidly 'customized' for a particular application.

In line with the different functions, the electronics are divided into two parts. One part is an insertion card for IBM PCs, the other a larger board, which is fitted external to the PC, and contains the power drivers.

 The PC insertion card described here is basically a digital I/O card based on the familiar 8255 PPI (programmable peripheral interface) from Intel. The 'half-size' insertion



card offers 24 input/output lines, and has an additional timer/counter IC Type 8253, a quartz oscillator and two relays. The quartz oscillator makes the timing of the I/O card independent of the computer speed. The two relays have changeover contacts and are suitable for switching mains loads.

The power driver board (to be described in part 2 of this article) has a fairly large power supply and 16 optocouplers that afford electrical isolation between the computer and the stepper motors. TTL buffers are provided between the optocouplers and the 16 power drivers. These buffers are also used to drive a LED-based readout that signals the active status of all stepper motor windings. The readout will be found particularly useful when a machine is first connected, or during program debugging.

### Circuit description

The PC interface shown in Fig. 1 is a more or less standard design based on the 8255 PPI. Apart from the data and address signals, the extension card uses a few control signals on the IBM slot, IOWR which indicates write activity in the I/O memory area,  $\overline{\text{IORD}}$  which has the same function form read operations, and, of course, RESET. The extension card is powered by the computer via the extension bus.

The datalines are buffered with a 74LS245 octal bidirectional driver. The buffered datalines are connected to the PPI (the 8255) and the PIT (programmable Interface Timer/counter; the 8253). A single PAL (programmable array logic), IC3, handles all address decoding. It uses address line A3 through A9 and the IORD and IOWR signals to generate chip select signals CS0, CS1, CS2 and CS3, and in addition the enable signal and the direction control signal for the databus buffer, IC2.

The I/O lines of ports A and B of IC1 are available on a double row PCB pin header, K2. Port C is connected to the outputs of the programmable timer, IC5. Connections PC4 and PC5 switch the two relays via darlington transistors T1-T2. In most cases, a value of 1 k $\Omega$  will be adequate for R5 and R6. These resistors may need to be made smaller, however, when the relays do not come on reliably. The minimum value of R5 and R6 is 330  $\Omega$ .

PPI line PC3 has a special use here as it is connected to an external emergency switch that stops the entire system. Normally, PC3 is held at +5 V by a pull-up resistor, R4. The two remaining port lines, PC6 and PC7, are not used here.

The internal block diagram of the 8253 counter/timer is shown in Fig. 2. The three 16-bit counters, numbered 0, 1 and 2, are identical and can be preset to count down. The counters operate independently and can be programmed separately. The counter values can be read from the 8253 without blocking the clock signal. The preset values are loaded with the aid of four control words stored in the control word register. Since this has only one address, two bits, SC0 and SC1,

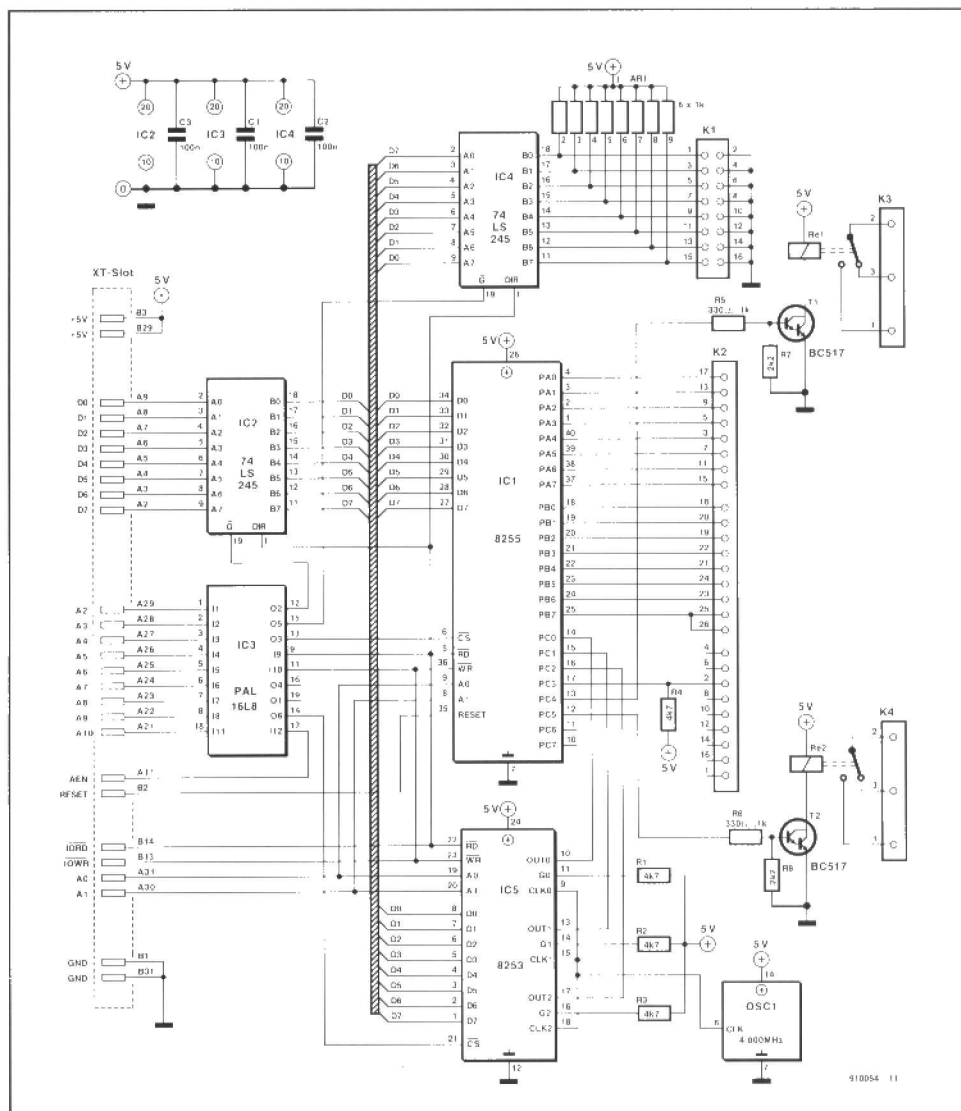


Fig. 1. Circuit diagram of the PC insertion card.

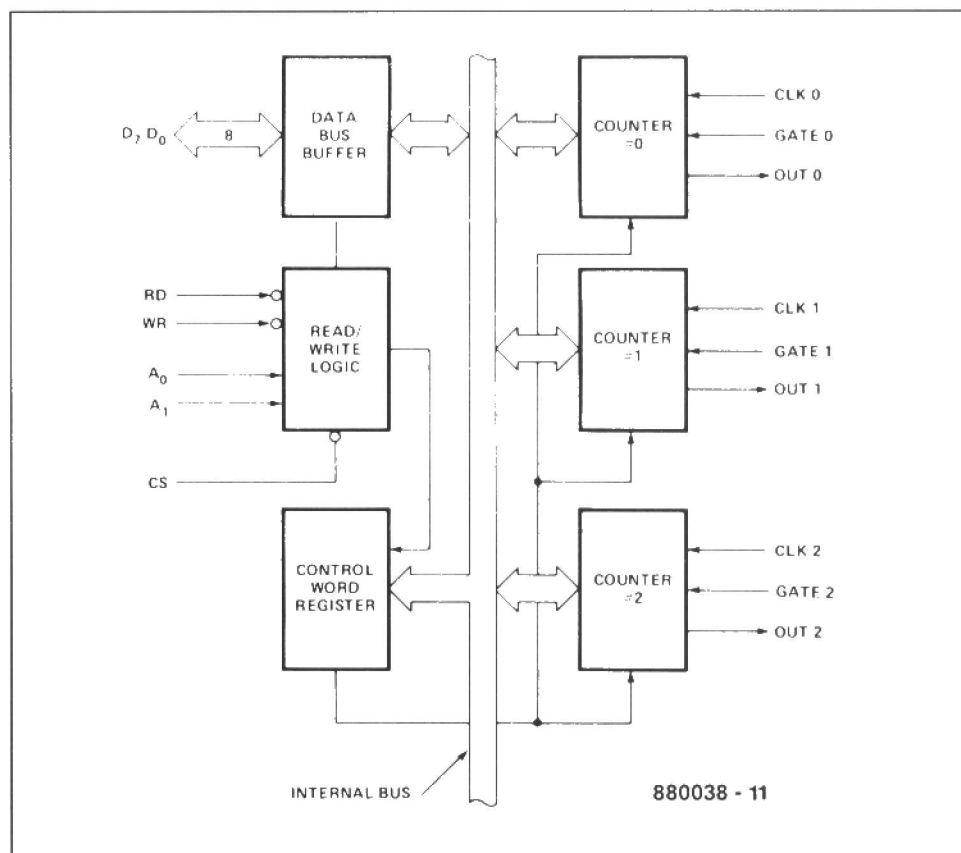


Fig. 2. Block diagram of the 8255 Programmable Peripheral Interface (PPI).

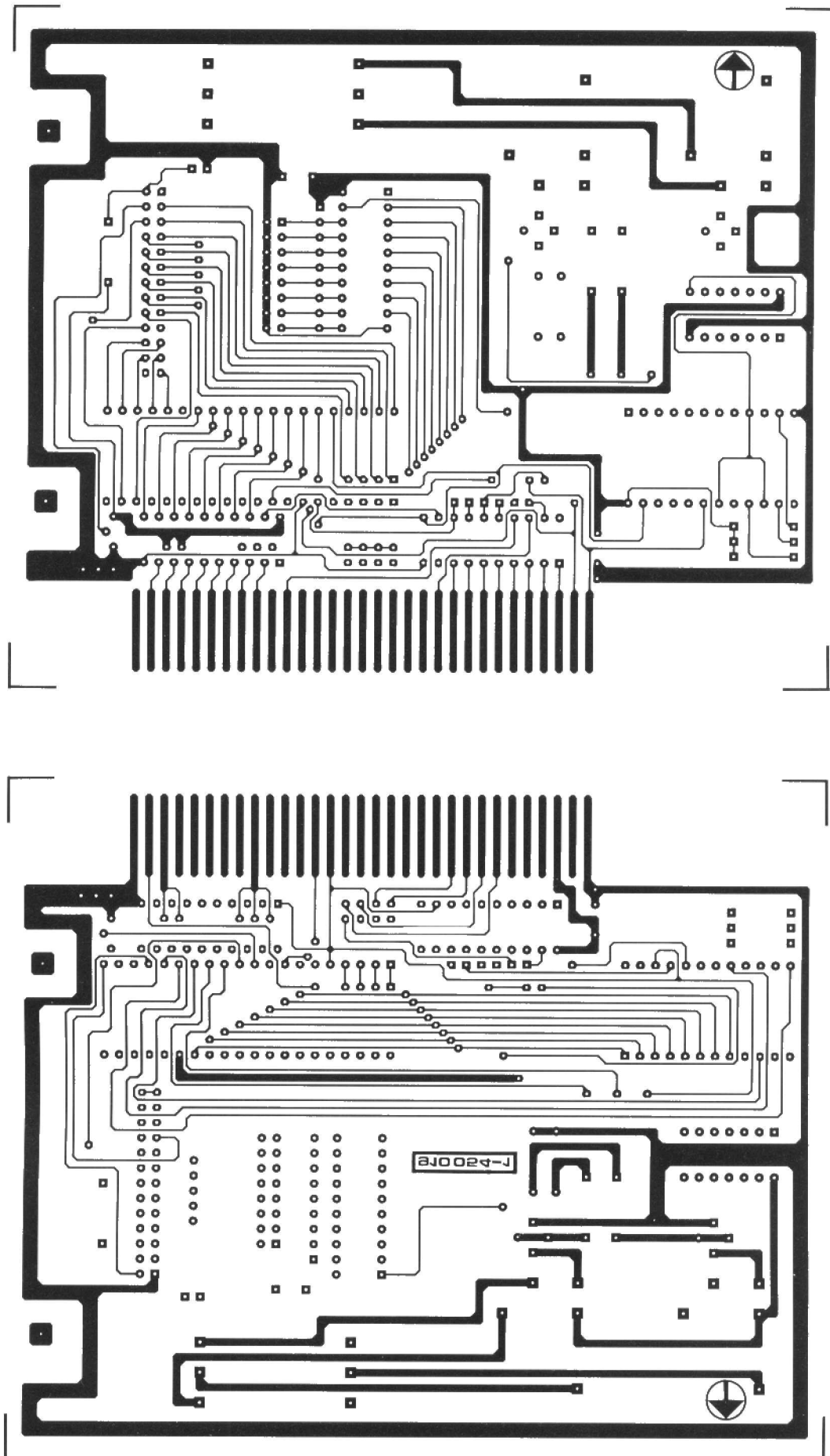


Fig. 3a. Track layouts of the component side and the solder side of the PC insertion card.

 


Fig. 3a. Component mounting plan of the PC insertion card.

## COMPONENTS LIST

### Resistors:

4	4k $\Omega$ 7	R1 - R4
2	1k $\Omega$ (see text)	R5;R6
2	2k $\Omega$ 2	R7;R8
1	8x4k $\Omega$ 7 array	AR1

### Capacitors:

3	100nF	C1;C2;C3
---	-------	----------

### Semiconductors:

1	8255	IC1
2	74LS245	IC2;IC4
1	16L8 (ESS 6011)	IC3
1	8253	IC5
2	BC517	T1;T2

### Miscellaneous:


1	4-MHz oscillator block	Osc1
2	PCB-mount 5V changeover relay	Re1;Re2
1	16-way 2-row PCB pin header	K1
1	26-way 2-row PCB pin header	K2
2	3-way PCB terminal block	K3;K4
1	printed-circuit board	910054-1

indicate the counter for which the control word is intended.

Returning to the circuit diagram in Fig. 1, the CLK0 through CLK3 inputs of the 8253 are supplied with a 4-MHz clock signal generated by oscillator block OSC1. All three gate (Gx) inputs of the counter/timer are

tied to +5 V via pull-up resistors.

 The 8253 is programmed to operate as a frequency divider. Depending on the preset value, a counter divides the oscillator frequency down to a particular value, for instance, 100 Hz, which is then passed to PPI port C. By loading different counter preset





values, the step duration of the stepper motors is made independent of the computer's speed.

IC<sub>4</sub>, a 74LS245, forms an 8-bit input port which is used to signal the status of a set of end switches fitted on the milling machine. The eight input lines of the port are held at +5 V with the aid of pull-up resistors. The end switches wired to K<sub>1</sub> should, therefore, connect to ground when active.

The address assignment of the ports on the insertion card, and their functions, are summarized in Tables 1 and 2.

## Construction

Populating the double-sided through-plated board (Fig. 3) should not cause difficulty. To make sure the card remains secure in the PC slot, you will need to secure it to a metal bracket as found on other insertion cards. Here, it is best to use (or make) a bracket with a relatively large vertical clearance that allows the two flatcables and the relay wires to pass.

Switch the computer off, fit the I/O card into a free slot, and secure the card to the metal frame at the rear of the PC. Switch on the PC, and check that a frequency of 4 MHz is present at pins 9, 15 and 18 of IC<sub>5</sub>. In case the PC will not boot up with the I/O card inserted, you are probably faced with a short-circuit on the board, or a faulty IC.

The data in Tables 1 and 2, and a few lines of BASIC or Pascal, allow the card to be checked for correct operation. For instance, reading address [base+8] (IC<sub>4</sub>) should return 1111 1111<sub>2</sub>, which equals FF<sub>16</sub>, or 256 decimal. Next, connect two or three jumpers to K<sub>1</sub> to pull the input datalines logic low. Run the read test again, when the result should match the set bit pattern (a jumper produces a logic low).

Next, test the PPI by writing to the control register at address [base+3] (0DE3<sub>16</sub>). Set all ports to output, then make all port lines logic high. The relays should come on.

The scope of this article does not allow a more detailed description of the way in which the 8255 and the 8253 are programmed. Fortunately, plenty of literature is available that covers the practical use of these ICs in great detail.

## Software

A number of different, fairly complex computer programs are required before the fraising machine can be made to work. The first step in making a fraised product is to draw it with the aid of a CAD program, such as AutoCAD or AutoSketch, and save the drawing file in the DXF format. Next, a program called AutoPack-II is used to convert the DXF file into a format suitable for further processing. AutoPack-II is a 2½-dimension version of the 3-dimension program AutoPack. None the less, AutoPack-II allows you to view the workpiece in 3-D to the ISO standard. Also, all side views of the workpiece can be displayed at the same time, and the program is capable of calculating the

### G routines supported by CNC-DIN

All dimensions in mm, DIN 66025.

#### Example of Syntax:

10 G00 x17.34 y200.0

20 G01 x10.90 y20.90

%	start of program
	remark
G00	Target point direction characteristic (x, y, z). Move to target point. Fraise carrier speed.
G01	Straight interpolation of target point (x, y, z). Fraise from current point to indicated target point. Fraise speed.
G02	Circle interpolation, clockwise. (xakt, yakt, x, y, i, j) current point (xakt, yakt), target point (x, y), centre of circle (i, j). Fraise an arc based circle information, from current point to target point.
G03	Circle interpolation, anti-clockwise. See G02.
G04	Spindle idle time. (f) idle time in seconds.
M58	Switch of spindle motor relay.
M59	Switch on spindle motor relay.
M08	Switch on pump for drill coolant.
M09	Switch off pump for drilling coolant.
G90	All absolute data.
G91	All incremental data.
G94	Spindle shift speed in mm/min. (x, y, z) speed indication for single spindle.
M30	end of program.

Fig. 4. Overview of Gerber commands supported by the CNC-DIN converter program.

curve described by the fraise. This curve is called fraise equidistant because the radius of the fraise itself is taken into account.

The fraise file generated by AutoPack-II consists of a set of so-called Gerber commands. The actual control software for the milling machine is a converter called CNC-DIN. Written in C, it reads the Gerber data and converts these into commands for the stepper motor board described here. CNC-DIN is available from the author, and allows you set a number of parameters related to the hardware. These parameters include the type of stepper motor used (2-phase or 4-phase), the number of steps per revolution, etc. The parameters and their settings are stored in a configuration file that can be modified as required for your own hardware. Figure 4 lists the G (Gerber-) functions to DIN-66025 that are supported by CNC-DIN.


#### Note:

The program CNC-DIN mentioned in this article is available from  
Kolter Elektronik • Steinstrasse 22 • W-5042  
Erfstadt • Germany. • Telephone: +49 (2235) 76707, Fax: +49 (2235) 72048.

 Part 2 of this article will describe the motor driver board. Tables 1 and 2 mentioned here will be included in Part 2.







# NICAM!

## ...set your sights on a better sound!

**E**xperience a new sensation. An experience that opens up a whole new spectrum of sound.

Put yourself on stage at the Albert Hall, surrounded by a great orchestra. Imagine the sound you will hear, every nuance, every note; or travel up the Nile with an intrepid explorer, a journey not only full of breathtaking beauty and colour, but rich in the sounds of another continent; or capture the hidden gasps of 100,000 hardened fans at Wembley for the F.A. Cup Final, when the ball skims the crossbar with the last kick of the match; follow with your ears as well as your eyes, dodging the bullets, as your favourite hero battles out of yet another tight corner, it's just like being in a cinema!

Nicam hi-fi stereo will turn your living-room into a living room of


sound! You don't settle for second best with television picture quality, why settle for second best in television sound quality? Nicam sound is the new high quality digital stereo sound system, pioneered by BBC, ITV and TV/video manufacturers. In fact so good is Nicam it is comparable to the superb sound reproduction of the compact disc, when played through your existing hi-fi arrangement. If your television hasn't got a built-in Nicam decoder, you will need the Maplin Nicam Tuner System. Ultimately almost all of your favourite programmes will be broadcast in superb hi-fi quality stereo-sound. Without a Maplin Nicam Tuner you won't be able to capture every sound to its full.

Nicam hi-fi stereo. Catch your breath, open your eyes, and pin back your ears! It's what your hi-fi system was made for... It's what your ears are made for!

### DIGITAL STEREO TV SOUND FROM YOUR HI-FI

The complete kit contains all the components required to build the unit. However you will also need: a power supply, 12V at 600mA regulated e.g. YZ21X at £9.95; a co-ax Y adaptor e.g. FS23A at £1.20; a co-ax lead to connect to your TV or video; RW36P 2m long at £1.36, JW39N 5m long at £1.98, or JW40T 10m long at £2.95; a phono lead to connect to your hi-fi e.g. RW50E at £1.06 or a SCART/Pentel lead JW36P at £5.95. An infra-red remote control kit is also available LP20W at £29.95.

 
**Complete kit LP19V only £149.95 incl. VAT + £1 mail-order handling charge.**



**Maplin ELECTRONICS**  
**CREDIT CARD HOTLINE**  
**0702 554161**

For a friendly welcome and the very best of service why not visit our shops in Birmingham, Brighton, Bristol, Leeds, London (Edgware and Hammersmith), Manchester, Newcastle-upon-Tyne, Nottingham, Reading, Southampton and Southend-on-Sea.

 *Subject to availability. Prices subject to change.*



Digital stereo sound companion for your TV set.